

Electronics

Advanced Subsidiary GCE

Unit **F611**: Simple Systems

Mark Scheme for June 2012

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, OCR Nationals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.


OCR will not enter into any discussion or correspondence in connection with this mark scheme.


© OCR 2012

Any enquiries about publications should be addressed to:

OCR Publications
PO Box 5050
Annesley
NOTTINGHAM
NG15 0DL

Telephone: 0870 770 6622
Facsimile: 01223 552610
E-mail: publications@ocr.org.uk

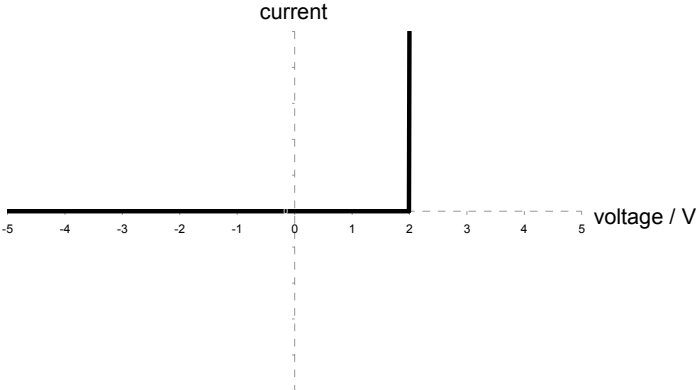Question			Answer	Marks	Guidance
1	(a)	B	flow of information through the system	1	accept information or signals
	(b)	(i)	C limits current/power in LED D so that the LED does not overheat	1 1	reduces voltage across LED/5 V is too high for the LED prevents damage <u>by too much current/power</u> Not blown
		(ii)	C Vout=5V A Voltage across R is 5-2=3V D I=1.5mA=0.0015A E R=3/0.0015 (ecf) B R=2000Ω	1 1 1 1 1	Evidence of output voltage of gate used Evidence of subtracting 2v from output Correct conversion from milli or use of kΩ in answer Correct use of Ohm's law Correct answer
		(iii)	D line at zero current for negative voltages E line rises <u>steeply</u> from x-axis at ~2V 		Accept graph which shows v. small current below threshold and then curve and steep gradient. Positive line within region 1.5 V – 2.5 V must touch 2V

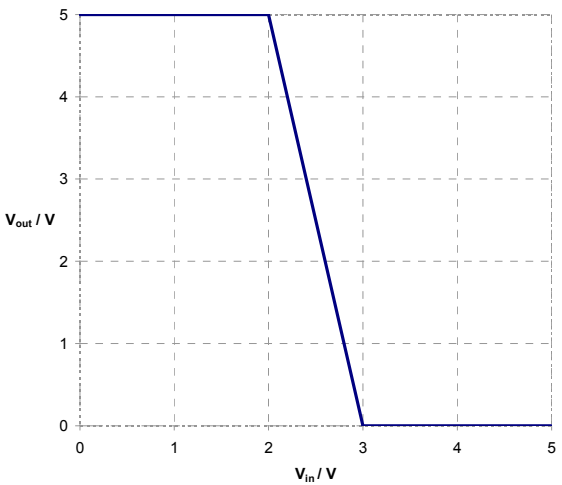Question		Answer	Marks	Guidance
(c)	(i)	<p>D 5V When V_{in} 0V – 1V</p> <p>D 5V at start 0V at other end of scale</p> <p>B Transition in region 2V - 3V (any gradient including step)</p> 	<p>1</p> <p>1</p> <p>1</p>	
	(ii)	<p>E When input is low output needs to be high</p> <p>A The voltages from the paper sensor are above and below the thresholds of the gate (wtte)</p>	<p>1</p> <p>1</p>	function of NOT gate behaviour thresholds

Question			Answer	Marks	Guidance
2	(a)	E	Ring around thermistor	1	
	(b)	E E	Resistance depends on temperature Resistance decreases as temperature increases	1 1	Or any statement that implies this or resistance increases as temperature decreases
	(c)	D C C	total resistance: $33k+39k=72k$ current: $15/72000=2.08 \times 10^{-4}$ A voltage: $IR = 39 \times 10^3 \times 2.08 \times 10^{-4}$ so $V=8.1(25)$ V (at least 2 s.f. needed)	1 1 1	evidence of adding two resistor ($33k + 39k$) ecf multiply current by 39k
	(d)	E A A A	conversion from $k\Omega$ to Ω : $R = 2100\Omega$ V across thermistor: $15 - 6 = 9V$ Calculation of current: $I = 9/2100 = 0.00429A$ $R = 6/0.00429 = 1400\Omega$ (ecf)	1 1 1 1	Any other valid method for [4] Conversion can come anywhere in the calculation. No ecf ecf for current
	(e)	D C B	LED is off Plus up to 2 of: <ul style="list-style-type: none"> • Because (voltage at) inverting input > non-inverting input • so output of op amp saturated negative (-13 V) / goes negative • so LED reverse biased 	1 1 1	comparing voltages at inputs or reference to saturation/comparator action for [1]
	(f)	C D A	LDR in voltage divider in circuit Fixed reference voltage circuit which turns on LED when dark	1 1 1	


Question				Answer	Marks	Guidance
3	(a)		E	$L = \overline{G}$	1	
			C		1	
			D	$N = H + \overline{G}$ ecf	1	
			B	$M = J \cdot K$	1	
				$P = J \cdot K + \overline{H + G}$ ecf		
	(b)		E	switch between H and 5V	1	
D			switch and resistor in series with power supply	1		

Question	Answer	Marks	Guidance												
<p>4</p>	<table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 50%; text-align: left;">Column 1</th> <th style="width: 50%; text-align: left;">Column 2</th> </tr> </thead> <tbody> <tr> <td>$X \cdot \bar{Y} + X \cdot Z$</td> <td>$\overline{\overline{X + \bar{Y}}} + X \cdot Z$</td> </tr> <tr> <td>$\bar{X} \cdot Y + X \cdot Z$</td> <td>$\bar{X} \cdot (Y + Z)$</td> </tr> <tr> <td>$\bar{X} \cdot Y + \bar{X} \cdot Z$</td> <td>$\bar{X} \cdot Y + X \cdot Z + Y \cdot Z$</td> </tr> <tr> <td>$X \cdot Y + X \cdot Z$</td> <td>$\overline{\overline{X \cdot \bar{Y}}} + X \cdot Z$</td> </tr> <tr> <td>$(X + Y) \cdot (\bar{X} + Z)$</td> <td>$X \cdot Y + X \cdot Z + \bar{Y} \cdot Y$</td> </tr> </tbody> </table>	Column 1	Column 2	$X \cdot \bar{Y} + X \cdot Z$	$\overline{\overline{X + \bar{Y}}} + X \cdot Z$	$\bar{X} \cdot Y + X \cdot Z$	$\bar{X} \cdot (Y + Z)$	$\bar{X} \cdot Y + \bar{X} \cdot Z$	$\bar{X} \cdot Y + X \cdot Z + Y \cdot Z$	$X \cdot Y + X \cdot Z$	$\overline{\overline{X \cdot \bar{Y}}} + X \cdot Z$	$(X + Y) \cdot (\bar{X} + Z)$	$X \cdot Y + X \cdot Z + \bar{Y} \cdot Y$	<p>3</p>	<p>E One correct [1] C Two correct [2] A All correct [3]</p> <p>4 1 (2) 5 3</p>
Column 1	Column 2														
$X \cdot \bar{Y} + X \cdot Z$	$\overline{\overline{X + \bar{Y}}} + X \cdot Z$														
$\bar{X} \cdot Y + X \cdot Z$	$\bar{X} \cdot (Y + Z)$														
$\bar{X} \cdot Y + \bar{X} \cdot Z$	$\bar{X} \cdot Y + X \cdot Z + Y \cdot Z$														
$X \cdot Y + X \cdot Z$	$\overline{\overline{X \cdot \bar{Y}}} + X \cdot Z$														
$(X + Y) \cdot (\bar{X} + Z)$	$X \cdot Y + X \cdot Z + \bar{Y} \cdot Y$														

Question		Answer	Marks	Guidance			
5	(a)	C	Correct MOSFET symbol	1			
		E	MOSFET in series with speaker across power supply	1			
		E	MOSFET gate to output of oscillator	1			
		C	speaker to connected to drain, source to 0V	1			
	(b)	E	680pF and 820kΩ values in equation	1			
		E	correct conversion from kΩ	1			
		D	correct conversion from pF	1			
		D	calculation of $T = 278 \times 10^{-6} \text{s}$	1			
	(c)	E	Conversion from μs to s (or MHz to Hz): 278μs or	1			
		E	300μs Correct calculation using $1/T: f = 3597 \pm 50 \text{ Hz}$ ($f = 3571 \text{ Hz}$ or $3333 \pm 50 \text{ Hz}$) (ecf)	1			
	(d)	(i)	E	1V/div	1		
			(ii)	E	50μs		1
				(iii)	E		Recognisable oscilloscope symbol connected across capacitor
	(iv)	B	<ul style="list-style-type: none"> (curved) triangular wave in phase with square wave 	1	Not a square wave or a sine wave		
		A	<ul style="list-style-type: none"> wave in step with square wave of amplitude less than 5 V 	1			
		A	<ul style="list-style-type: none"> rising when square wave high 	1			
	(e)		Up to 3 of: <ul style="list-style-type: none"> output of NOT gate high; diode reverse biased; capacitor can charge and discharge; MOSFET turns on and off operating speaker; 	3	Allow reverse argument for when switch pressed		

Question			Answer	Marks	Guidance	
6	(a)	E	R at least 10k Ω	1		
		E	Use of 30s = 0.7 RC	1		
		C	Calculation of C to make RC = 42.8 s to 43 s	1		
	(b)	E	LED turns on	1		
		E	for 30s (but does not comes on again without pressing switch)	1		
	(c)	(i)	E	correct voltmeter symbol	1	
			E	connected across switch	1	
		(ii)	D	0V	1	
	(d)	A	$5 - 1.2 = 3.8V$;	1		
		A	$I = \frac{3.8}{220} = 0.017A$ (ecf from V);	1	must use 220 Ω or V^2/R	
		B	$P = 3.8 \times 0.017 = 0.066W$;	1		
	(e)	(i)	D	B	1	
		(ii)	E	Correct resistance	1	Allow if ei answer is D
		E	maximum power above power needed (wtte)	1		

Question		Answer	Marks	Guidance
7	(a)	D D D	1 1 1	Any correct expression for 3 marks, e.g. $R = C \cdot \bar{E} + D \cdot \bar{E}$ $R = (C + D) \cdot \bar{E}$ $R = \overline{\overline{(C + D)}} + E$ If correct 3 terms not ORed together [1]
	(b)	E E C B	1 1 1 1	or any other working circuit No ecf from a

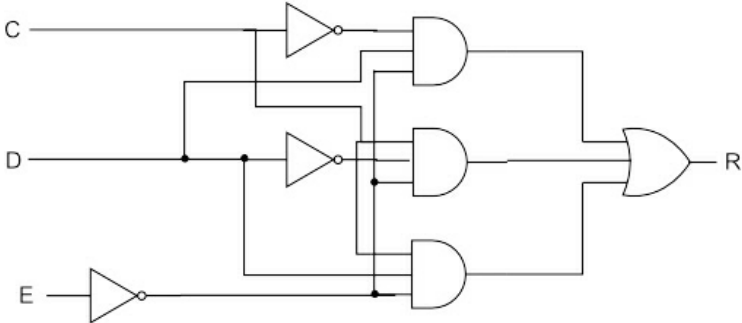

Question			Answer	Marks	Guidance															
8	(a)		E EOR or XOR or EXOR or exclusive OR	1																
	(b)		E C All combinations of A & B (any order) Correct Q <table border="1" style="margin-left: 40px;"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	Q	0	0	0	0	1	1	1	0	1	1	1	0	1 1	No ecf
A	B	Q																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	0																		
	(c)	(i)	B LED on	1																
		(ii)	A A A When switch 1 is open A is low When switch 2 is open B is high (When A is high and B is low) Q is high making LED glow/LED is forward biased/current flows through LED	1 1 1																

APPENDIX 1

- 3 The candidate expresses complex ideas extremely clearly and fluently. Sentences and paragraphs follow on from one another smoothly and logically. Arguments are consistently relevant and well structured. There will be few, if any, errors of grammar, punctuation and spelling.
- 2 The candidate expresses straightforward ideas clearly, if not always fluently. Sentences and paragraphs may not always be well connected. Arguments may sometimes stray from the point or be weakly presented. There may be some errors of grammar, punctuation and spelling, but not such as to suggest a weakness in these areas.
- 1 The candidate expresses simple ideas clearly, but may be imprecise and awkward in dealing with complex or subtle concepts. Arguments may be of doubtful relevance or obscurely presented. Errors in grammar, punctuation and spelling may be noticeable and intrusive, suggesting weaknesses in these areas.
- 0 The language has no rewardable features.

OCR (Oxford Cambridge and RSA Examinations)
1 Hills Road
Cambridge
CB1 2EU

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; 1 Hills Road, Cambridge, CB1 2EU
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2012

