

**Electronics**

Advanced Subsidiary GCE

Unit **F612**: Signal Processors

**Mark Scheme for June 2012**

---

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, OCR Nationals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.

OCR will not enter into any discussion or correspondence in connection with this mark scheme.

© OCR 2012

Any enquiries about publications should be addressed to:


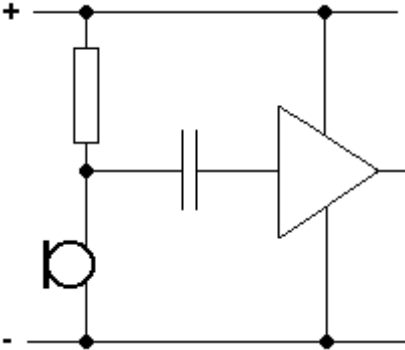
OCR Publications  
PO Box 5050  
Annesley  
NOTTINGHAM  
NG15 0DL



Telephone: 0870 770 6622  
Facsimile: 01223 552610  
E-mail: [publications@ocr.org.uk](mailto:publications@ocr.org.uk)


Question		Answer	Marks	Guidance
1	(a)		3	straight line through origin [1] gradient of +1 [1] saturating at +13 V and -13 V ( $\pm 1$ V by eye) [1]
	(b)	power amplifier	1	
	(c) (i)	any two of the following [1] each: <ul style="list-style-type: none"> <li><math>V_+</math> = voltage at X, <math>V_-</math> = voltage at Y; <math>V_{out}</math> = voltage at Z,</li> <li><math>A</math> is op-amp gain without any feedback;</li> <li>voltage at output divided by difference at inputs;</li> <li>when op-amp not saturated;</li> </ul>	2	<b>accept</b> signal for voltage <b>reject</b> current / charge / power for voltage  <b>accept</b> $A = \frac{V_{out}}{V_+ - V_-}$ instead of words
	(ii)	6.0 V	1	accept 5.95 V
	(iii)	$I = V/R$ (eor); $= 6/16 = 0.375$ A;	1 1	<b>accept</b> reverse calculation with $V = IR$ (not $R = V/I$ ) for [2] no ecf from incorrect $V$ :
	(iv)	$P = VI = 2.25$ W	1	allow ecf from incorrect $V, I$ 400 mA gives 2.4 W for [1]

Question	Answer	Marks	Guidance									
2 (a)	<pre> graph TD     Start([start]) --&gt; Input[/let S7 = input/]     Input --&gt; Decision{S7 = 20}     Decision -- yes --&gt; B((b))     Decision -- no --&gt; A((a))     A --&gt; Input     </pre>	4	<p>correct input box for [1]                      correct decision box for [2]                      incorrect decision box with S7 for [1]                      correct connection labels for [1]</p> <p>look for correct syntax</p> <p><b>accept</b> 20<sub>16</sub> or 20<sub>H</sub></p>									
2 (b)	<table border="1"> <tbody> <tr> <td data-bbox="360 805 611 837">S6</td> <td data-bbox="611 805 857 837">0110 000</td> <td data-bbox="857 805 1117 837">1</td> </tr> <tr> <td data-bbox="360 837 611 869">S5</td> <td data-bbox="611 837 857 869">1111 0010</td> <td data-bbox="857 837 1117 869">3</td> </tr> <tr> <td data-bbox="360 869 611 901">S4</td> <td data-bbox="611 869 857 901">1101 1010</td> <td data-bbox="857 869 1117 901">2</td> </tr> </tbody> </table>	S6	0110 000	1	S5	1111 0010	3	S4	1101 1010	2	3	<p>each correct binary word for [1] each                      all three display numbers match binary for [1]</p>
S6	0110 000	1										
S5	1111 0010	3										
S4	1101 1010	2										

Question	Answer	Marks	Guidance
<p>2 (c)</p>	<pre> graph TD     c((c)) --&gt; S0_in[/let S0 = input/]     S0_in --&gt; S0_eq04{S0 = 04}     S0_eq04 -- yes --&gt; d((d))     S0_eq04 -- no --&gt; e((e))     d --&gt; S0_00[let S0 = 00]     S0_00 --&gt; S0_out[/let output = S0/]     S0_out --&gt; a((a))     e --&gt; S5[/let output = S5/]     S5 --&gt; P500_1[pause 500]     P500_1 --&gt; S4[/let output = S4/]     S4 --&gt; P500_2[pause 500]     P500_2 --&gt; S6[/let output = S6/]     S6 --&gt; P500_3[pause 500]     P500_3 --&gt; c2((c))     </pre>	<p>2</p> <p>2</p> <p>2</p>	<p>from c, copy input port to a register (not S4, S5, S6) for [1] test to see if register contains 04, pass to <b>d</b> if yes, pass to <b>e</b> if no for [1]</p> <p><b>reject</b> decision box with ?</p> <p><b>reject</b> 4 instead of 04</p> <p>load any register (not S4, S5 or S6) with 00 for [1] copy that register to output and return to a for [1]</p> <p><b>accept</b> let output = 00 and return to a for [1]</p> <p>output contents of S5, S4 and S6 in order, pass to c for [1] <b>ecf</b>: incorrect sequence of numbers (3,2,1) from 2(b) with 500 ms delay after each output for [1]</p> <p><b>ecf</b>: penalise incorrect box shape only once <b>ecf</b>: penalise missing arrows only once</p>


Question	Answer	Marks	Guidance
3 (a)		4	microphone first, loudspeaker last for [1] power amplifier just before loudspeaker for [1] volume control anywhere before power amplifier for [1] tone control anywhere before voltage amplifier for [1]
3 (b) (i)		3	correct symbols for all three components, as shown [1] resistor and microphone in series with supply rails [1] capacitor between microphone-resistor to amplifier input [1]
	(ii) 10 kΩ or above; to allow most of the signal from the microphone to reach the amplifier owtte;	1  1	<b>accept</b> input impedance should always be larger than output impedance / reduce lost volts in microphone / reduce current in microphone / reduce loss of signal from microphone  <b>reject</b> to match impedances

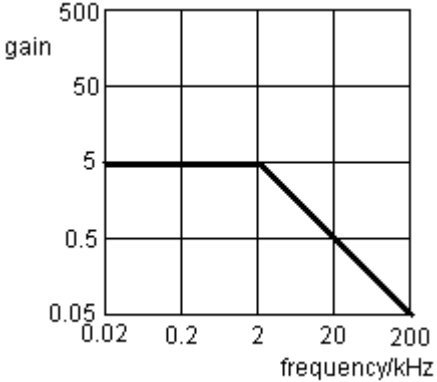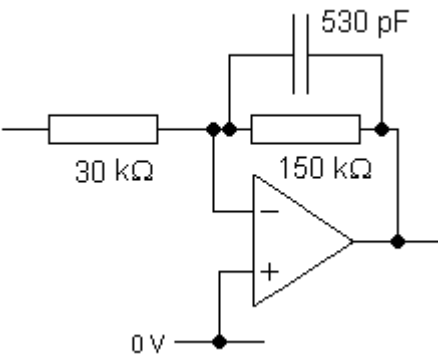Question	Answer	Marks	Guidance
(c) (i)		3	correct shape (horizontal then dropping), any values [1] horizontal 5 from 0.02 to 2 kHz [1] dropping at 45° above 2 kHz [1]
(ii)		5	correct resistor placement [1] correct capacitor placement [1] correct resistor values [1] correct capacitor value with ecf ( $RC = 80 \mu\text{s}$ ) [1] use of $f_0 = \frac{1}{2\pi RC}$ to justify a capacitor value [1]  no ecf from incorrect (c)(i)


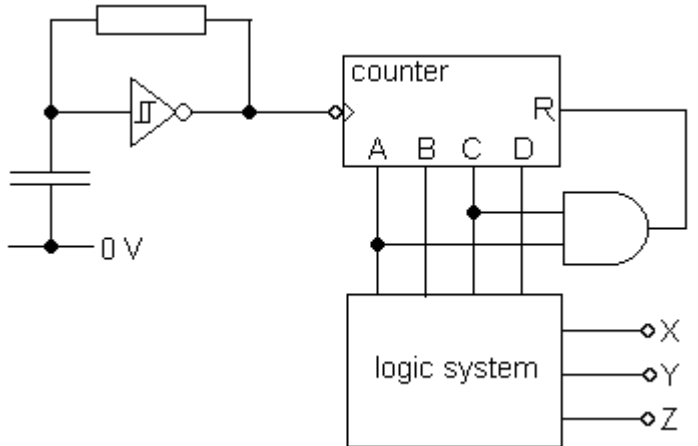
Question	Answer	Marks	Guidance																																										
4 (a)		2	AND gate output connected to R [1] gate inputs to C and A [1]																																										
(b)	<p>R at least 1 kΩ; RC = 8.0 s to give value of C;</p>	1 1																																											
(c) (i)	<table border="1" data-bbox="358 853 1041 1244"> <thead> <tr> <th>state</th> <th>C</th> <th>B</th> <th>A</th> <th>X</th> <th>Y</th> <th>Z</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>2</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>3</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>4</td> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> </tr> </tbody> </table>	state	C	B	A	X	Y	Z	0	0	0	0	1	0	0	1	0	0	1	1	1	0	2	0	1	0	0	1	0	3	0	1	1	0	1	1	4	1	0	0	0	0	1	2	correct pattern for [2] A and C swapped round for [1]
state	C	B	A	X	Y	Z																																							
0	0	0	0	1	0	0																																							
1	0	0	1	1	1	0																																							
2	0	1	0	0	1	0																																							
3	0	1	1	0	1	1																																							
4	1	0	0	0	0	1																																							
(ii)	$Z = \bar{C}.B.A + C.\bar{B}.\bar{A}$	2	each correct term for [1] <b>accept</b> ecf from if 4ci worth [1] e.g. $Z = \bar{A}.B.C + A.\bar{B}.\bar{C}$ <b>accept</b> simplified $Z = C + B.A$																																										



Question	Answer	Marks	Guidance
(iii)		3	<p>use of NOT gates to invert each input [1]                      correct AND gates to generate both terms [1]                      correct OR gate to generate final expression [1]</p> <p>accept three input AND gates</p> <p>accept ecf <b>either</b> from <math>Z = \bar{A}.B.C + A.\bar{B}.\bar{C}</math> <b>or</b> <math>Z = C + B.A</math> for full marks</p> <p>accept correct simplified circuit for [3]</p>

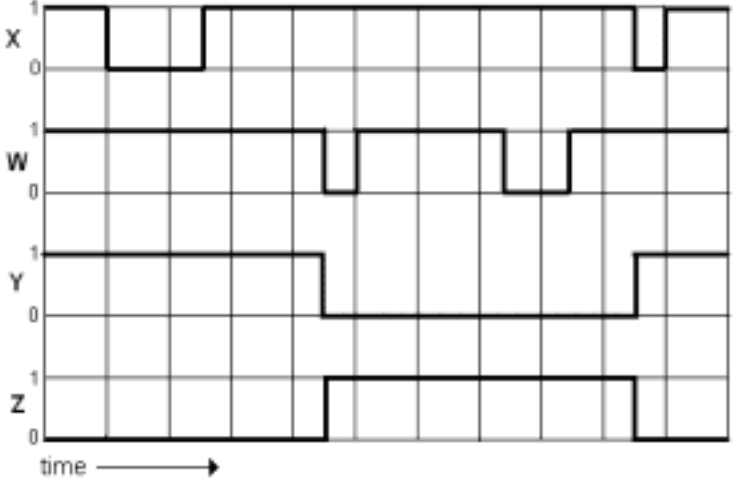Question		Answer	Marks	Guidance
5	(a)	output low when both inputs high; otherwise output high;	1 1	<b>accept</b> output <i>only</i> low when both inputs high for [2] <b>accept</b> 1 or 5V for high, 0 or 0V for low <b>reject</b> on/off, input/no input, positive/negative ...
	(b) (i)	active-low: inputs need to go low to change output; set: make output high; reset: make output low;	1 1 1	<b>not just</b> normally held high, activates circuit <b>accept</b> Z for output throughout <b>accept</b> set and reset round wrong way for [1]
	(ii)	gate 1 has one input (X) low so Y must be high; gate 2 has two inputs (W, Y) high so Z must be low;	1 1	<b>not just</b> Y is high <b>not just</b> Z is low
	(iii)	 <p>The timing diagram shows four signals over time. The vertical axis for each signal is labeled 1 (high) and 0 (low). The horizontal axis is labeled 'time' with an arrow pointing right. Signal X starts high, then pulses low for a short duration, then returns to high. Signal W starts high, then pulses low for a short duration, then returns to high. Signal Y starts high, then drops to low for a longer duration, then returns to high. Signal Z starts low, then pulses high for a short duration, then returns to low.</p>	3	Y and Z have opposite states throughout [1] Z goes high and stays high when W pulsed low [1] Z goes low and stays low when X pulsed low [1]

Question			Answer	Marks	Guidance
6	(a)	(i)		4	S and R to 0 V rail [1] $\bar{Q}$ to D and Q goes to output [1] NOT gate to clock [1] correct input and output [1]
		(ii)	$2^{10} / 1024 \text{ Hz}$	1	
		(iii)	frequency less likely to change as time goes on / easier to get the correct frequency (than setting $RC$ value)	1	<b>not just</b> more precise / accurate / reliable
	(b)		four; one nought; ten; seven;	1 1 1 1	in any order
	(c)		(F) E AD BC	3	first box E for [1] D immediately after A anywhere for [1] then C immediately after B for [1]  remember AD before BC?

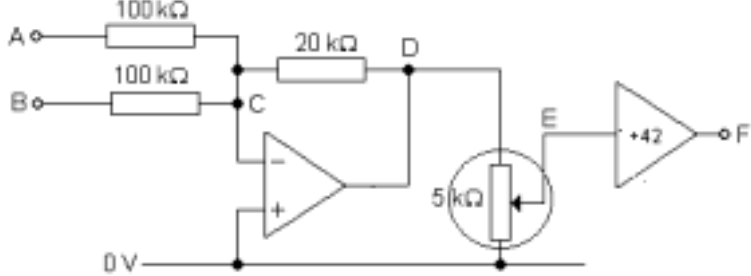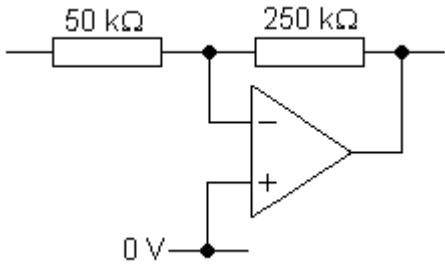Question	Answer	Marks	Guidance
7 (a)		1	
(b)	<p>correct substitution into summing amp formula</p> <p>e.g. <math>-\frac{V_{out}}{20k} = \frac{5.2}{100k} + \frac{-1.3}{100k}</math>;                      - 0.78 V;</p>	1 2	<p><b>accept</b> 20, 100 and 100 in substitution</p> <p>accept 0.78 V for [2]                      accept -0.8 V for [3]</p>
(c)		3	<p>all resistors between 1 kΩ and 10 MΩ [1]                      resistors to give gain of magnitude 5 [1]                      correct inverting amplifier circuit [1]</p>

Question		Answer	Marks	Guidance
8	(a)		4	each correct link for [1]
	(b) (i)	one chip makes many different systems / only one chip for a complete system / (smaller pcb) because one chip replaces many in a system	1	<b>not just</b> programmable / reprogrammable owtte
	(ii)	any one of: <ul style="list-style-type: none"> <li>• system is faster;</li> <li>• don't need programming skills;</li> <li>• easier to understand;</li> <li>• less complicated to design;</li> </ul>	1	<b>not</b> cheaper

## APPENDIX 1

## Quality of Written Communication

3	<p>The candidate expresses complex ideas extremely clearly and fluently. Sentences and paragraphs follow on from one another smoothly and logically. Arguments are consistently relevant and well structured. There will be few, if any, errors of grammar, punctuation and spelling.</p>
2	<p>The candidate expresses straightforward ideas clearly, if not always fluently. Sentences and paragraphs may not always be well connected. Arguments may sometimes stray from the point or be weakly presented. There may be some errors of grammar, punctuation and spelling, but not such as to suggest a weakness in these areas.</p>
1	<p>The candidate expresses simple ideas clearly, but may be imprecise and awkward in dealing with complex or subtle concepts. Arguments may be of doubtful relevance or obscurely presented. Errors in grammar, punctuation and spelling may be noticeable and intrusive, suggesting weaknesses in these areas.</p>
0	<p>The language has no rewardable features.</p>

**OCR (Oxford Cambridge and RSA Examinations)**  
1 Hills Road  
Cambridge  
CB1 2EU

**OCR Customer Contact Centre**

**Education and Learning**

Telephone: 01223 553998

Facsimile: 01223 552627

Email: [general.qualifications@ocr.org.uk](mailto:general.qualifications@ocr.org.uk)

**[www.ocr.org.uk](http://www.ocr.org.uk)**

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations  
is a Company Limited by Guarantee  
Registered in England  
Registered Office; 1 Hills Road, Cambridge, CB1 2EU  
Registered Company Number: 3484466  
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)  
Head office  
Telephone: 01223 552552  
Facsimile: 01223 552553

© OCR 2012

