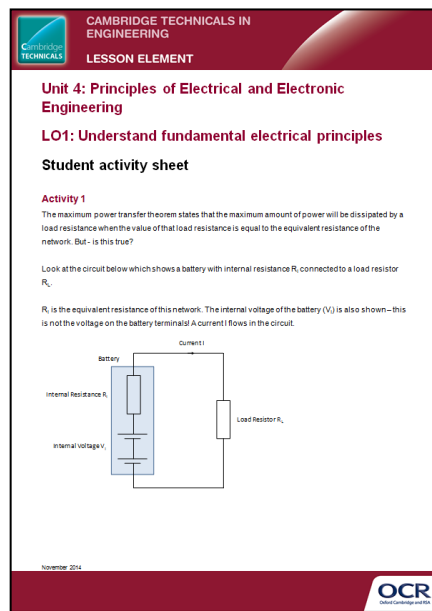


## Unit 4: Principles of Electrical and Electronic Engineering

### LO1: Understand fundamental electrical principles – Maximum power transfer

#### *Instructions and answers for teachers*

*These instructions should accompany the OCR resource 'Understanding fundamental electrical principles – Maximum power transfer' activity which supports Cambridge Technicals in Engineering Level 3.*



The screenshot shows a document header with the Cambridge Technicals logo and the text 'CAMBRIDGE TECHNICALS IN ENGINEERING LESSON ELEMENT'. The main content includes the unit title 'Unit 4: Principles of Electrical and Electronic Engineering', the learning objective 'LO1: Understand fundamental electrical principles', and the title 'Student activity sheet'. Under 'Activity 1', it states: 'The maximum power transfer theorem states that the maximum amount of power will be dissipated by a load resistance when the value of that load resistance is equal to the equivalent resistance of the network. But - is this true?'. It then asks the student to look at a circuit diagram showing a battery with internal resistance  $R_i$  connected to a load resistor  $R_L$ . The diagram labels the battery, internal resistance  $R_i$ , internal voltage  $V_i$ , current  $I$ , and load resistor  $R_L$ . The OCR logo is visible in the bottom right corner of the document.

#### **The Activity:**

In this task the students are tasked with finding the internal resistance of a battery including plotting a graph to show load power for varying values of resistance.



*This activity offers an opportunity for English skills development.*



*This activity offers an opportunity for maths skills development.*


#### **Suggested timings:**

2 hours
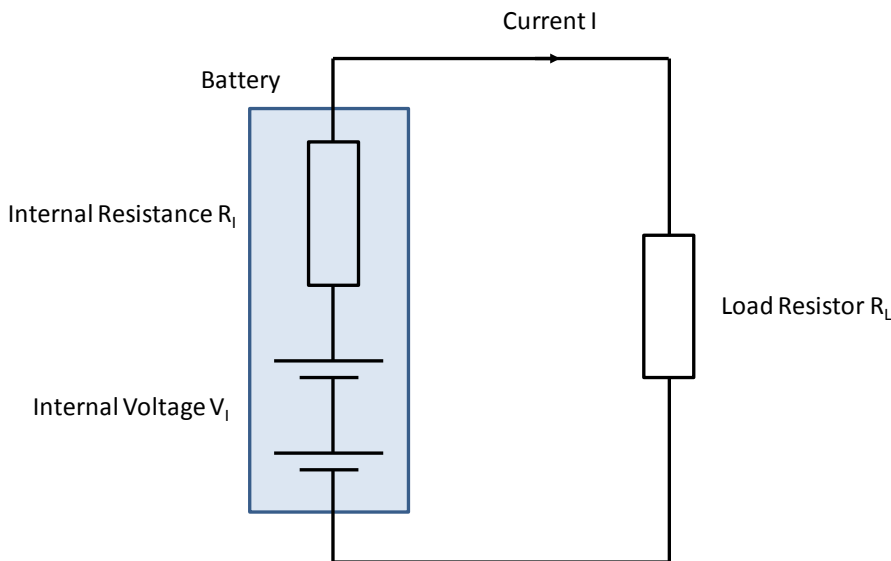
### Activity 1

The maximum power transfer theorem states that the maximum amount of power will be dissipated by a load resistance when the value of that load resistance is equal to the equivalent resistance of the network.

Learners have been presented with a circuit showing a battery with internal resistance  $R_i$  connected to a load resistor  $R_L$ . The circuit is shown below:



The internal resistance of the battery is  $200\Omega$  and the internal battery voltage is  $9v$ .

1. Maximum power will be transferred to the load when its value is equivalent to the internal resistance of the battery according to the Power Law. For maximum power transfer  $R_L$  should be  $200\Omega$ .
2. Learners have been tasked to plot a graph showing load power for varying values of load resistance from  $50\Omega$  to  $400\Omega$  (in steps of  $10\Omega$ ).

Load Resistor Value $R_L$	Circuit Current I	Load Power P
$50\Omega$	0.036A	0.0648W
$60\Omega$	0.034615A	0.0719W
$70\Omega$		
$80\Omega$		


In order to calculate circuit current, learners will need to apply Ohms law using internal battery voltage and total circuit resistance ie:

$$I = \frac{\text{Internal battery voltage } V_I}{\text{Internal Resistance } R_I + \text{Load Resistance } R_L} \text{ (Amps)}$$

Power in the load resistance is calculated using the circuit current and value of load resistance ie:

$$P_{LOAD} = I^2 R_L \text{ (Watts)}$$

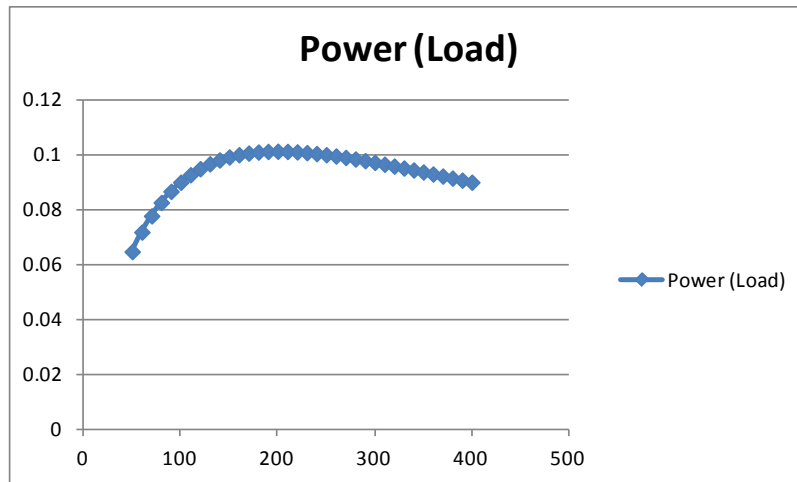
Learners might be able to use a spreadsheet (available with this Lesson Element) to plot a graph of load power (vertically) against load resistance (horizontally). The resulting graph is shown below:



The graph demonstrates that maximum power is transferred to the load resistor when it has the same value as the internal resistance of the battery. In this example maximum power transfer occurs when the value of the load resistor is 200Ω.
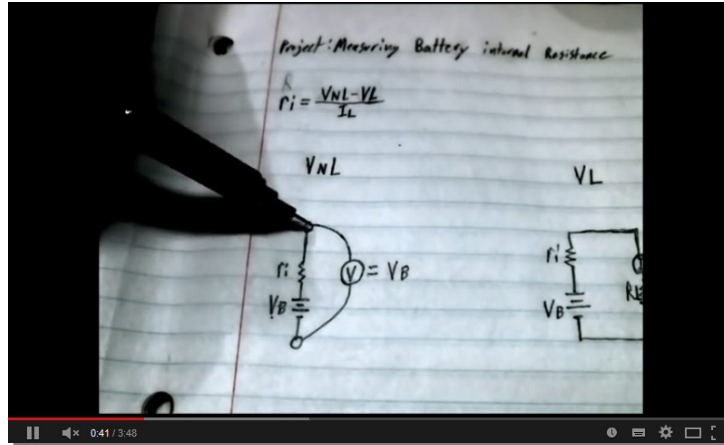
### Activity 2

In the second activity learners are tasked to watch a video showing how to measure the internal resistance of a battery.



<http://youtu.be/HZUDFcOSe48>

Learners could undertake this activity as a practical experiment if access to suitable resources is available.

Equipment to undertake the experiment:

- 9V PP9 battery.
- Load Resistor (in the range  $500\Omega$  to  $1000\Omega$ ,  $\frac{1}{4}$  watt).
- Multimeter (with volts and amps ranges).

Learners could determine the internal resistance of the battery and write this as an experimental report (to include list of equipment used, method, results and conclusions). Learners should apply Ohms law (as shown in the video) to determine internal resistance.

Learners should conclude that connecting a resistor to the battery, with a value equivalent to the internal resistance of the battery, will result in maximum power being transferred.

The experiment could be extended, by investigating the effects of varying the load resistance on the battery, and a graph of load resistance vs load power being plotted from measured values. This is similar to Activity 1, except that learners are undertaking an experiment to determine maximum power transfer practically.



We'd like to know your view on the resources we produce. By clicking on the 'Like' or 'Dislike' button you can help us to ensure that our resources work for you. When the email template pops up please add additional comments if you wish and then just click 'Send'. Thank you.

**OCR Resources: *the small print***

OCR's resources are provided to support the teaching of OCR specifications, but in no way constitute an endorsed teaching method that is required by the Board, and the decision to use them lies with the individual teacher. Whilst every effort is made to ensure the accuracy of the content, OCR cannot be held responsible for any errors or omissions within these resources. We update our resources on a regular basis, so please check the OCR website to ensure you have the most up to date version.

© OCR 2014 - This resource may be freely copied and distributed, as long as the OCR logo and this message remain intact and OCR is acknowledged as the originator of this work.

OCR acknowledges the use of the following content: Maths and English icons: Air0ne/Shutterstock.com