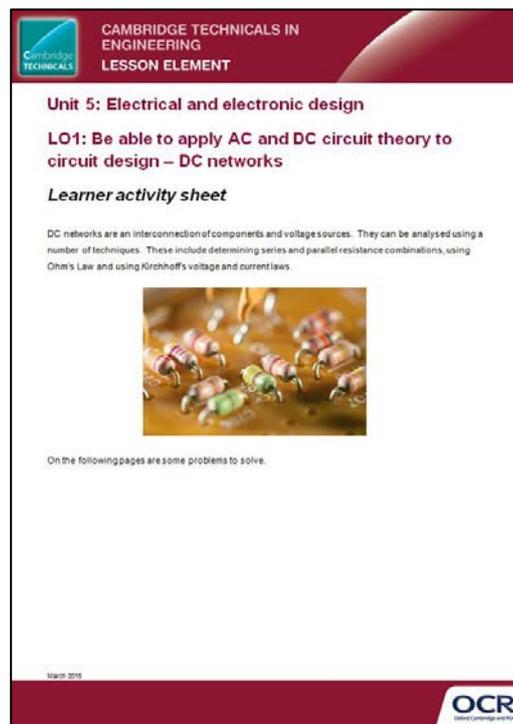


Unit 5: Electrical and electronic design

LO1: Be able to apply AC and DC circuit theory to circuit design – DC networks

Instructions and answers for teachers

These instructions should accompany the OCR resource 'Be able to apply AC and DC theory to circuit design – DC networks' activity which supports Cambridge Technicals in Engineering Level 3.



The Activity:

In this task the students are tasked with familiarising themselves with DC networks.



This activity offers an opportunity for English skills development.




This activity offers an opportunity for maths skills development.

Suggested timings:

1 hour

Activity 1

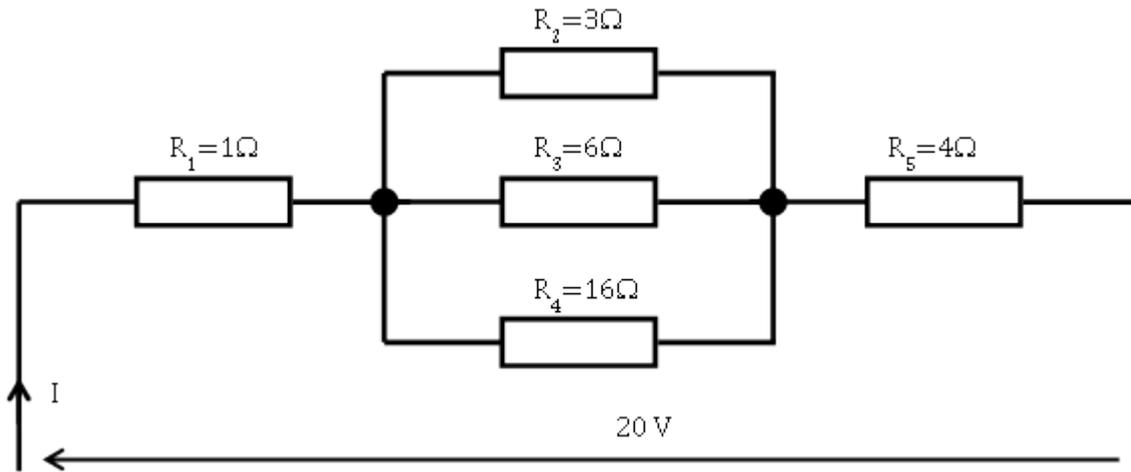

Activity 1 involves a circuit with series and parallel resistances, and an applied voltage. The problems can be solved by calculating overall circuit resistance and using Ohm's Law to calculate current. Learners will require some knowledge of series and parallel resistor combinations and Ohm's Law before attempting the problem.

1. Total circuit resistance involves calculating both series and parallel resistance.

Calculating resistance of parallel combination R_2 , R_3 and R_4

$$1/R_T = 1/R_2 + 1/R_3 + 1/R_4 = 1/3 + 1/6 + 1/16 = 0.5625 \Omega$$

$$\text{Therefore } R_T = 1/0.5625 = 1.78 \Omega$$

$$\text{Total circuit resistance} = R_1 + 1.78 \Omega + R_5 = 1 \Omega + 1.78 \Omega + 4 \Omega = \mathbf{6.78 \Omega}$$


2. Current (I) can be calculated using Ohm's Law:

$$V = I/R \text{ and } I = V/R \text{ (transposing formula)}$$

$$I = 20 \text{ V} / 6.78 \Omega = \mathbf{2.95 \text{ A}}$$

Learners could solve similar problems involving series and parallel resistors, and an applied voltage.

Activity 2

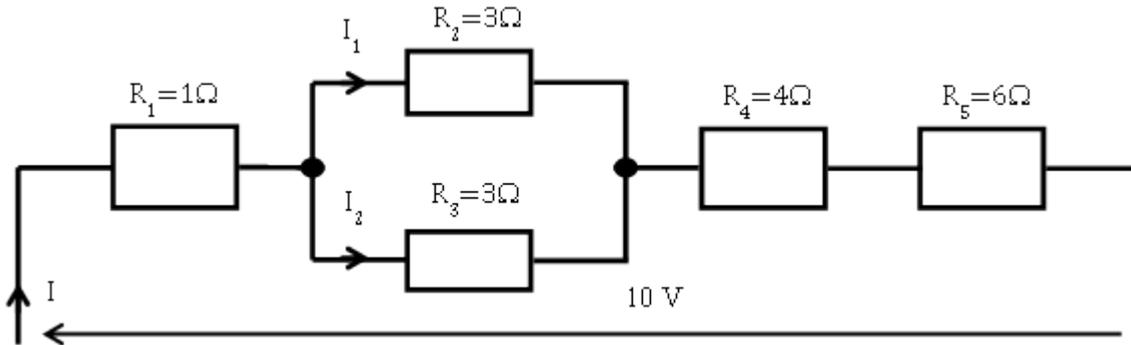

Activity 2 is similar to Activity 1, but demonstrates the application of Kirchhoff's Laws. Learners will require knowledge of Kirchhoff's Laws before attempting the problem.

1. Total resistance is calculated in a similar way to Activity 1.

To determine the total resistance of two resistors in parallel the following can be applied (rather than taking reciprocals):

$$R_T = (R_2 \times R_3) / (R_2 + R_3) = (3 \times 3) / (3 + 3) = 1.5 \Omega$$

[Note: when two identical resistors are connected in parallel, then the overall resistance is always half the value of one of the resistors – this is a special case]

$$\text{Total circuit resistance} = 1 \Omega + 1.5 \Omega + 4 \Omega + 6 \Omega = 12.5 \Omega$$

2. Total circuit current is calculated using Ohm's Law:

$$V = I/R \text{ and } I = V/R \text{ (transposing formula)}$$

$$I = 10 \text{ V} / 12.5 \Omega = 0.8 \text{ A}$$

3. Currents I_1 and I_2 can be determined using Kirchhoff's current law.

At the first node in the circuit the current divides equally (as R_2 and R_3 have identical value)

$$\text{Current } I_1 = I_2 = 0.8/2 = \mathbf{0.4 \text{ A}}$$

The current divides in the ratio of R_2 and R_3 .

Alternatively, the current division rule can be used for parallel resistors:

In the circuit – the voltage across the parallel pair of resistors is 1.2 V

So – the sum of the PDs in the closed circuit loop is:

$$0.8 \text{ V} + 1.2 \text{ V} + 3.2 \text{ V} + 4.8 \text{ V} = 10 \text{ V}$$

This is equal to the applied voltage of 10 V – thereby satisfying Kirchhoff's voltage law

Learners could solve similar problems to Activity 2, using series and parallel resistors, Ohm's Law and Kirchhoff's Laws.



We'd like to know your view on the resources we produce. By clicking on the 'Like' or 'Dislike' button you can help us to ensure that our resources work for you. When the email template pops up please add additional comments if you wish and then just click 'Send'. Thank you.

OCR Resources: *the small print*

OCR's resources are provided to support the teaching of OCR specifications, but in no way constitute an endorsed teaching method that is required by the Board, and the decision to use them lies with the individual teacher. Whilst every effort is made to ensure the accuracy of the content, OCR cannot be held responsible for any errors or omissions within these resources. We update our resources on a regular basis, so please check the OCR website to ensure you have the most up to date version.

© OCR 2015 - This resource may be freely copied and distributed, as long as the OCR logo and this message remain intact and OCR is acknowledged as the originator of this work.

OCR acknowledges the use of the following content: Maths and English icons: AirOne/Shutterstock.com

Please get in touch if you want to discuss the accessibility of resources we offer to support delivery of our qualifications: resources.feedback@ocr.org.uk