



Wednesday 11 June 2014 – Morning

A2 GCE ELECTRONICS

F615/01 Communication Systems

Candidates answer on the Question Paper.

OCR supplied materials:
None

Other materials required:
• Scientific calculator

Duration: 1 hour 40 minutes



Candidate forename		Candidate surname	
-----------------------	--	----------------------	--


Centre number						Candidate number				
---------------	--	--	--	--	--	------------------	--	--	--	--

INSTRUCTIONS TO CANDIDATES

- Write your name, centre number and candidate number in the boxes above. Please write clearly and in capital letters.
- Use black ink. HB pencil may be used for graphs and diagrams only.
- Answer **all** the questions.
- Read each question carefully. Make sure you know what you have to do before starting your answer.
- Write your answer to each question in the space provided. Additional paper may be used if necessary but you must clearly show your candidate number, centre number and question number(s).
- Do **not** write in the bar codes.

INFORMATION FOR CANDIDATES

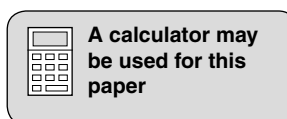- The number of marks is given in brackets [] at the end of each question or part question.
- The total number of marks for this paper is **110**.
- You will be awarded marks for your Quality of Written Communication.
- You are advised to show all the steps in any calculations.
- This document consists of **20** pages. Any blank pages are indicated.



Data Sheet

Unless otherwise indicated, you can assume that:

- op-amps are run off supply rails at +15V and –15V
- logic circuits are run off supply rails at +5V and 0V.

resistance	$R = \frac{V}{I}$
power	$P = VI$
series resistors	$R = R_1 + R_2$
time constant	$\tau = RC$
monostable pulse time	$T = 0.7 RC$
relaxation oscillator period	$T = 0.5 RC$
frequency	$f = \frac{1}{T}$
voltage gain	$G = \frac{V_{\text{out}}}{V_{\text{in}}}$
open-loop op-amp	$V_{\text{out}} = A(V_+ - V_-)$
non-inverting amplifier gain	$G = 1 + \frac{R_f}{R_d}$
inverting amplifier gain	$G = -\frac{R_f}{R_{\text{in}}}$
summing amplifier	$-\frac{V_{\text{out}}}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} \dots$
break frequency	$f_0 = \frac{1}{2\pi RC}$

Boolean Algebra

$$A.\bar{A} = 0$$

$$A + \bar{A} = 1$$

$$A.(B + C) = A.B + A.C$$

$$\overline{A.B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A}.\bar{B}$$

$$A + A.B = A$$

$$A.B + \bar{A}.C = A.B + \bar{A}.C + B.C$$

amplifier gain

$$G = -g_m R_d$$

ramp generator

$$\Delta V_{out} = -V_{in} \frac{\Delta t}{RC}$$

inductor reactance

$$X_L = 2\pi fL$$

capacitor reactance

$$X_C = \frac{1}{2\pi fC}$$

resonant frequency

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Answer **all** questions.

- 1 Fig. 1.1 shows the five connections which carry digital information from a computer to a colour monitor.

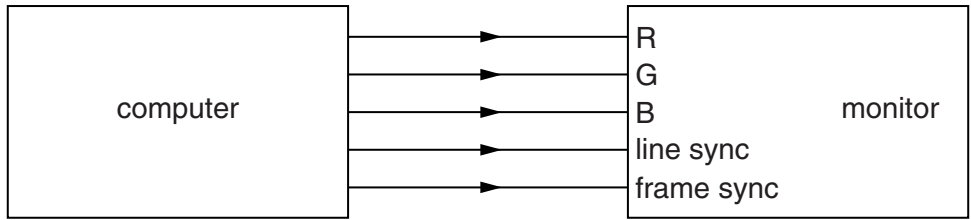


Fig. 1.1

- (a) Explain how the **five** signals control the raster scan which displays a colour picture on the monitor screen.

.....
.....
.....
.....
.....
.....
..... [5]

- (b) Each of the three video signals are packets of 7-bit words.
Explain why this suggests about 30 different levels of intensity for each pixel.

.....
.....
.....
..... [3]

- (c) Each video signal has its own cable.
The bandwidth of each video signal is 170 MHz.

Calculate the rate at which each packet passes through each video cable.

packet rate = MHz [2]

Fig. 1.2 is an oscilloscope trace of the frame sync signal.

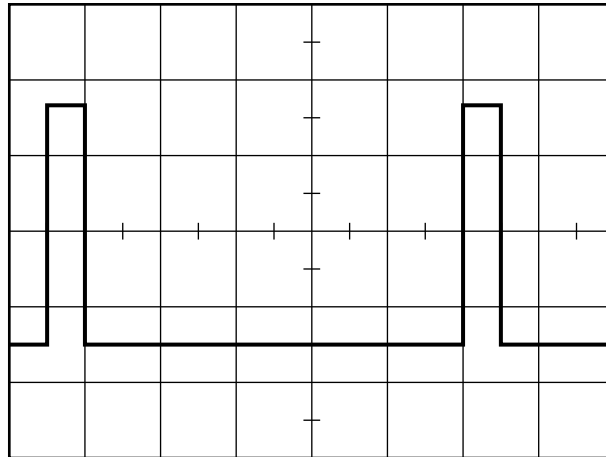


Fig. 1.2

(d) The oscilloscope settings are as follows:

- timebase setting 2 ms/div
- vertical scale 500 mV/div

Show that the refresh rate is about 100 Hz.

[2]

[Total: 12]

2 Fig. 2.1 shows a voltage-controlled amplifier and its transfer characteristic.

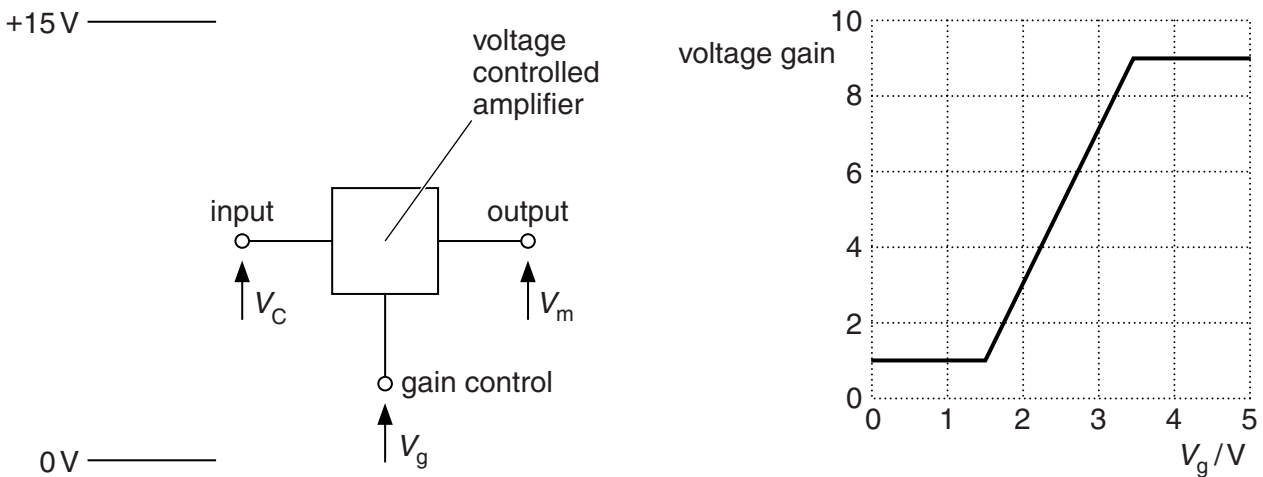


Fig. 2.1

(a) The amplifier is part of an amplitude modulator. The amplifier alters the amplitude of the carrier signal V_C by an amount which depends on the value of the signal V_g .

(i) In the absence of a modulating signal, the amplifier gain needs to be 5. Draw on Fig. 2.1 to show how a pair of resistors can be used to bias the amplifier. Show component values and justify them with calculations.

[3]

(ii) Draw on Fig. 2.1 to show how a capacitor should be connected to allow an audio frequency signal V_S to amplitude modulate the carrier signal V_C .

[1]

(iii) Suggest the maximum amplitude of audio frequency signal V_S which should be used. Explain your choice.

.....

.....

.....

.....

.....

.....

..... [3]

(b) Fig. 2.2 shows an amplitude demodulator for use with the modulator of Fig. 2.1.

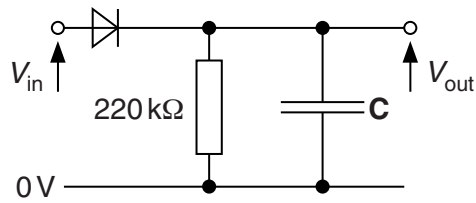


Fig. 2.2

- (i) The carrier signal V_C has a frequency of 450 kHz. Calculate a suitable value for the capacitor **C** if the audio frequency signal ranges from 50 Hz to 5 kHz.

C = pF [2]

- (ii) The diode in Fig. 2.2 has a voltage drop of 100 mV in forward bias. On Fig. 2.3 draw a voltage-time graph for V_{out} when V_{in} has the following properties.

carrier frequency	450 kHz
signal frequency	5 kHz
maximum carrier amplitude	600 mV
minimum carrier amplitude	200 mV

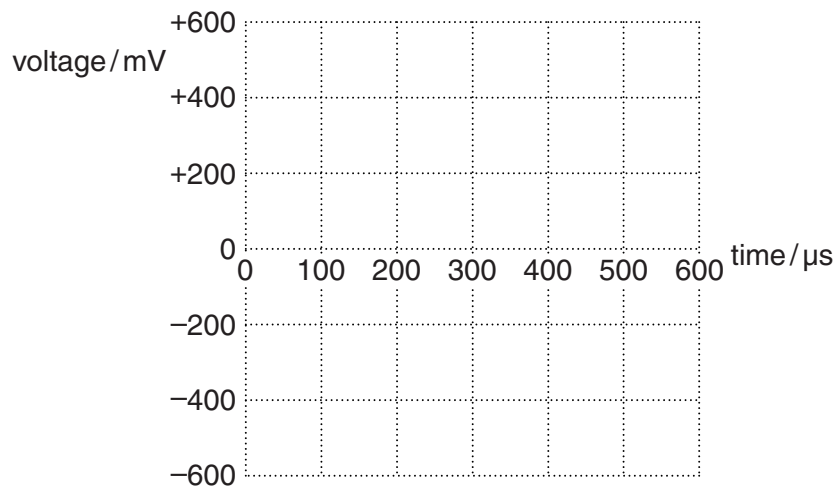


Fig. 2.3

[3]

[Total: 12]

- 3 Fig. 3.1 shows the block diagram of a demodulator of frequency modulated signals.

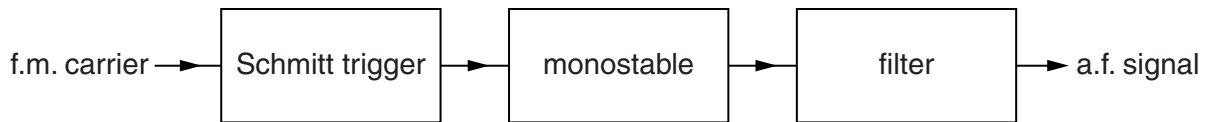


Fig. 3.1

- (a) Explain the function of the Schmitt trigger.

.....

.....

.....

..... [2]

- (b) The monostable produces a pulse of duration $2\mu\text{s}$ each time a falling edge arrives from the Schmitt trigger. The pulse goes from 0V to 5V and back. In the space below, draw a circuit diagram for the monostable. Include all component values and justify them.

[4]

(c) Fig. 3.2 contains the circuit diagram for the filter.

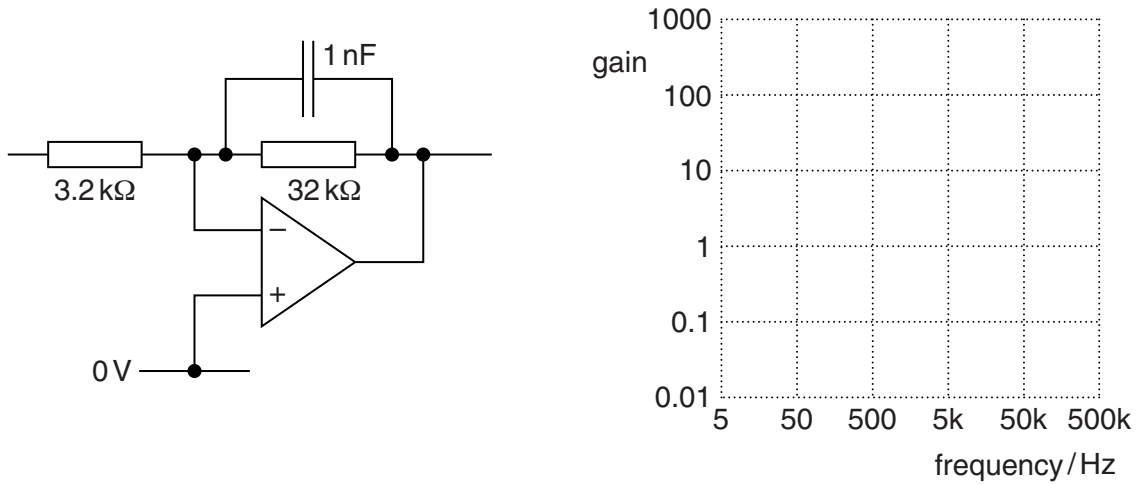


Fig. 3.2

(i) Draw a gain-frequency graph for the filter on the axes of Fig. 3.2. Show your calculations in the space below.

[4]

(ii) Calculate a value for the bandwidth required by the f.m. carrier.

bandwidth = kHz [2]

[Total: 12]

4 Fig. 4.1 is the circuit diagram of a pulse-width modulator (PWM).

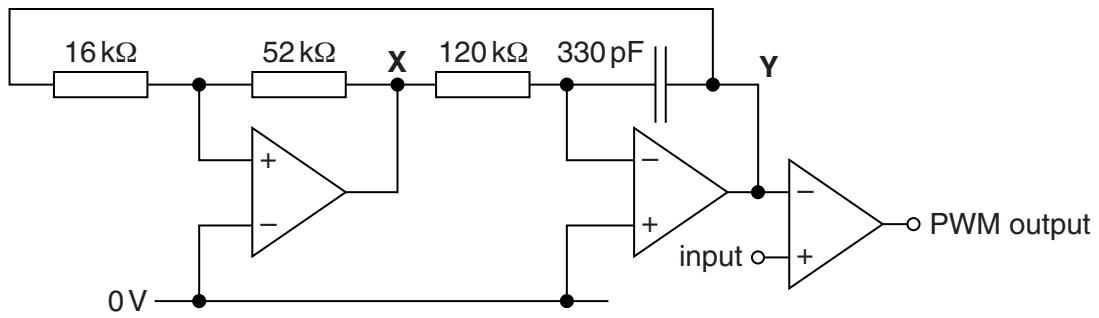


Fig. 4.1

(a) **X** is the output of the Schmitt trigger. It is either positive or negative. Explain, with calculations, why the signal at **Y** has to be raised above +4.0V to change **X** from negative to positive.

[3]

(b) Calculate how long it takes for the signal at **Y** to rise from -4.0V to +4.0V.

time = μs [2]

(c) Calculate the highest frequency signal at the modulator input which will be correctly encoded.

frequency = kHz [3]

(d) Fig. 4.2 is an incomplete block diagram for a demodulator of a PWM signal.



Fig. 4.2

(i) Complete the block diagram. Choose from the list below.

ramp generator Schmitt trigger tone control treble cut filter voltage amplifier [2]

(ii) Suggest a reason why the system contains a power amplifier.

.....
.....
.....
..... [1]

[Total: 11]

5 This question is about the transmission of signals as pulses of waves.

(a) Name the type of wave which carries pulses down an optical fibre.

..... [1]

(b) State and explain what happens to these pulses as they move along the fibre.

.....
.....
..... [2]

(c) Explain why optical fibre transmission systems usually have large values for their signal-to-noise ratio.

.....
.....
.....
..... [3]

(d) Optical fibre systems do **not** have problems with interference. This is partly because of the opaque cladding around the fibres.

(i) Explain why interference is a problem for systems which use radio waves.

.....
.....
.....
..... [3]

(ii) Explain how this can be overcome by systems which use radio waves.

.....
.....
.....
..... [3]

[Total: 12]

6 This question is about the use of frequency division multiplexing (FDM) for mobile phone systems. A mobile phone uses radio waves for two-way communication with the nearest phone mast.

(a) Suggest why mobile phone systems use FDM.

.....
.....
.....
.....
..... [3]

(b) A particular mast uses the frequencies between 909.375 MHz and 915.625 MHz. How many phones can simultaneously communicate with the mast if each phone signal has a bandwidth of 64 kHz?

number of phones = [2]

(c) The phones communicate by amplitude modulating a digital signal onto a carrier. Calculate the number of phones which could simultaneously communicate with the mast if frequency modulation was used instead. Explain your answer.

[3]

(d) Show in the space below how a bandpass filter for a phone can be assembled from a resistor, inductor and capacitor. Label the input and output. No component values are required.

[2]

[Total: 10]

7 Fig. 7.1 is an incomplete block diagram for part of a superhet radio receiver.

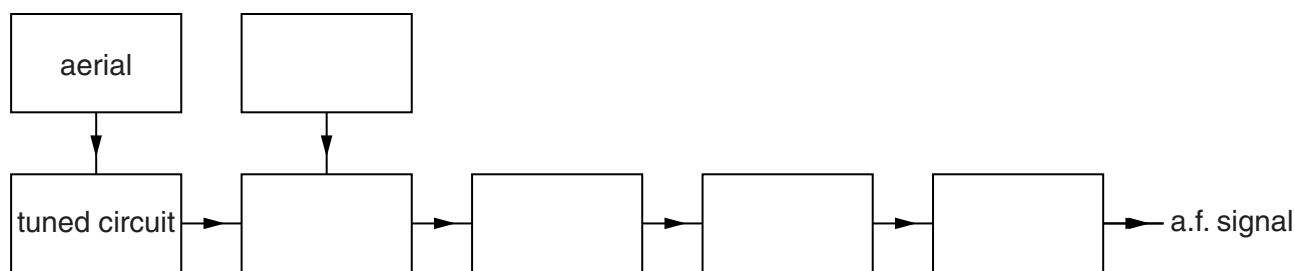


Fig. 7.1

(a) Complete the block diagram. Choose from the list below.

- amplifier demodulator filter mixer oscillator ramp generator Schmitt trigger** [5]

(b) The tuned circuit contains a 4.7 nH inductor and a variable capacitor. The circuit is to select a signal at 902.50 MHz from the aerial. Calculate the required setting of the variable capacitor.

capacitor = pF [2]

(c) Explain why a superhet receiver has better selectivity than a simple radio receiver.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

..... [4]

(d) Fig. 7.2 shows the rest of the block diagram for the superhet receiver.

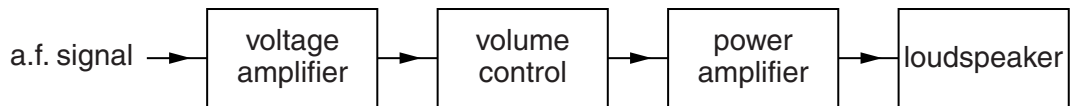


Fig. 7.2

The voltage amplifier has these properties:

- input impedance $100\text{ k}\Omega$
- voltage gain +50

Complete Fig. 7.3 to show how the amplifier can be assembled.
Show all component values.

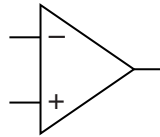


Fig. 7.3

[4]

[Total: 15]

8 Fig. 8.1 shows the circuit diagram of a 6-bit analogue-to-digital converter (ADC).

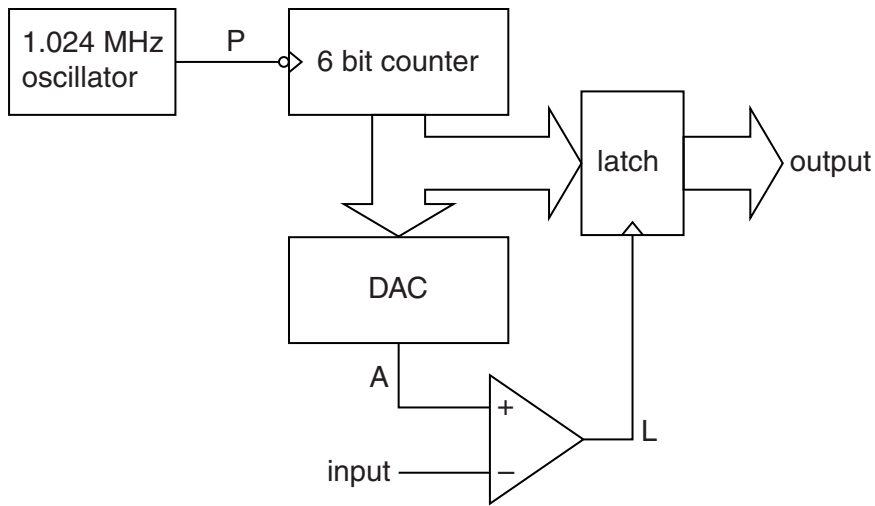


Fig. 8.1

(a) The block labelled DAC is a 6-bit digital-to-analogue converter.

(i) Describe the behaviour of a digital-to-analogue converter.

.....

.....

..... [1]

(ii) The DAC in Fig. 8.1 has a resolution of 100mV. Show that the range of the DAC is 6.3V.

[2]

(b) Describe the behaviour of the block labelled **latch**.

.....

.....

.....

.....

..... [3]

(c) Explain why the sample rate of the ADC of Fig. 8.1 is 16kHz.

.....
.....
.....
.....
..... [2]

(d) Explain how the ADC of Fig. 8.1 converts the voltage at **input** into a 6-bit word at **output**.

.....
.....
.....
.....
.....
.....
.....
.....
..... [5]

[Total: 13]

- 9 Fig. 9.1 shows how a number of computers (labelled A to Z) can exchange packets of data along a single cable.



Fig. 9.1

- (a) Each packet is a 1024-bit word. It starts with a 0 (the start bit) and ends with a 1 (the stop bit). Name the other parts of the packet and explain their function.

.....
.....
.....
.....
..... [4]

- (b) For correct transmission, each packet must be the only one on the line at that instant. Explain how this is achieved by the computers.

.....
.....
.....
.....
..... [3]

- (c) Each computer has a serial transmitter and serial receiver connected to the cable. Explain why only one of them is connected to the cable through an analogue switch.

.....
.....
.....
.....
..... [3]

[Total: 10]

Quality of Written Communication [3]

19
BLANK PAGE

PLEASE DO NOT WRITE ON THIS PAGE

PLEASE DO NOT WRITE ON THIS PAGE



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.