

GCE

Electronics

Unit **F612**: Signal Processors

Advanced Subsidiary GCE

Mark Scheme for June 2015

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, Cambridge Nationals, Cambridge Technicals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.



OCR will not enter into any discussion or correspondence in connection with this mark scheme.

© OCR 2015



Question			Answer	Marks	Guidance	
1	a	i	set means output/Q is high/1/5V; reset means output/Q is low/0/0V; active-high means inputs need to go high/1/5V to affect state of output;	1 1 1	accept rising-edge not falling edge	
		ii	does not change from previous value	1		not unqualified high or low not indeterminate
	b	i	A	P	Q	1
			1	1	0	
			1	0	0	
			0	1	0	
			0	0	1	
		ii	hold A low; pulse / hold B high; forcing P to be low and Q to be high;	1 1 1	Accept output of gate 1 as P	
2			<p>time →</p>	5	B correct [1] C correct [1] Q correct for first 4.5 squares [1] Q correct from 4.5 to 8.5 [1] Q correct from 8.5 to 12 [1]	

Question			Answer	Marks	Guidance
3	a	i		3	correct shape [1] correct phase [1] correct amplitude [1]
		ii		4	correct negative feedback circuit [1] non-inverting input directly to 0 V [1] correct input resistor [1] feedback resistor 2.5 x input resistor with ecf [1] accept non-inverting amplifier circuit <ul style="list-style-type: none"> • correct circuit for [1] • correct resistor ratio and input resistor for [1]
	b	i	amplitude	1	accept phase, (peak) voltage, power, polarity
		ii	(waveform) shape; frequency / period;	1 1	not wavelength

Question		Answer	Marks	Guidance
	c		3	straight line through origin [1] correct gradient [1] saturation at +13V and -13 V [1] accept 12.5 V to `13.5 V by eye for saturation look for three straight lines (by eye)
4	a	i	use of $G = 1 + \frac{R_f}{R_d}$; $G = 8.0(2)$; amplitude = 1.2 V;	1 1 1 ecf from any incorrectly calculated G $G = -7.0(2)$ gives (-)1.05 V for [1] $G = 2.5$ gives 0.375 V for [2]
		ii	amplifies difference between inputs; with very high gain; negative feedback (reduces overall gain); so that tiny difference between inputs can result in finite signal at output (that is not saturated);	1 1 1 1 accept $V_{out} = A(V_+ - V_-)$ A at least 1000
	b	i	less signal loss / greater signal transfer / greater output voltage with 120 k Ω ; 12 k Ω and 22 k Ω form a voltage divider; some microphone signal lost across 12 k Ω / appears across 22 k Ω ; input impedance needs to be much greater than output impedance for good signal transfer;	1 1 1 1

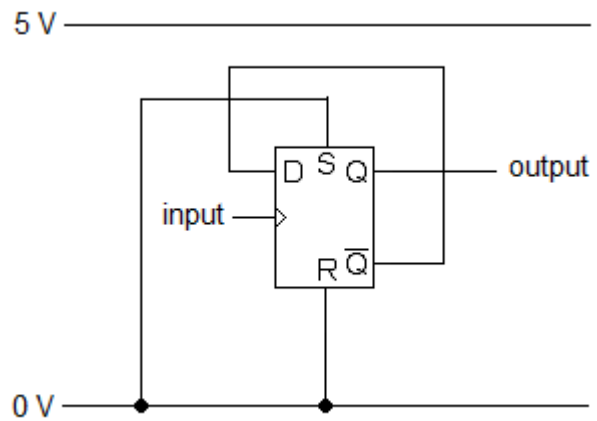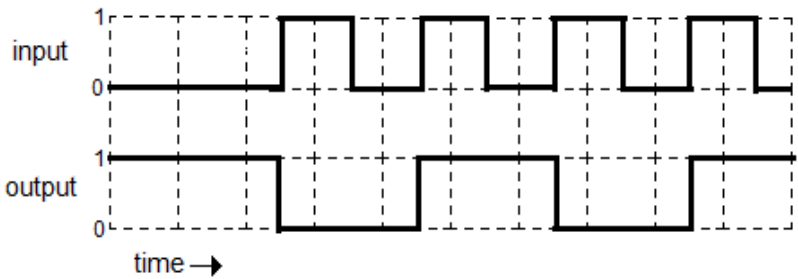Question		Answer	Marks	Guidance	
	ii	current in $22\text{ k}\Omega = 0.25/22\text{k} = 1.14 \times 10^{-5}\text{ A}$; internal signal amplitude = $1.14 \times 10^{-5} \times (22\text{k} + 12\text{k}) = 0.386\text{ V}$; current in $120\text{ k}\Omega = 0.386 / (12\text{k} + 120\text{k}) = 2.93 \times 10^{-6}\text{ A}$; amplitude at X = $2.93 \times 10^{-6} \times 120\text{k} = 351\text{ mV}$	1 1 1 1	accept 350 mV	
5	a	i		3	D to \bar{Q} [1] Q as output [1] S and R to 0 V [1]
		ii		2	only rising edges of input change the output [2] only falling edges of input change the output [1] accept input signal with any mark-space ratio ignore the position of the last falling edge
	b	i	counter resets when both C and A are high; which happens on every fifth pulse (at input);	1 1	accept when output is 0101 / gate inputs are high

Question		Answer					Marks	Guidance	
	ii	input	A	B	C	D	3	second row correct for [1] third row correct for [1] last two rows correct for [1]	
		0	1	1	0	0			
		1	0	0	1	0			
		2	0	0	0	0			
		3	1	0	0	0			
		4	0	1	0	0			
	iii	3 kHz					1		
6	a	use of $T = 0.5RC$; period of pulses at P = $0.5 \times 270k \times 32\mu = 4.32$ s; counter sequence has 2^3 states; sequence period is $8 \times 4.32 = 34.6$ s;					1 1 1 1	accept 8 states ecf on incorrect calculated value of T	
	b	<p>The diagram shows four digital signals over time. Signal A is a square wave with a period of 4 units. Signal B is a square wave that is high when A is high and low when A is low. Signal C is a square wave that is high when B is high and low when B is low. Signal X is a square wave that is high only when both A and C are high.</p>					4	A correct [1] ecf on A: B changes on each falling edge of A [1] ecf on B: C changes on each falling edge of B: [1] X is only high when A and C are the same. [1]	
	c	i	$Y = \overline{C}.B.\overline{A} + \overline{C}.B.A + C.B.\overline{A}$					1	

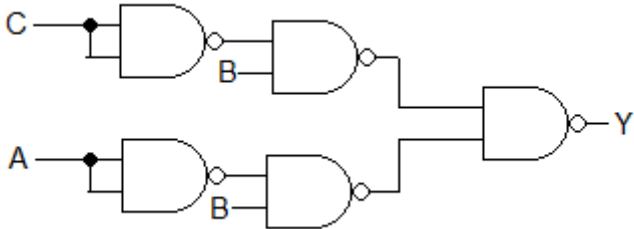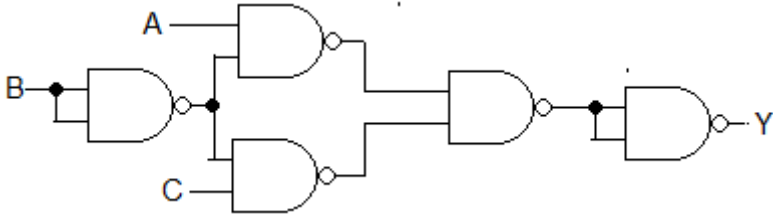Question	Answer	Marks	Guidance
ii	any two of the following for [1] each: use of theorems to show that $\overline{C}.B.\overline{A} + \overline{C}.B.A = \overline{C}.B$; use of theorems to show that $\overline{C}.B.\overline{A} + C.B.\overline{A} = B.\overline{A}$; use of theorems to show that $\overline{C}.B + C.B.\overline{A} = B.\overline{A}$; use of theorems to show that $\overline{C}.B.A + B.\overline{A} = \overline{C}.B$;	2	Ignore names of rules look for use of brackets and $A + \overline{A} = 1$ look for use of brackets and $C + \overline{C} = 1$ look for $B.(C + C.\overline{A})$ and $\overline{C} + C.\overline{A} (= \overline{C} + C.\overline{A} + \overline{A}) = \overline{A}$ look for $B.(C.A + \overline{A})$ and $\overline{A} + \overline{C}.A (= \overline{A} + \overline{C}.A + \overline{C}) = \overline{C}$
iii	EITHER  OR 	3	Correct circuit [3] One mistake for [2] Two mistakes for [1] A mistake is: <ul style="list-style-type: none"> • an extra gate • a missing gate • an incorrect gate • a missing input label (allow un-simplified version) ignore pairs of redundant inverters allow use of more than two inputs to gates

Question			Answer	Marks	Guidance
7	a	i	77 is 01110111, C7 is 11000111	1	
		ii	any three from following, [1] each: <ul style="list-style-type: none"> • MOSFET gate goes low / driver not activated; • so buzzer does not makes a noise / no current in buzzer; • LEDs a, b, c, d, e and f have current in them / glow; • so O is displayed; 	3	accept alarm / speaker
	b		any six of the following, [1] each: <ul style="list-style-type: none"> • reads input port until > 00010101; • switch A closed gives > 00010101; • then puts 01110111 on output port; • which turns off buzzer; • displays A; • waits 500 ms • until input port is not 00000001; • which means flooding / either switch pressed; • so passes control to b; 	6	ignore incorrect statements not until > 15

Question	Answer	Marks	Guidance
<p>c</p>	<p>for example:</p> <pre> graph TD subgraph LeftFlowchart b((b)) --> S3_in[/let S3 = input/] S3_in --> S3_gt_01{S3 > 01} S3_gt_01 -- yes --> x((x)) S3_gt_01 -- no --> z((z)) z --> S3_eq_00{S3 = 00} S3_eq_00 -- yes --> y((y)) S3_eq_00 -- no --> a((a)) end subgraph RightFlowchart x2((x)) --> S2_out[/let output=S2/] S2_out --> stop([stop]) y2((y)) --> S4_FF[let S4 = FF] S4_FF --> S4_out[/let output=S4/] S4_out --> pause[pause 500] pause --> a2((a)) end </pre>	<p>4</p>	<p>each correct segment of the program for [1]</p> <p>accept alternative which works as required</p> <p>a segment is incorrect if it does not have correct use of arrows, symbols and syntax</p> <p>top left segment: tests input port to see if I4 or I2 are high, where I0 can be high or low</p> <p>bottom left segment: tests input port to see if I0 is low and return control to a if I0 is high</p> <p>top right segment: if I4 or I2 are high, outputs the contents of S2 (C7) and either stops or loops back to x or b</p> <p>bottom right segment: if I0 is low, outputs FF, waits for 500 ms and returns to a</p>

Question		Answer	Marks	Guidance
8	a	<p>reduce amplitude of (unwanted) low frequency signals; any one of the following:</p> <ul style="list-style-type: none"> • from recording / microphone / signal source; • to remove noise / interference • signals can't be heard • compensates for transfer characteristic of microphone • compensates for transfer characteristic of speaker • adjusts balance to suit the listener 	1 1	accept remove/cut low frequencies or bass (notes) not just bass cut filter
	b		5	<p>correct circuit [1] resistor values between 1 kΩ and 10 MΩ [1] feedback resistor = 30 x input resistor [1] RC of filter network = 8 ms [1] use of $f_0 = \frac{1}{2\pi R C}$ to justify RC value [1]</p>

Quality of Written Communication

3	The candidate expresses complex ideas extremely clearly and fluently. Sentences and paragraphs follow on from one another smoothly and logically. Arguments are consistently relevant and well structured. There will be few, if any, errors of grammar, punctuation and spelling.
2	The candidate expresses straightforward ideas clearly, if not always fluently. Sentences and paragraphs may not always be well connected. Arguments may sometimes stray from the point or be weakly presented. There may be some errors of grammar, punctuation and spelling, but not such as to suggest a weakness in these areas.
1	The candidate expresses simple ideas clearly, but may be imprecise and awkward in dealing with complex or subtle concepts. Arguments may be of doubtful relevance or obscurely presented. Errors in grammar, punctuation and spelling may be noticeable and intrusive, suggesting weaknesses in these areas.
0	The language has no rewardable features.

OCR (Oxford Cambridge and RSA Examinations)
1 Hills Road
Cambridge
CB1 2EU

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; 1 Hills Road, Cambridge, CB1 2EU
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2015

