

GCE

Electronics

Unit **F615**: Communications Systems

Advanced GCE

Mark Scheme for June 2015

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, Cambridge Nationals, Cambridge Technicals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.



Mark schemes should be read in conjunction with the published question papers and the report on the examination.

OCR will not enter into any discussion or correspondence in connection with this mark scheme.


© OCR 2015

Question			Answer	Mark	Guidance
1	a	i	set intensity / brightness; of each pixel; one after the other / from left to right in successive rows / from top to bottom (on the screen);	1 1 1 1	ignore raster scan
		ii	as each pulse arrives; start to scan a new row of pixels;	1 1	not just new line
		pixels per second = $320 / 80\mu = 4.0 \times 10^6$; bandwidth = 2.0 MHz;	1 1	no ecf for incorrect pixel rate	
	iii iv	frame display time = $220 \times 80\mu = 17.6$ ms; refresh rate = 57 Hz; greater than 25 Hz; so image is flicker-free;	1 1 1 1	accept range of 20 to 30 Hz ecf from calculated refresh rate if less than 25 Hz	
	b	two more cables needed; allows separate video signals (for three pixels in a cluster); for red, green and blue pixels;	1 1 1	ignore RGB	
2	a		3	correct sinusoidal shape with constant amplitude [1] correct amplitude [1] correct period [1] accept any phase	

Question		Answer	Mark	Guidance
	b	Z; Y; 113; X	2	113 kHz for [1] X, Y and Z correct for [1] accept X and Y interchanged
	c	i	break frequency from 5 kHz to 10 kHz; $f_0 = \frac{1}{2\pi RC}$; use of C between 50 pF and 100 pF;	1 1 1 no ecf for incorrect break frequency
		ii	transfer characteristic <ul style="list-style-type: none"> • diode only conducts in forward bias; • with voltage drop; • which rises steeply with increasing current; circuit operation <ul style="list-style-type: none"> • only <u>negative</u> parts of signal amplified; • carrier frequency filtered out by capacitor and (feedback) resistor 	1 1 1 1 1 accept any value below 1 V look for high quality responses to circuit operation accept (rectified) signal smoothed by capacitor and resistor accept treble cut filter as capacitor and feedback resistor ignore references to gain
3	a	output has a frequency of 27.2 MHz (for zero volt signal); frequency increases/decreases with increasing signal voltage; amplitude of output remains constant;	1 1 1	ignore amplitude
	b	bandwidth = 200 kHz maximum frequency = 40 kHz	1 1	no ecf on incorrect bandwidth
	c	removes noise / interference added to FM signal; by restoring FM signal to a square wave / digital signal;	1 1	
	d	output of monostable is a fixed duration pulse; for each cycle/pulse of FM carrier; so mean voltage of monostable output changes for changing frequency of FM carrier; (treble cut) filter removes carrier frequencies; smoothing / averaging the pulses (producing a copy of the original signal);	1 1 1 1 1	accept rising / falling edge for cycle accept pulse spacing depends on frequency of carrier

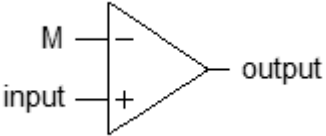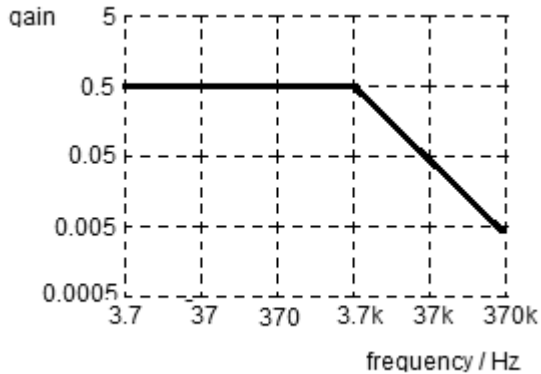Question		Answer	Mark	Guidance
4	a	<p>ST threshold calculation</p> <ul style="list-style-type: none"> $I = 13/42k = 3.09 \times 10^{-4} \text{ A};$ $V = 3.09 \times 10^{-4} \times 27k = 8.4 \text{ V};$ <p>RG calculation</p> <ul style="list-style-type: none"> $\frac{4 \times 8.4}{T} = \frac{13}{15k \times 3.3n}$ $T = 1.3 \times 10^{-4} \text{ s, so } f = 7.8 \text{ kHz};$ 	<p>1</p> <p>1</p> <p>1</p> <p>1</p>	<p>method shown [1] accept 13 x (27/42) not 13 x (-27/42)</p> <p>correct value [1]</p> <p>method shown [1]</p> <p>correct value [1]</p> <p>accept anything that rounds to 8 kHz with correct method for [2]</p>
	b	<p>i</p> 	<p>2</p>	<p>comparator with any input to M [1]</p> <p>correct input and output labels [1]</p>
		<p>ii</p> <p>voltage at input;</p> <p>sets mark-space ratio of output;</p>	<p>1</p> <p>1</p>	<p>ignore amplitude / signal</p> <p>ignore frequency</p> <p>ignore description of op-amp behaviour</p>
	c	<p>i</p> 	<p>5</p>	<p>$G = -\frac{R_f}{R_{in}}$</p> <p>use of $G = -\frac{R_f}{R_{in}}$ to calculate low frequency gain of (-) 0.51 [1]</p> <p>$f_0 = \frac{1}{2\pi RC}$</p> <p>use of $f_0 = \frac{1}{2\pi RC}$ to calculate break frequency of 3.7 kHz [1]</p> <p>suitable log axes labelled [1]</p> <p>correct shape [1]</p> <p>correct break frequency [1]</p> <p>accept 4, 40, 400 ... as frequency axis labels</p>
		<p>ii</p> <p>break frequency is close to maximum signal frequency that can be correctly coded;</p> <p>need at least two samples per signal cycle;</p> <p>maximum signal frequency should be $7.8 / 2 = 3.9 \text{ kHz};$</p>	<p>1</p> <p>1</p> <p>1</p>	

Question		Answer	Mark	Guidance
5	a	Any of the following for [1];	1	accept use optical fibre [1] as cladding stops outside signals [1]
		<ul style="list-style-type: none"> • put metal shielding around cables • keep cables away from other systems • keep cables short idea that interference is signal from other circuits;	1	accept use frequency / digital coding [1] as interference can be removed by ST (at receiver) [1]
b		any two of the following: <ul style="list-style-type: none"> • both cables follow same path • pick up the same interference • so can be removed by difference amplifier 	2	not noise
6	c	signal at A is copied to C by voltage follower;	1	
		signal at A is inverted and placed at B;	1	
		signals arrive at D and E with interference;	1	
		difference amplifier cancels out interference;	1	
		and recreates (double) the original signal (at F);	1	
a		each station is allocated a channel / carrier frequency; with a unique range of frequencies / bandwidth;	1 1	allow frequency for carrier
b	i	channel bandwidth = 9 kHz; channels = $(1607 - 527) / 9 = 120$	1 1	ecf 4.5 kHz gives 240 channels for [1]
	ii	much larger bandwidth per channel; so fewer channels / stations in the band;	1 1	
iii		EITHER		
		FM (receivers) can eliminate noise; by using limiters / Schmitt triggers; to restore shape of signal;	1 1 1	accept interference for noise, accept less susceptible to noise
		OR AM (receivers) can't eliminate noise; because it affects amplitude; so can't be separated from signal by demodulator;		

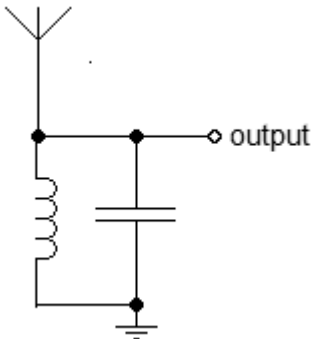Question	Answer	Mark	Guidance
7 a		5	correct arrangement of components [1] ignore resistor in series with aerial earthing / 0 V shown <u>and</u> output labelled [1] $LC = 1.9 \times 10^{-15} \text{ s}$ [1] C in range 1 pF to 1 μF [1] use of $f_0 = \frac{1}{2\pi\sqrt{LC}}$ to justify correct values [1]
b i	filter centre frequency 470 kHz; oscillator = 3650 + 470 = 4120 kHz;	1 1	accept 3180 kHz for [2] accept 4100, 4140, 3200 or 3160 kHz for [1]
	ii any four of the following: <ul style="list-style-type: none"> • oscillator produces signal of one frequency; • which is at carrier \pm filter frequency; • which amplitude modulates tuner signal in mixer; • to produce a copy of tuner signal; • which can pass through filter; 	4	not mixes / combines accept create sidebands
c i	amplifier; boosts signals from weak transmitter;	1 1	accept aerial [1] altering position / length increases signal from weak stations [1].
	ii filter; only lets through carrier and sidebands from one transmitter;	1 1	not tuned circuit
8 a i	takes (serial) bits from link one after the other; assembles them into (parallel) words;	1 1	allow just serial-to-parallel converter for [1]
	ii takes in binary words; outputs corresponding voltage;	1 1	allow just digital-to-analogue converter for [1]
b i	number of states = $4/0.025 = 160$; $2^7 = 128$, $2^8 = 256$; so needs 8 bits;	1 1 1	accept $\log_2 160 = 7.32$ correct answer with no working for [1]
	ii must sample twice in each cycle; sample frequency = $1/125\mu = 8 \text{ kHz}$; maximum signal frequency = 4 kHz;	1 1 1	

Question		Answer	Mark	Guidance
c	i	any five of the following; <ul style="list-style-type: none"> • pulse sets flip-flop • makes register load word from input • AND gate with one input high outputs pulses • clock pulses appear at CK • contents of register / bits appear at output in turn • counter output increases on each clock pulse • logic system resets flip-flop and counter at end 	5	
	ii	need one for each bit of the word at input; one for the start bit (before the word); one for the stop bit (at the end of the word);	1 1 1	
		Total	107	
		QWC	3	Overleaf
		=	110	

OCR (Oxford Cambridge and RSA Examinations)
1 Hills Road
Cambridge
CB1 2EU

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; 1 Hills Road, Cambridge, CB1 2EU
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2015

