

**Electronics**

Advanced GCE

Unit **F614**: Control Systems

**Mark Scheme for June 2011**

---

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of pupils of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, OCR Nationals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by Examiners. It does not indicate the details of the discussions which took place at an Examiners' meeting before marking commenced.

All Examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the Report on the Examination.

OCR will not enter into any discussion or correspondence in connection with this mark scheme.

© OCR 2011

Any enquiries about publications should be addressed to:

OCR Publications  
PO Box 5050  
Annesley  
NOTTINGHAM  
NG15 0DL

Telephone: 0870 770 6622  
Facsimile: 01223 552610  
E-mail: [publications@ocr.org.uk](mailto:publications@ocr.org.uk)

Question	Expected answer	Mark	Additional guidance															
1	<p>(a)</p> <table border="1" data-bbox="472 233 1081 491"> <thead> <tr> <th>A</th> <th>E</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>High impedance</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>High impedance</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>all combinations of A and E</p>	A	E	Q	0	0	High impedance	0	1	0	1	0	High impedance	1	1	1	<p>[1] [1] [1] [1]</p>	
A	E	Q																
0	0	High impedance																
0	1	0																
1	0	High impedance																
1	1	1																
	<p>(b)</p> <p>EITHER</p> <p>to allow more than one device to be connected to the databus</p> <p>OR</p> <p>to allow the databus to be bidirectional (owtte)</p>	<p>[1]</p>																
	<p>(c)</p> <p>Read kept low</p> <p>make data high [or 1 or 5V]</p> <p>make write high [or 1 or 5V] (turning on tri-state)</p> <p>(output of the tri-state) charges the capacitor to Y=5V</p> <p>Y = 5V so MOSFET on and Z pulled low.</p> <p>NOT gate inverts Z to make X high</p> <p>[max 3 marks]</p>	<p>[1] [1] [1] [1]</p>	<p>Some points may be in answer (d)</p>															
	<p>(d)</p> <p>make read high [or 1 or 5V]</p> <p>to turn tri-state on so data goes high to be read</p> <p>capacitor holds charge</p> <p>Write kept high</p> <p>max 3</p>	<p>[1] [1] [1]</p>	<p>Some points may be in answer (c)</p>															

Question	Expected answer	Mark	Additional guidance
2	(a) Ramp generator	[1]	Allow integrator
	(b) immediately negative	[1]	
	increasing	[1]	
	increasing	[1]	
	zero	[1]	
	zero	[1]	
	constant	[1]	
		[1]	
		[1]	
		[1]	
	(c) correct units conversion of R and C	[1]	
	change in $V = (-)9 \times 2 / (10 \times 10^6 \times 470 \times 10^{-9}) = (-)3.8$ (ecf)	[1]	
	minus sign in $\Delta V$	[1]	<u>-3.8V</u> gets 3 marks
	$V_{out} = 5 - 3.8 = 1.2V$ (ecf)	[1]	

Question	Expected answer	Mark	Additional guidance
3	(a) Path showing flow of information from output back to oscillator (wtte)	[1]	
	(b) The output of an open loop system does not change when the <u>conditions change</u> . Closed loop systems <u>automatically adjust</u> to keep the output at the desired level (owtte)	[1] [1]	
	(c) correct rectifier correct polarity of output capacitor for smoothing on dc output	[1] [1] [1]	
	(d) <u>LED</u> <u>photo-transistor</u> LED give out light when current/voltage present photo-x switches on/conducts when receives light	[1] [1] [1]	
	(e) to prevent accidents/electrocution/damage if high voltage signals connect to low voltage output to allows comparator to control oscillator turn on/off oscillator when V to high/low no electrical connection (owtte) up to max 3 marks	[1] [1] [1]	

Question	Expected answer	Mark	Additional guidance
(f)	<u>Top graph:</u> continues rising to 12V stabilises hunts around stable voltage <u>bottom graph:</u> square wave high until smoother voltage stabilises changes each time smoother voltage crosses 12V	[1] [1] [1] [1] [1] [1]	
(g)	an accurate reference would not be produced until the smoother voltage was >12V output does not switch at correct voltage correct comments comparing voltage from potential divider with voltage from zener smoothed output would be too large (>12V)	[1] [1]	

Question		Expected answer	Mark	Additional guidance	
4	(a)	blue LED glows	[1]		
		first two lines send 08H to output port	[1]		
		makes output 00001000 so <b>Q<sub>3</sub> high</b>	[1]		
	(b)	dry: MOVI S <sub>n</sub> , 88 OUT Q, S <sub>n</sub> RET  (n is any integer between 0 and 7)	[2] [1] [1]	1 mark for MOVI S <sub>n</sub> and 1 mark for 88	
	(c)	MOVI S0, <u>80</u>  <u>JZ skip</u>	[1]  [2]		
	(d)	turn off blue LED and heater&motor toggle lsb store 100 decimal in S7; do nothing for 1ms take away 1 from S7; keep going back until S7=0 makes the yellow LED flashes continuously everything else off (implied)	[1] [1] [1] [1] [1] [1] [1] [1]	turn everything off 2 marks	
	(e)	(i)	code can be tested in small chunks code can easily be reused from other projects code can be used several times in the same program saving memory saves development time makes program easier to understand max 2	[1] [1]	

Question	Expected answer	Mark	Additional guidance
	<p>(ii) program counter loaded with return address from top of stack stack pointer decremented/incremented return address stored on stack [max 3]</p>	<p>[1] [1] [1]</p>	
(f)	<p><u>resets</u> program counter to 0/makes program go to line 0 lights blue LED and waits for hands to be sensed which stops the yellow LED flashing/cancels fault/everything else off</p>	<p>[1] [1] [1]</p>	



Question	Expected answer	Mark	Additional guidance
5	(a) input connected to gate through capacitor output connected to drain through capacitor	[1] [1] [1] [1]	
	(b) $I = \frac{V_S - V_D}{R} = \frac{15 - 3}{680 \times 10^3} = 1.8 \times 10^{-5} \text{ A}$ $R = \frac{V}{I} = \frac{3}{1.8 \times 10^{-5}} = 167000 \Omega$ Correct calculation of pd across 680k resistor Calculation of I dividing by 680k (ecf) Calculation of R by diving 3 by I (ecf)	[1] [1] [1]	
	(c) I=40mA V across 180Ω resistor is 0.04x180=7.2V V <sub>D</sub> =15-7.2=7.8V	[1] [1] [1]	7.2V for 2 marks
	(d) To allow V <sub>D</sub> to wobble up and down (owtte) allows maximum (7V) amplitude at output (owtte)	[1] [1]	Allow above half maintains pd across MOSFET for second mark.
	(e) 2.6V	[1]	
	(f) correct conversion of mA to A for ΔI correct calculation of gradient of sloping graph g <sub>m</sub> =0.1S Identification of 180Ω resistor Calculation of gain = -g <sub>m</sub> xR = -0.1x180=-18	[1] [1]	1X10 <sup>9</sup> S for 1 mark

Question	Expected answer	Mark	Additional guidance	
5	(g)	The new MOSFET has different characteristics Either	[1]	
		g <sub>m</sub> is larger	threshold voltage is lower	
	(h)	Drawing of MOSFET amplifier with resistor connected between gate and drain. Correctly drain biased MOSFET amplifier	[1] [1]	

Question	Expected answer	Mark	Additional guidance
6	(a) 8x2=16	[1]	
	(b) number of addresses $2^3=8$ each bit needs its own wire to get data in and out	[1] [1]	
	(c) each A from a module to a corresponding A on bus each control line to corresponding control bus line data lines from 1 <sup>st</sup> module to 2 different data-bus lines data lines from 2 <sup>nd</sup> module to 2 different data-bus lines from 1 <sup>st</sup> module	[1] [1] [1] [1]	
	(d) read and write from each module to read and write bus $D_1$ & $D_0$ from each modules to data bus $A_2-A_0$ on each module to $A_2-A_0$ on bus CE on each module connected to some logic/demultiplexer fro $A_3$ /CE bus $A_3$ correctly decoded to turn on one module when high one when low CE decoded to control access to combined modules	[1] [1] [1] [1] [1] [1]	

**Quality of Written Communication**

- 3** The candidate expresses complex ideas extremely clearly and fluently. Sentences and paragraphs follow on from one another smoothly and logically. Arguments are consistently relevant and well structured. There will be few, if any, errors of grammar, punctuation and spelling.
- 2** The candidate expresses straightforward ideas clearly, if not always fluently. Sentences and paragraphs may not always be well connected. Arguments may sometimes stray from the point or be weakly presented. There may be some errors of grammar, punctuation and spelling, but not such as to suggest a weakness in these areas.
- 1** The candidate expresses simple ideas clearly, but may be imprecise and awkward in dealing with complex or subtle concepts. Arguments may be of doubtful relevance or obscurely presented. Errors in grammar, punctuation and spelling may be noticeable and intrusive, suggesting weaknesses in these areas.
- 0** The language has no rewardable features.

**OCR (Oxford Cambridge and RSA Examinations)**  
**1 Hills Road**  
**Cambridge**  
**CB1 2EU**

**OCR Customer Contact Centre**

**14 – 19 Qualifications (General)**

Telephone: 01223 553998

Facsimile: 01223 552627

Email: [general.qualifications@ocr.org.uk](mailto:general.qualifications@ocr.org.uk)

**[www.ocr.org.uk](http://www.ocr.org.uk)**

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

**Oxford Cambridge and RSA Examinations**  
is a Company Limited by Guarantee  
Registered in England  
Registered Office; 1 Hills Road, Cambridge, CB1 2EU  
Registered Company Number: 3484466  
OCR is an exempt Charity



**OCR (Oxford Cambridge and RSA Examinations)**  
Head office  
Telephone: 01223 552552  
Facsimile: 01223 552553