

Unit 4: Principles of Electrical and Electronic Engineering


LO1: Understand digital electronics

D type bistable flip-flop

The expected duration is: 2 hours


Instructions and answers for teachers

These instructions should accompany the OCR resource ‘Understand digital electronics – D type bistable flip-flop’ activity which supports Cambridge Technicals in Engineering Level 3.

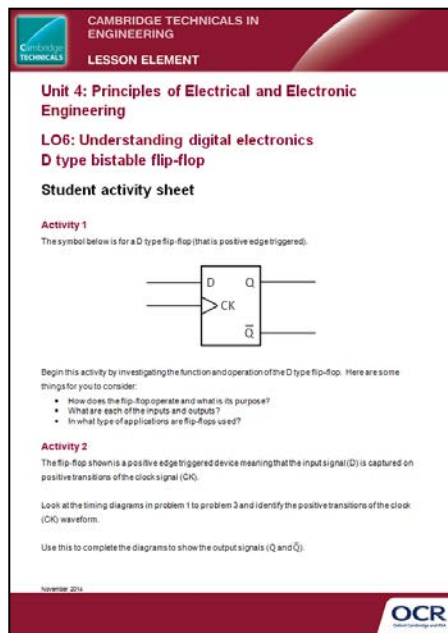

Unit 4: Principles of Electrical and Electronic Engineering
LO6: Understanding digital electronics
D type bistable flip-flop
Student activity sheet

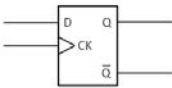Activity 1
The symbol below is for a D type flip-flop (that is positive edge triggered).




Begin this activity by investigating the function and operation of the D type flip-flop. Here are some things for you to consider:

- How does the flip-flop operate and what is its purpose?
- What are each of the inputs and outputs?
- In what type of applications are flip-flops used?

Activity 2
The flip-flop shown is a positive edge triggered device meaning that the input signal (D) is captured on positive transitions of the clock signal (CK).

Look at the timing diagrams in problem 1 to problem 3 and identify the positive transitions of the clock (CK) waveform.

Use this to complete the diagrams to show the output signals (Q and \bar{Q}).

Version 2014 

The Activity:

In this task the students investigate the functions and operations of a D Type flip-flop featuring a set of tasks.



This activity offers an opportunity for English skills development.



This activity offers an opportunity for maths skills development.


Suggested timings:

2 hours

Activity 1

In Activity 1 learners are tasked to investigate the function and operation of the D type flip flop and to consider:

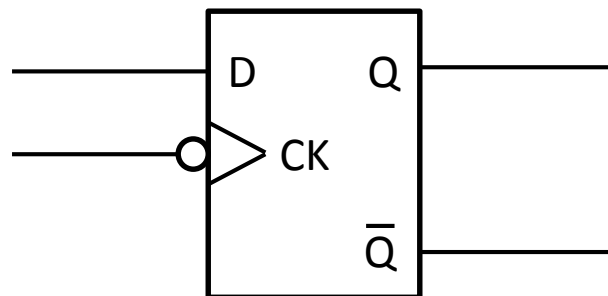- How does the flip flop operate and what is its purpose?
- What are each of the inputs and outputs?
- In what type of applications are flip flops used?



Solutions

- The D type flip flop is a latching device with outputs that have two stable states. This means that the output can be switched from logic 0 to logic 1, or logic 1 to logic 0 when required. Once set into either of these states it will remain there indefinitely so long as power is maintained to the device. For this reason it is often termed a 'bistable'.
- The purpose of a D type flip flop is to act as a latch or memory or storage device. It can store the information present on its inputs.
- The terminals are as follows:


D	The terminal labelled D is called the data input terminal and is where the flip flop receives data
CK	CK is the clock input. When a logic 1 is applied to the terminal, whatever signal is on the D terminal (0 or 1) is transferred to the Q terminal. For the device shown this is usually referred to as rising edge triggered.
Q	Q is the output terminal
\bar{Q}	Q bar or NOT Q is another output terminal which is the inverse of Q

- Typical applications of the D type flip flop are: Latches, Counters, Memory Devices, Shift Registers.


Activity 2:

In Activity 2 learners are asked to complete timing diagrams for a positive edge triggered D type flip flop. Solutions to Activity 2 are given below. Note that input signal D is captured on positive transitions of CK only. Learners are tasked to complete Q and \bar{Q} .


Solution to Problem 1

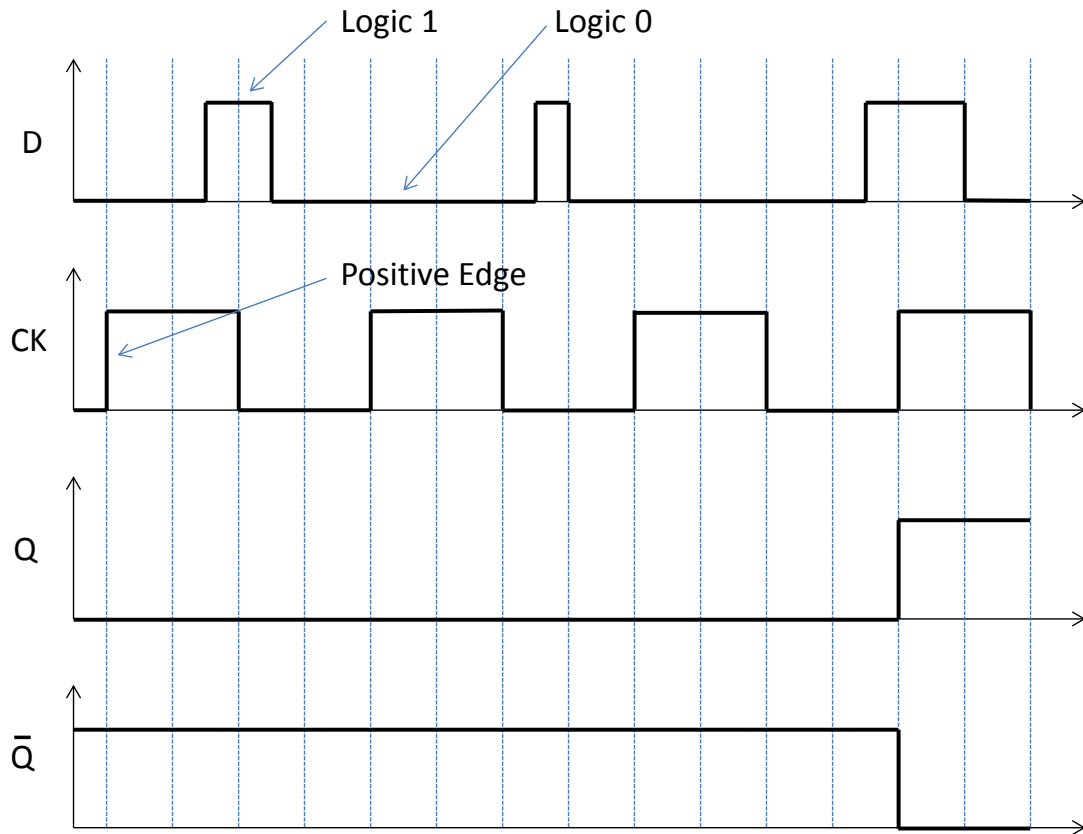

Solution to Problem 2

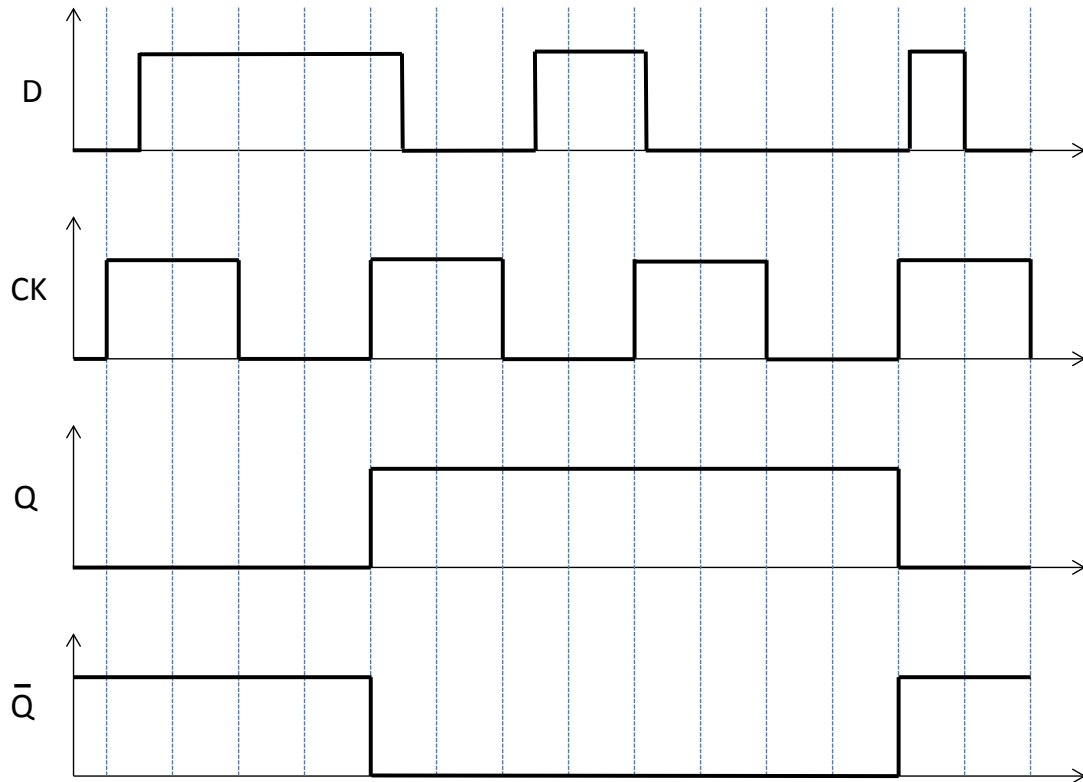


Solution to Problem 3

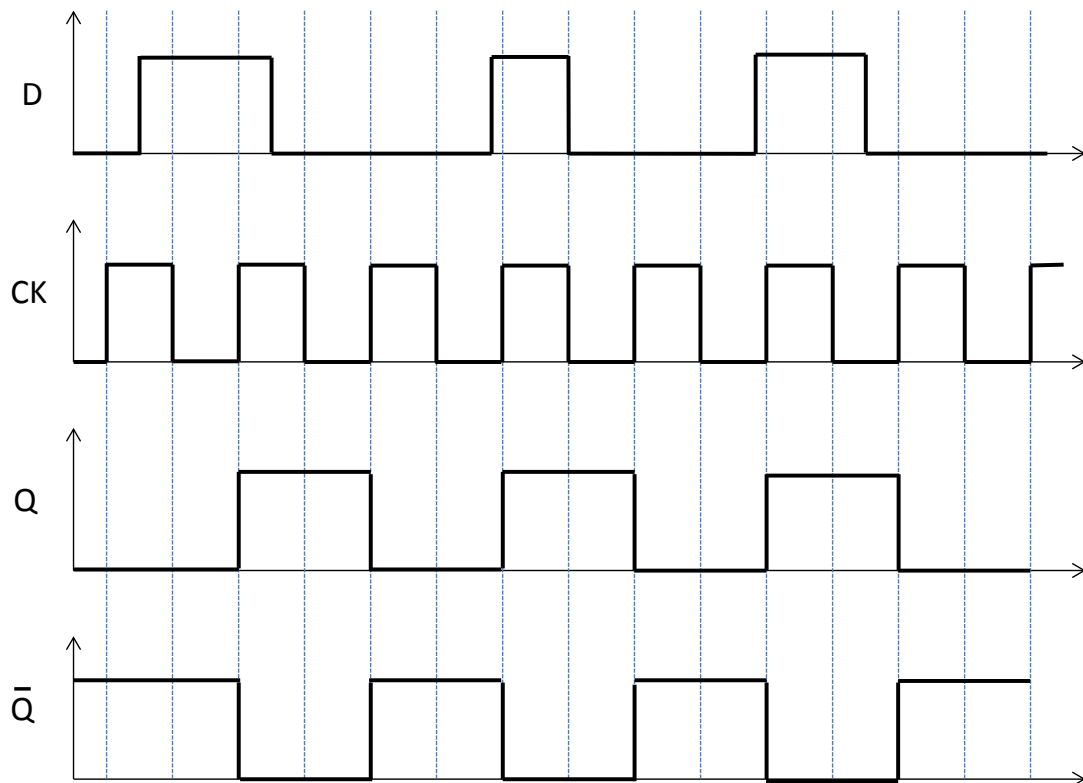


Activity 3:

In Activity 3 learners are asked to complete timing diagrams for a negative edge triggered D type flip flop. Solutions to Activity 3 are given below. Note that input signal D is captured on negative transitions of CK only. Learners are tasked to complete Q and \bar{Q} .


Solution to Problem 4

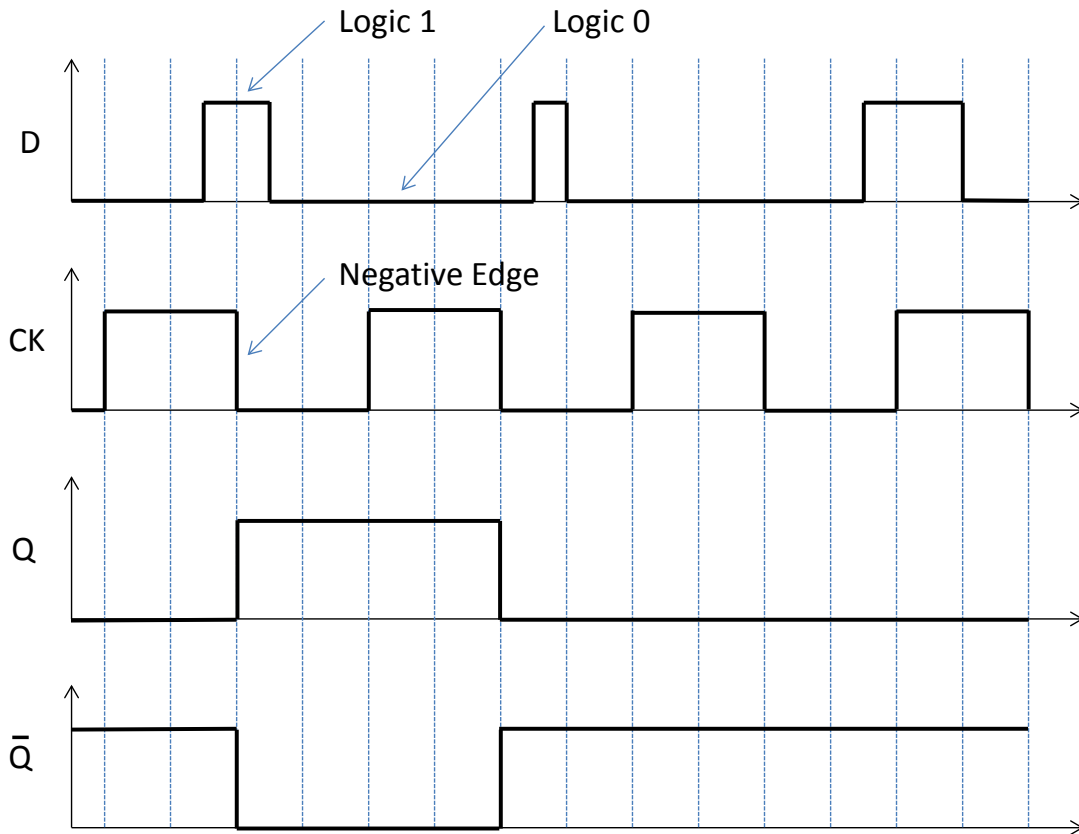

Solution to Problem 5

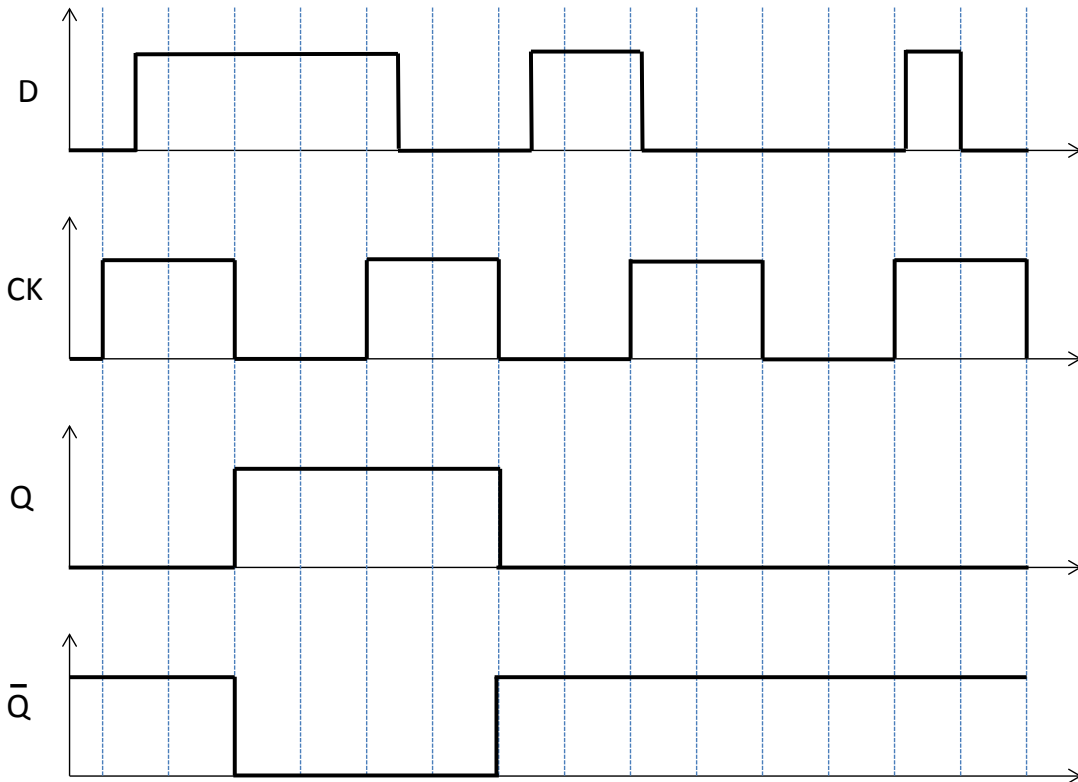


Solution to Problem 6

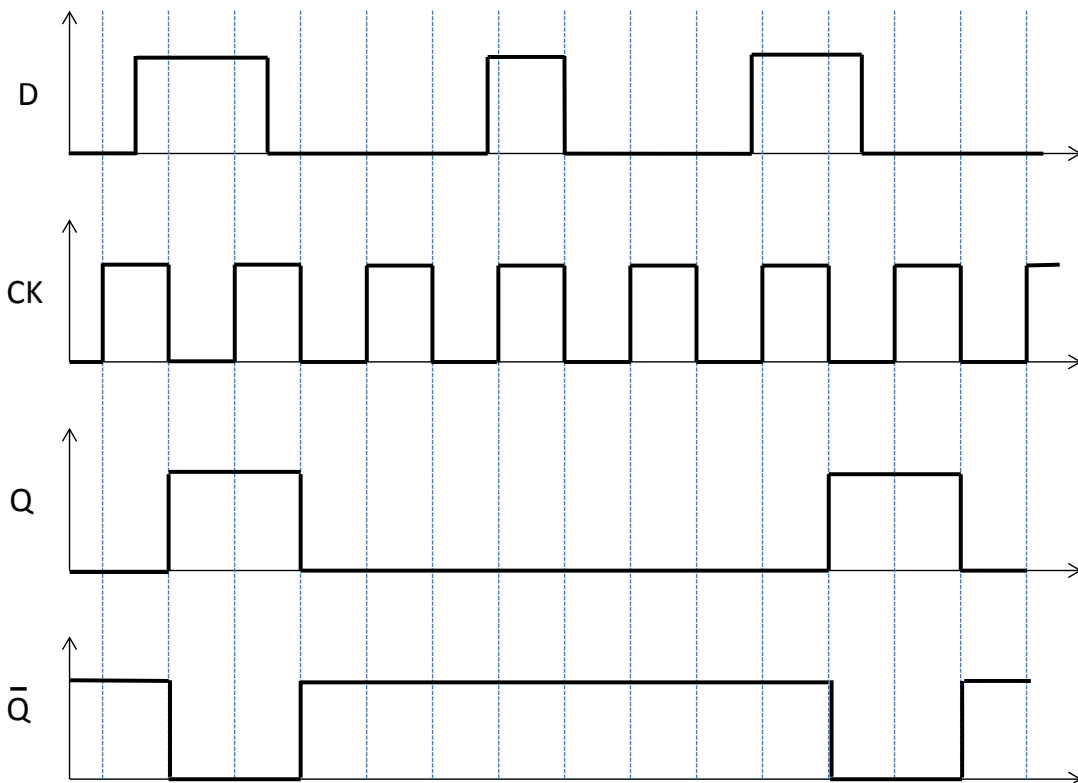


Activity 4:

For Activity 4 learners are asked to consider building or simulating a circuit containing a D type flip flop. Learners may have access equipment where this could be undertaken practically. An alternative may be to undertake a simulation using simulation software. Learners have been provided with a link to a free web-based simulation tool. This tool is free and will simulate many different types of circuit. Free sign up is required.
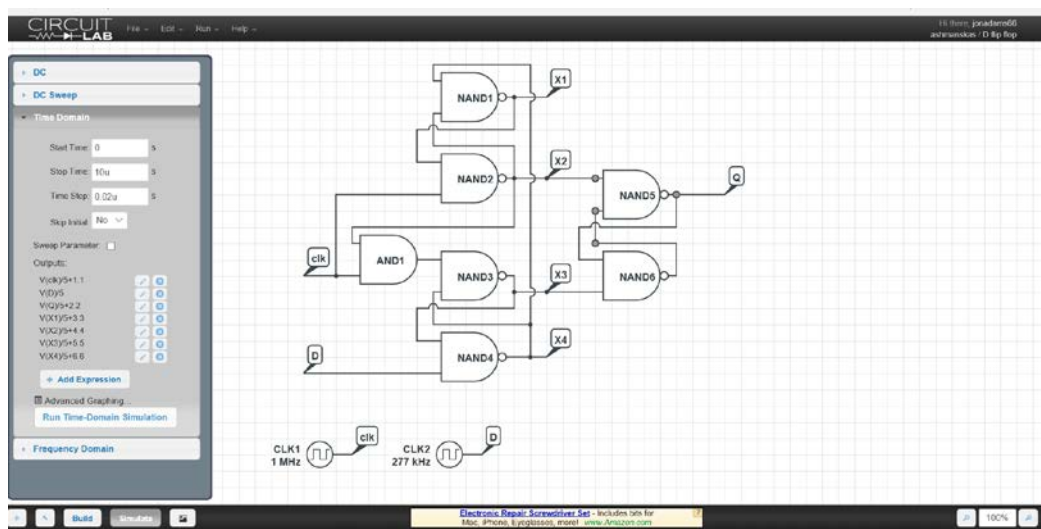
<https://www.circuitlab.com/circuit/ywmw4t/d-flip-flop/>



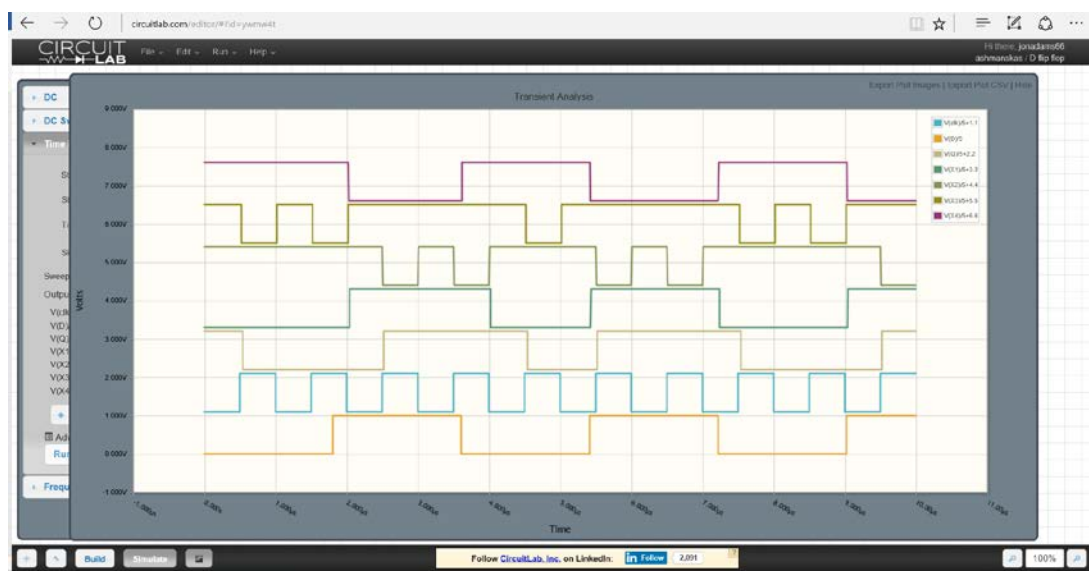The simulation provided produces a timing diagram from which learners might determine that the D type flip flop is operating correctly. Typical simulation results are shown below. These show a change in output with a change in input based on the clock transition (from high to low).



To complete the activity learners are tasked to explain the function of the S and R input pins on the D type flip flop. These are not shown in this simulation.

S	S is the SET input. Applying a logic 1 to the S input will make Q logic 1, and \bar{Q} logic 0. This will happen irrespective of the state of any signal on the D or CK inputs
R	R is the RESET input. Applying a logic 1 to the S input will make Q logic 0, and \bar{Q} logic 1. This will happen irrespective of the state of any signal on the D or CK inputs

It should be noted that S and R pins are present on most flip flop devices.



We'd like to know your view on the resources we produce. By clicking on the 'Like' or 'Dislike' button you can help us to ensure that our resources work for you. When the email template pops up please add additional comments if you wish and then just click 'Send'. Thank you.

OCR Resources: *the small print*

OCR's resources are provided to support the teaching of OCR specifications, but in no way constitute an endorsed teaching method that is required by the Board, and the decision to use them lies with the individual teacher. Whilst every effort is made to ensure the accuracy of the content, OCR cannot be held responsible for any errors or omissions within these resources. We update our resources on a regular basis, so please check the OCR website to ensure you have the most up to date version.

© OCR 2018 - This resource may be freely copied and distributed, as long as the OCR logo and this message remain intact and OCR is acknowledged as the originator of this work.

OCR acknowledges the use of the following content: Maths and English icons: Air0ne/Shutterstock.com