


Unit 7: Electrical devices

LO3: Understand how to use signal conditioning techniques and signal conversion devices

Digital to Analogue conversion – the R-2R ladder

Instructions and answers for teachers

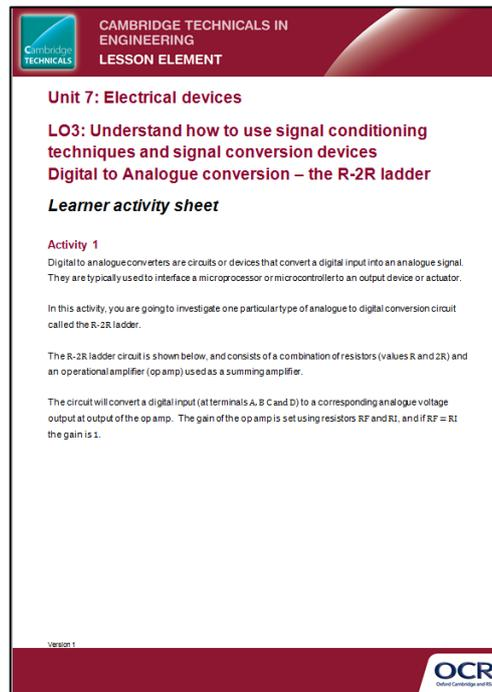These instructions should accompany the OCR resource ‘LO3: Understand how to use signal conditioning techniques and signal conversion devices Digital to Analogue conversion – the R-2R ladder’ activity which supports Cambridge Technicals in Engineering Level 3.



**CAMBRIDGE TECHNICALS IN
ENGINEERING
LESSON ELEMENT**

Unit 7: Electrical devices

LO3: Understand how to use signal conditioning techniques and signal conversion devices
Digital to Analogue conversion – the R-2R ladder

Leamer activity sheet

Activity 1
Digital to analogue converters are circuits or devices that convert a digital input into an analogue signal. They are typically used to interface a microprocessor or microcontroller to an output device or actuator.

In this activity, you are going to investigate one particular type of analogue to digital conversion circuit called the R-2R ladder.

The R-2R ladder circuit is shown below, and consists of a combination of resistors (values R and 2R) and an operational amplifier (op amp) used as a summing amplifier.

The circuit will convert a digital input (at terminals A, B and C) to a corresponding analogue voltage output at output of the op amp. The gain of the op amp is set using resistors R_F and R_I , and if $R_F = R_I$ the gain is 1.

Version 1

OCR
Oxford Cambridge and RSA

The Activity:

In this task the students are tasked with familiarising themselves with a R-2R ladder.



This activity offers an opportunity for English skills development.



This activity offers an opportunity for maths skills development.

Suggested timings:

2 hours


Activity 1

In Activity 1 learners are required to investigate the operation of a digital to analogue converter using an R-2R ladder.

The circuit diagram is shown below.

A good description of operation can be found at the following web link:
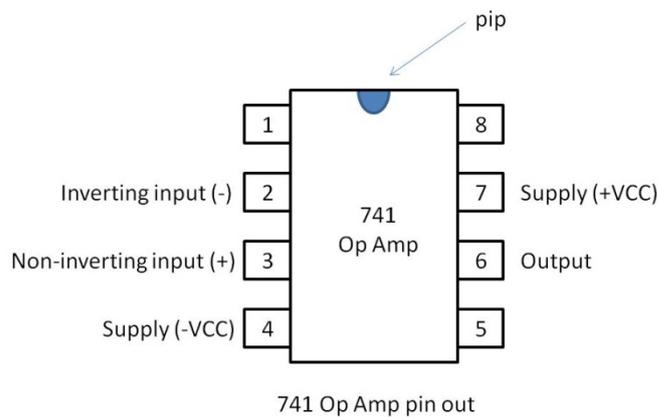
<http://www.circuitgallery.com/2012/04/digital-to-analog-converter-using-r-2r.html>



Output voltage is given by the following formula:

$$\text{Analogue Output (V)} = -\frac{RF}{RI} \left(\frac{D}{2} + \frac{C}{4} + \frac{B}{8} + \frac{A}{16} \right)$$

Learners should concentrate on the basic operation of the circuit, which requires basic knowledge of Ohm's Law, resistors in series and parallel, and the potential divider circuit.

Learners also need to understand the operation of the summing operational amplifier.

Activity 2

For Activity 2 learners are tasked to perform an experiment to investigate the operation of the R-2R ladder circuit.


Learners could build the circuit using breadboard, veroboard (and soldered construction) or using a printed circuit board.

Alternatively or additionally, the circuit could be simulated using circuit simulation software.

The components required are shown below, including a pin out diagram of the 741 op amp.

Equipment you will need:

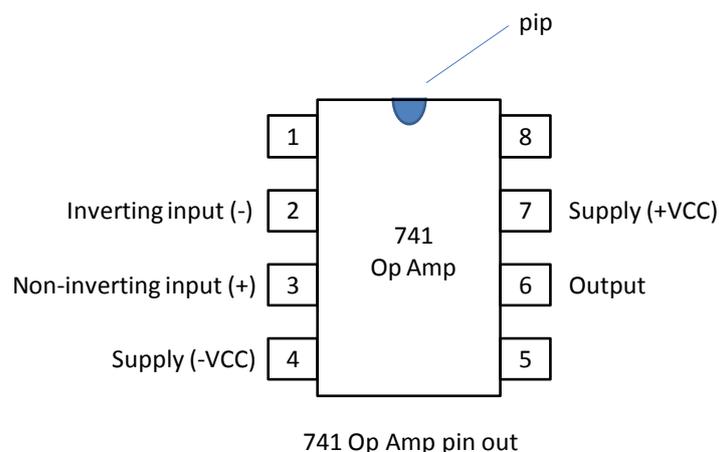Op Amp (741)
 Resistors ($R = 1K$, $R_F = 1K$, $R_I = 1K$) – to make $2R$ you will need 2 x 1K resistors in series
 Breadboard or veroboard
 Connecting wire
 Power supply (with positive and negative outputs)
 Multimeter (or oscilloscope) to measure output voltage



Learners should investigate the circuit and tabulate results. Output voltage should be calculated and measured for all combinations of digital inputs. Results should be tabulated and plotted.

A	B	C	D	Output Voltage (calculated)	Output Voltage (measured)
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		


Continue the table to include all combinations of digital inputs to A, B, C and D.

There are 16 combinations in total, and so this is often termed a '16 bit digital to analogue converter'.

Answers to questions:

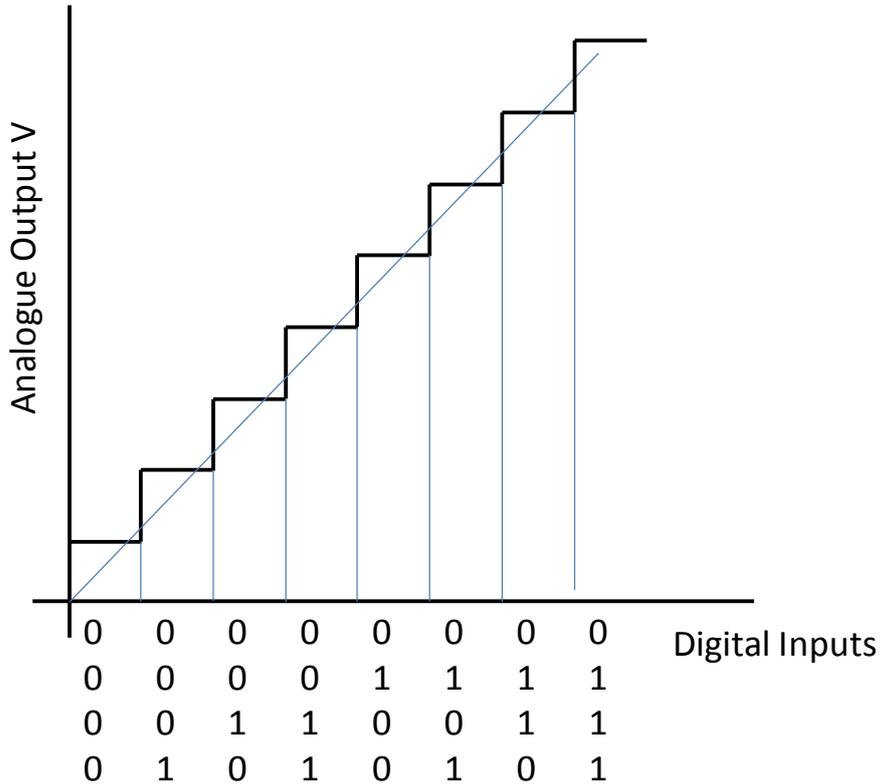1. **Does the circuit perform as expected – comment on the shape of the graph?**

Learners should comment on the performance of the circuit. The graph will be a stepped graph of output voltage vs. digital inputs. The graph will be 'linear'. Each step represents changing digital inputs, with small steps for changes in the least significant bit (D) and large steps for changes in the most significant bit (A). Typical graph shape is shown below:



2. **Do the measured values of output voltage agree with the calculated values – and if not, why?**

Learners should comment on the agreement of calculated and measured values. Discrepancies are likely to be due to experimental error (such as misread values) or component tolerances.

3. **How could the circuit be extended to include further digital inputs?**

Further digital inputs can be added by adding more R and 2R components to the ladder to add further bits.

4. How is the R-2R ladder principle used in the design of commercial Digital to Analogue converter integrated circuits?

The R-2R ladder is used to form the internal workings of many commercial digital to analogue converter integrated circuits. These typically have 8, 10, 12 or 16 digital inputs, and an analogue output. Learners could explore suitable manufacturer data sheets.

Teachers could produce a similar activity for learners to explore the operation of analogue to digital conversion.



We'd like to know your view on the resources we produce. By clicking on the 'Like' or 'Dislike' button you can help us to ensure that our resources work for you. When the email template pops up please add additional comments if you wish and then just click 'Send'. Thank you.

OCR Resources: the small print

OCR's resources are provided to support the teaching of OCR specifications, but in no way constitute an endorsed teaching method that is required by the Board, and the decision to use them lies with the individual teacher. Whilst every effort is made to ensure the accuracy of the content, OCR cannot be held responsible for any errors or omissions within these resources. We update our resources on a regular basis, so please check the OCR website to ensure you have the most up to date version.

© OCR 2015 - This resource may be freely copied and distributed, as long as the OCR logo and this message remain intact and OCR is acknowledged as the originator of this work.

OCR acknowledges the use of the following content: Maths and English icons: Air0ne/Shutterstock.com

Please get in touch if you want to discuss the accessibility of resources we offer to support delivery of our qualifications: <mailto:resources.feedback@ocr.org.uk>