



Oxford Cambridge and RSA

Thursday 9 January 2020 – Afternoon

Level 1/2 Cambridge National in Systems Control in Engineering

R113/01 Electronic principles

Time allowed: 1 hour



You must have:

- a scientific or graphical calculator



Please write clearly in black ink. **Do not write in the barcodes.**

Centre number

--	--	--	--	--

Candidate number

--	--	--	--

First name(s)

Last name

INSTRUCTIONS

- Use black ink. You can use an HB pencil, but only for graphs and diagrams.
- Write your answer to each question in the space provided. If you need extra space use the lined pages at the end of this booklet. The question numbers must be clearly shown.
- Answer **all** the questions.

INFORMATION


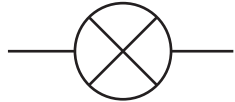

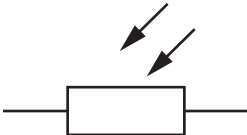
- The total mark for this paper is **60**.
- The marks for each question are shown in brackets [].
- Quality of written communication will be assessed in questions marked with an asterisk (*).
- This document has **8** pages.

ADVICE

- Read each question carefully before you start your answer.

Answer **all** the questions.

- 1 (a) Complete the table by naming the component for each electronic symbol shown. Part of each answer has been given for you.

Symbol	Component
	polarised
 lamp
 to switch
 resistor

[4]

- (b) Calculate the resistance in ohms of a lamp rated at 12 volts 0.5 amperes.

.....

 [3]

- (c) Calculate the energy in kilowatt hours when a 900 watt hairdryer is used for 10 minutes.

.....

 [3]

- (d) Circle the **two** polarised capacitors in the list of capacitor types below.

ceramic polyester electrolytic polystyrene tantalum

[2]

- 2 (a) Complete the table by identifying which components are **input** devices and which are **output** devices.

The first one has been done for you.

Component	Type of Device
Solenoid	Output
Relay	
Microphone	
Phototransistor	
Pressure switch	
Light Emitting Diode	
Touch screen	

[6]

- (b) The diagram below shows a resistor and a colour code chart.



Colour	Band 1	Band 2	Band 3	Band 4
Black	0	0	×1	
Brown	1	1	×10	±1%
Red	2	2	×100	±2%
Orange	3	3	×1K	
Yellow	4	4	×10K	
Green	5	5	×100K	±0.5%
Blue	6	6	×1M	±0.25%
Violet	7	7	×10M	
Grey	8	8		
White	9	9		
Gold			×0.1	±5%
Silver			×0.01	±10%

- (i) State the value of a resistor colour coded Brown, Grey, Red and Gold.

.....
 [3]

- (ii) State why resistors of different power ratings are available.

..... [1]

3 A multimeter is used to test electronic circuits.

(a) Name **four** other pieces of equipment that are used to test electronic circuits.

- 1
- 2
- 3
- 4

[4]

(b) (i) Describe **four** stages in using a multimeter to test for continuity in a fuse.

-
-
-
-
-
-
-
-
-
-

[4]

(ii) Give **two** other specific uses for a multimeter.

- 1
- 2

[2]

6 (a) Fig. 2 shows a linear integrated circuit (IC).

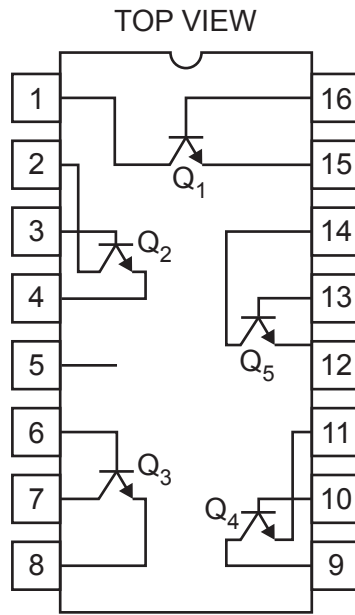


Fig. 2

- (i) State the name of the component shown at positions Q_1 to Q_5 in Fig. 2.
 [2]
- (ii) State the name that is given to the group of components arranged as shown in Fig. 2.
 [2]

(b) Draw a labelled diagram that shows the connections for a Darlington Pair.

[4]

END OF QUESTION PAPER

ADDITIONAL ANSWER SPACE

If additional space is required, you should use the following lined page(s). The question number(s) must be clearly shown in the margin(s).

A large rectangular area with a solid vertical line on the left side and horizontal dotted lines across the rest of the page, providing space for writing answers.



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series. If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.