



Oxford Cambridge and RSA

# Monday 17 January 2022 – Morning

## Level 3 Cambridge Technical in Engineering

### 05822/05823/05824/05825/05873 Unit 4: Principles of electrical and electronic engineering

**Time allowed: 1 hour 30 minutes**  
**C304/2201**



**You must have:**

- the Formula Booklet for Level 3 Cambridge Technical in Engineering (inside this document)
- a ruler (cm/mm)
- a scientific calculator



Please write clearly in black ink.

Centre number

Candidate number

First name(s) \_\_\_\_\_

Last name \_\_\_\_\_

Date of birth

### INSTRUCTIONS

- Use black ink. You can use an HB pencil, but only for graphs and diagrams.
- Write your answer to each question in the space provided. If you need extra space use the lined pages at the end of this booklet. The question numbers must be clearly shown.
- Answer **all** the questions.
- Where appropriate, your answer should be supported with working.
- Give your final answers to a degree of accuracy that is appropriate to the context.

### INFORMATION

- The total mark for this paper is **60**.
- The marks for each question are shown in brackets [ ].
- This document has **20** pages.


### ADVICE

- Read each question carefully before you start your answer.

FOR EXAMINER USE ONLY	
Question No	Mark
1	/9
2	/11
3	/9
4	/11
5	/10
6	/10
<b>Total</b>	<b>/60</b>

Answer **all** the questions.

- 1 The circuit diagram in **Fig. 1** shows a network of resistors.

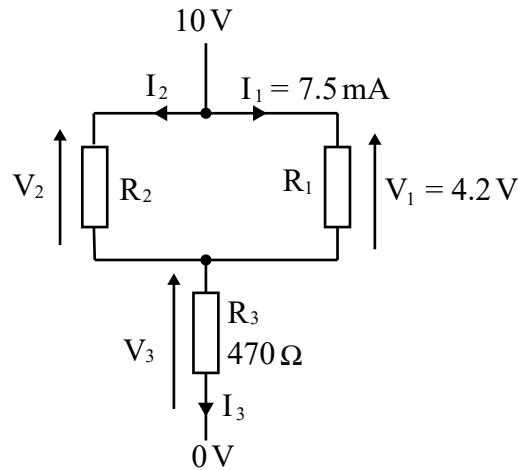

**Fig. 1**


- (a) A voltmeter is used to measure the voltage  $V_1$ .

- (i) Draw **on Fig. 1** to show how a voltmeter should be connected to measure the voltage  $V_1$ . [1]


- (ii) A multimeter is used as a voltmeter to measure the voltage  $V_1$ .

**Fig. 2a** shows a multimeter with the dial in the off position.

Draw an arrow **on Fig. 2b** showing the correct position of the dial to precisely measure the voltage  $V_1$ .

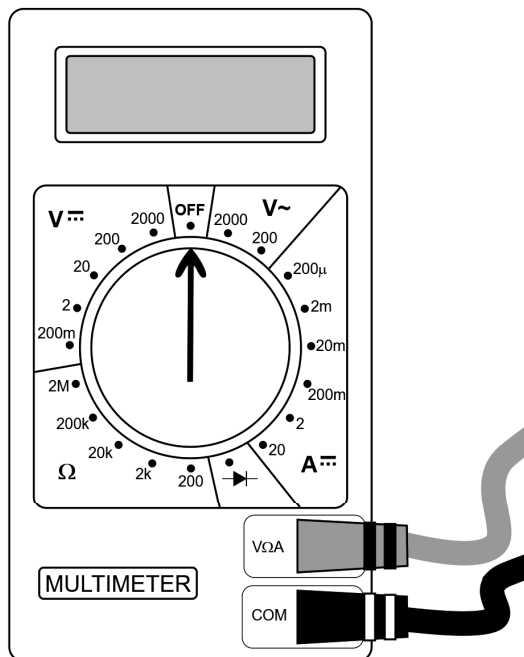

**Fig. 2a**

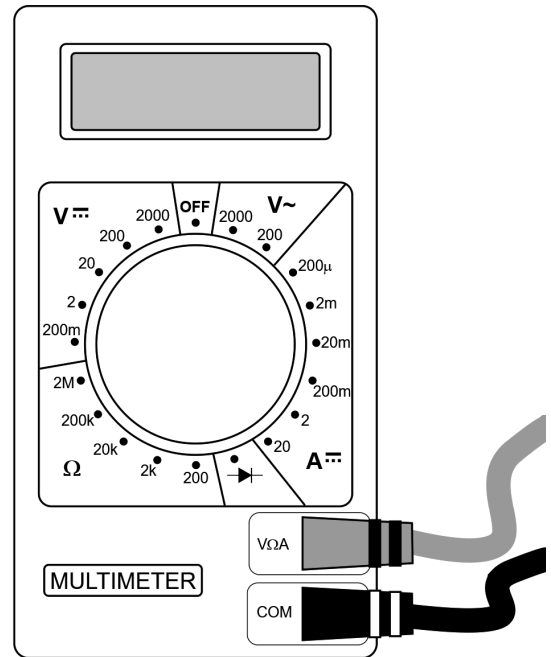

**Fig. 2b**

[1]

(b) Calculate the value of the resistor  $R_1$ .

$$R_1 = \dots\dots\dots \Omega \text{ [1]}$$

(c) Calculate the voltage  $V_3$ .

$$V_3 = \dots\dots\dots \text{ V [1]}$$

(d) Calculate the current  $I_3$ .

$$I_3 = \dots\dots\dots \text{ A [1]}$$

(e) Calculate the value of the resistor  $R_2$ .

$$R_2 = \dots\dots\dots \Omega \text{ [2]}$$

(f) Calculate the resistance of the network of resistors.

$$\text{resistance of the network of resistors} = \dots\dots\dots \Omega \text{ [2]}$$

- 2 (a) A sine wave alternating current (AC) supply of frequency  $f = 455$  kHz is connected in series with a resistor ( $R$ ), a capacitor ( $C$ ) and an inductor ( $L$ ).

(i) Draw a diagram of the circuit.

Label all components.

[2]

(ii) The value of inductor  $L = 240$   $\mu\text{H}$ .

Calculate the reactance  $X_L$  of the inductor when the frequency  $f = 455$  kHz.

$$X_L = \dots\dots\dots \Omega \text{ [3]}$$

(iii) The reactance of the capacitor  $X_C = 910$   $\Omega$  when the frequency  $f = 455$  kHz.

Calculate the value of the capacitor ( $C$ ).

Give the units for your answer.

$$C = \dots\dots\dots \text{ [3]}$$

(iv) The value of the resistor  $R = 330 \Omega$ .

Calculate the impedance ( $Z$ ) of the circuit at a frequency of 455 kHz.

$Z = \dots\dots\dots \Omega$  [2]


(v) Calculate the amplitude of the current in the circuit when it is supplied with a sine wave of amplitude 15 V at a frequency of 455 kHz.

Use the equation  $I = \frac{V}{Z}$

$I = \dots\dots\dots \text{A}$  [1]

3 An electric food mixer uses a shunt-wound DC motor.

- (a) Draw on **Fig. 3** to show how a field winding and armature should be connected to a 14.4 V power supply in a shunt-wound DC motor.

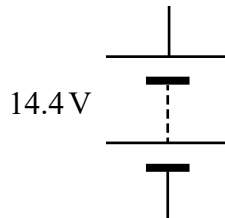

**Fig. 3**

[2]

- (b) Complete the sentences in the paragraph below by choosing the most appropriate words from the list.

Use each word once, more than once or not at all.

**constant**

**increased**

**infinite**

**reduced**

**zero**

A shunt-wound DC motor maintains a fairly constant speed regardless of load.

When the motor is running with no load, it spins at high speed.

When a load is applied to the motor, the speed reduces, and the EMF generated in the armature is .....

This means that the current in the armature is increased and so the torque is .....

The current in the field winding is .....

All of this keeps the load speed of the motor close to its no-load speed.

[3]

(c) The shunt-wound motor has a field winding resistance ( $R_f$ ) of  $48 \Omega$  and an armature winding resistance ( $R_a$ ) of  $18 \Omega$ .

(i) Calculate the current in the field winding ( $I_f$ ) when  $14.4 \text{ V}$  is supplied to the motor.

$$I_f = \dots\dots\dots \text{ A [1]}$$

(ii) The motor operates from a  $14.4 \text{ V}$  power supply ( $V$ ).

When the motor is turning at high speed, it produces a back EMF ( $E$ ) of  $12.2 \text{ V}$ .

Calculate the armature current ( $I_a$ ) in the motor.

Use the equation  $V = E + I_a R_a$

$$I_a = \dots\dots\dots \text{ A [2]}$$

(iii) Calculate the total current ( $I_t$ ) drawn from the power supply when the motor is turning at high speed.

$$I_t = \dots\dots\dots \text{ A [1]}$$

- 4 (a) The block diagram and circuit diagram for a power supply are shown in Fig. 4.

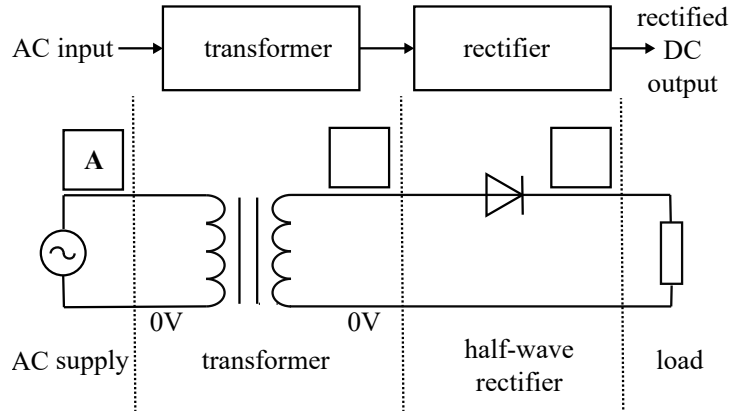


Fig. 4

Graphs A-E in Fig. 5 show how voltage can change over time.

In Fig. 4, the letter A indicates that **Graph A** shows the way that voltage changes over time at this point in the circuit.

Fill in the **two** blank boxes  in Fig. 4 to show which graph (B, C, D or E) represents the way that voltage changes over time at each point in the circuit.

[2]

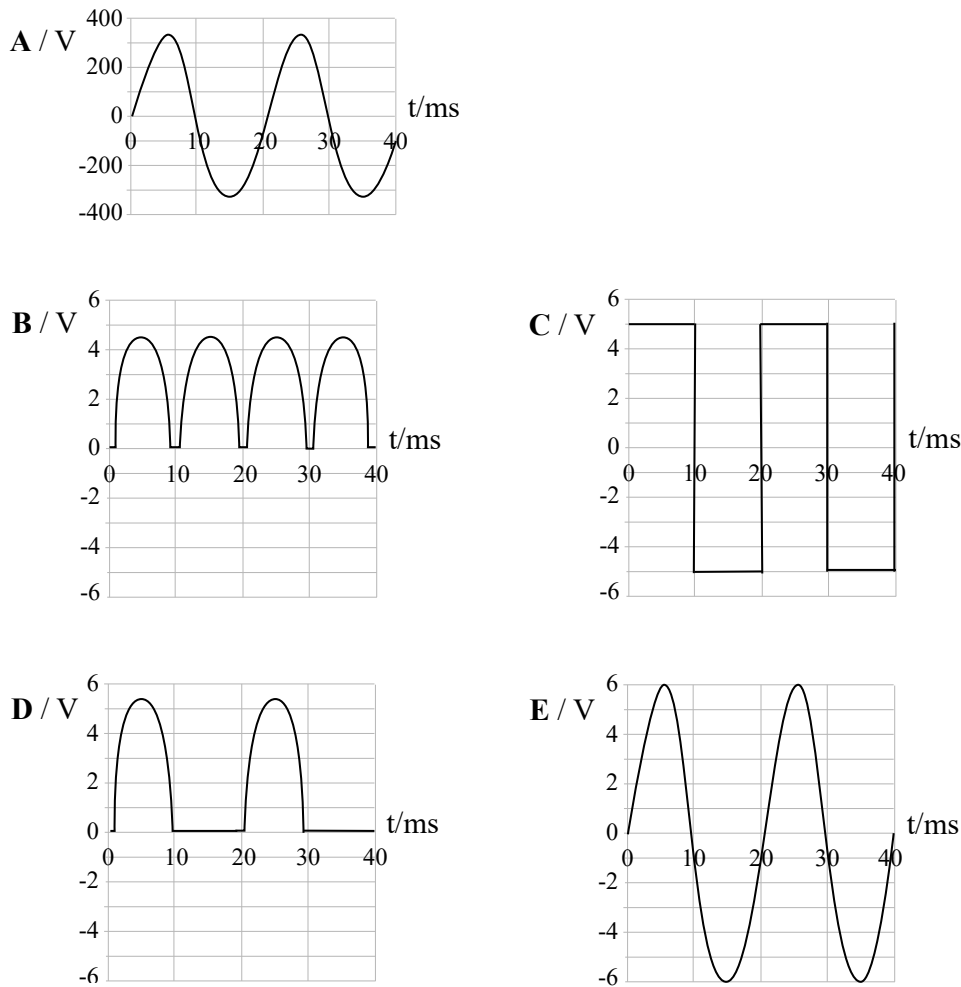


Fig. 5



(b) An incomplete block diagram of a stabilised power supply is shown in Fig. 6.

(i) Add the names of the **two** missing blocks to complete the stabilised power supply.

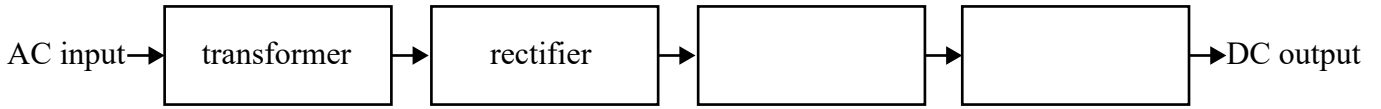


Fig. 6

[2]

(ii) A stabilised power supply has good load regulation.

Explain what is meant by good load regulation.

.....  
.....  
.....  
..... [2]

(c) An LED is used to show that the DC output of a 3.3 V power supply is operating.

(i) Complete Fig. 7 to show how an LED and current limiting resistor can be used to show that the power is operating.

Label the parts in your diagram.

+3.3 V —————

0 V —————

Fig. 7

[3]

(ii) Explain the function of the current limiting resistor in **Fig. 7**.

.....

.....

.....

..... [2]

- 5 (a) The table shows the input voltage ( $V_{in}$ ), output voltage ( $V_{out}$ ) and voltage gain of three different amplifiers.

Complete the table with the missing values.

Use the equation: Voltage Gain =  $\frac{V_{out}}{V_{in}}$

Input voltage ( $V_{in}$ )	Output voltage ( $V_{out}$ )	Voltage gain
3.0	1.5	
-2.5		3
	6	-1.5

[3]

- (b) Calculate the resistors for a non-inverting operational amplifier, constructed from an operational amplifier (op-amp) with a voltage gain of 1.5.


Use the equation: Voltage Gain =  $1 + \frac{R_F}{R_2}$

$$R_F = \dots\dots\dots \text{k}\Omega$$

$$R_2 = \dots\dots\dots \text{k}\Omega$$

[2]


- (c) Complete **Fig. 8** to show a non-inverting amplifier.  
Label the input, output,  $R_F$  and  $R_2$ .

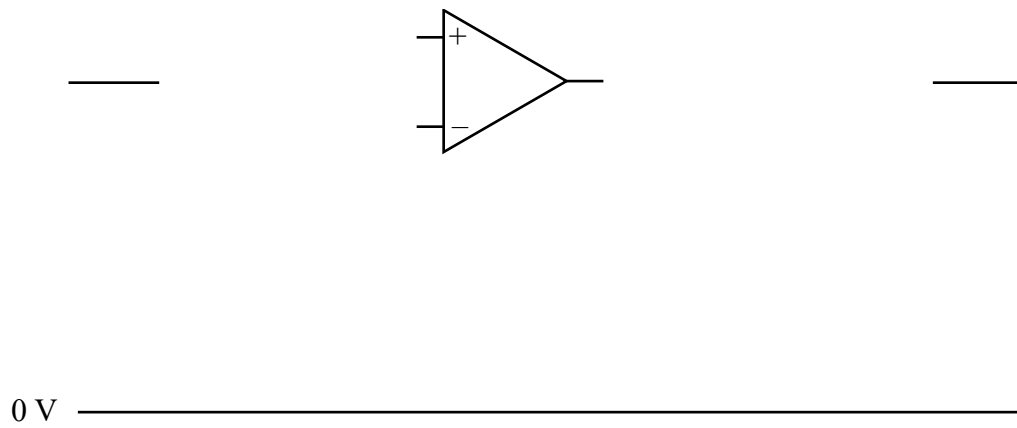

**Fig. 8**

[5]

- 6 (a) The circuit symbol for a T-type flip-flop is shown in **Fig. 9**.

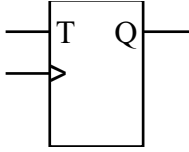

**Fig. 9**

Draw a line to join the start of each sentence to the most appropriate end of sentence about the behaviour of a T-type flip-flop.

There will be some end of sentences without a connecting line.

**Start of sentence**

**End of sentence**

When a T-type flip-flop is triggered and T is low, ...

...Q changes.

...Q stays the same.

...T changes.

When a T-type flip-flop is triggered and T is high, ...

...the clock is  $\bar{T}$ .

[2]

**Question 6(b) begins on page 14**

(b) A partially complete truth table for a logic gate is shown below.

<b>A</b>	<b>B</b>	<b>Q</b>
0	0	1
		0
		0
		0

(i) Complete the truth table by filling in columns **A** and **B**.

[1]

(ii) Name the logic gate described by the truth table.

..... [1]

(iii) Draw the circuit symbol for the logic gate described by the truth table.

Label the inputs **A** and **B** and label the output **Q**.

[1]

(iv) Put a **ring** around the correct Boolean expression for the logic gate described by the truth table.

$$Q = A + B \quad Q = \overline{A + B} \quad Q = A \cdot B \quad Q = \overline{A \cdot B} \quad Q = A \oplus B$$

[1]

(c) Fig. 10 shows a logic gate circuit.

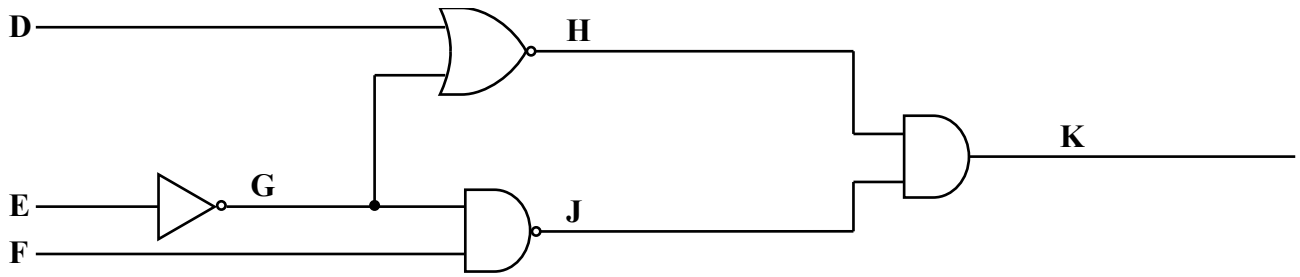


Fig. 10

Complete the truth table for this circuit.

D	E	F	G	H	J	K
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

[4]

**END OF QUESTION PAPER**

**ADDITIONAL ANSWER SPACE**

If additional answer space is required, you should use the following lined pages. The question numbers must be clearly shown – for example, 1(d) or 6(c).

A vertical line on the left side of the page is followed by 25 horizontal dotted lines, providing a ruled area for writing answers.



A series of horizontal dotted lines for writing, spanning the width of the page.

A series of horizontal dotted lines for writing, spanning the width of the page.

A series of horizontal dotted lines for writing, spanning the width of the page. A solid vertical line is positioned on the left side of the page, serving as a margin.



Oxford Cambridge and RSA

Copyright Information:

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website ([www.ocr.org.uk](http://www.ocr.org.uk)) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, OCR (Oxford Cambridge and RSA Examinations), The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.