



Oxford Cambridge and RSA

Tuesday 10 January 2023 – Afternoon

Level 1/2 Cambridge National in Systems Control in Engineering

R113/01 Electronic principles

Time allowed: 1 hour



You must have:

- a scientific or graphical calculator



Please write clearly in black ink. **Do not write in the barcodes.**

Centre number

--	--	--	--	--

Candidate number

--	--	--	--

First name(s)

Last name

INSTRUCTIONS

- Use black ink. You can use an HB pencil, but only for graphs and diagrams.
- Write your answer to each question in the space provided. If you need extra space use the lined page at the end of this booklet. The question numbers must be clearly shown.
- Answer **all** the questions.

INFORMATION

- The total mark for this paper is **60**.
- The marks for each question are shown in brackets [].
- Quality of written communication will be assessed in questions marked with an asterisk (*).
- This document has **8** pages.


ADVICE

- Read each question carefully before you start your answer.

Answer **all** the questions.

1 **Fig. 1** shows a partly completed circuit diagram.

Fig. 1

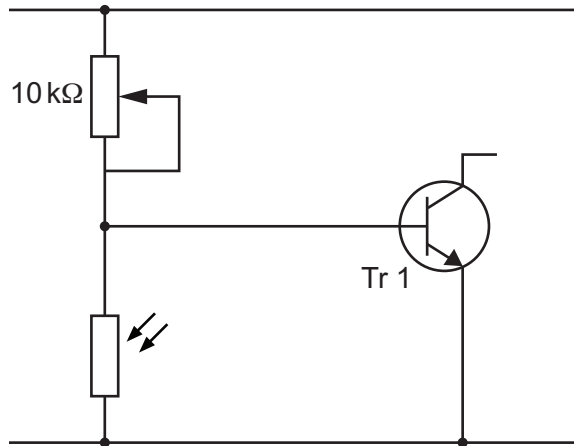

(a) Complete the circuit diagram in **Fig. 1** by adding:


- a light emitting diode (LED) connected to Tr1
- a current limiting resistor for the LED
- +9V and 0V labels for the power supply rails.

[6]

(b) **Fig. 2** shows a switch being used to control the direction of rotation of a motor.

Complete the name of the switch type shown in **Fig. 2** that is being used to control the motor.

Fig. 2

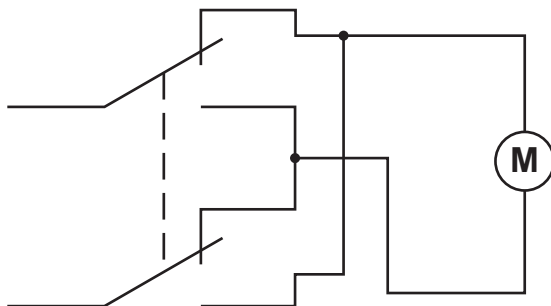

Double Pole Double

[1]

(c) Calculate the total resistance of three resistors, each of value 10Ω , connected in series.

Total resistance

.....

..... [3]

- 2 (a) State how you would identify the difference between a polarised capacitor and a non polarised capacitor when making a connection in a circuit.

.....

 [2]

- (b) A capacitor colour code chart to give values in pF is shown in **Table 1** below.

Table 1

Band 1	Band 2	Band 3	Band 4
Black 0	Black 0	Black 0	Black $\pm 20\%$
Brown 1	Brown 1	Brown 1	Brown $\pm 1\%$
Red 2	Red 2	Red 2	Red $\pm 2\%$
Orange 3	Orange 3	Orange 3	Gold $\pm 5\%$
Yellow 4	Yellow 4	Yellow 4	Silver $\pm 10\%$
Green 5	Green 5	Green 5	
Blue 6	Blue 6	Blue 6	
Violet 7	Violet 7		
Grey 8	Grey 8		
White 9	White 9		

- (i) Write down the value of a capacitor colour coded Red, Brown, Orange and Gold. Gold has been completed for you.

Red indicates

Brown indicates

Orange indicates

Gold indicates $\pm 5\%$

The capacitor value is pF \pm [4]

- (ii) Calculate the **minimum** and **maximum** value of a 200 pF $\pm 5\%$ capacitor.

Minimum value

.....

Maximum value


.....

[4]

Turn over

3 Fig. 3 is a block diagram of a control system.

Fig. 3

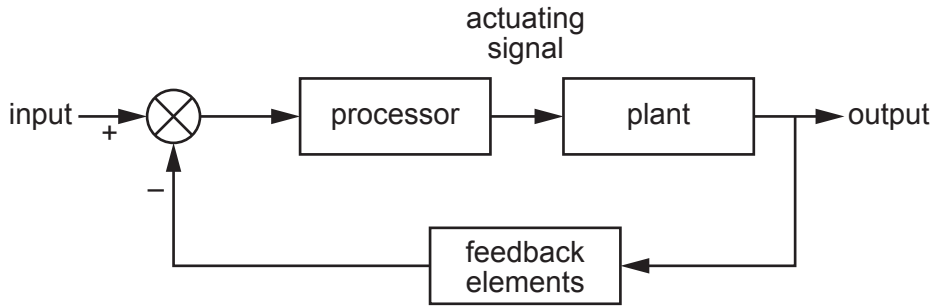

(a) State the type of control loop being used in the diagram shown in Fig. 3.
 [1]

(b) State the purpose of input, output, processor and feedback elements in the system.
 (i) Input [1]

(ii) Output [1]

(iii) Processor [2]

(iv) Feedback elements [2]

(c) Calculate the potential difference across a lamp if its resistance is $40\ \Omega$ and the current flow is 0.3A .
 V [3]

4 (a)* Visual inspection is a technique used to identify potential electrical hazards in electronic circuits.

Discuss the **two** other techniques shown below that are used to identify hazards in electronic circuits:

- portable appliance testing (PAT) compliance
- use of residual current device (RCD).

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

[6]


(b) List **four** items of electrical test equipment.

- 1
- 2
- 3
- 4

[4]

5 Fig. 4 shows **six** logic gate symbols and **six** names of logic gates.

Fig. 4

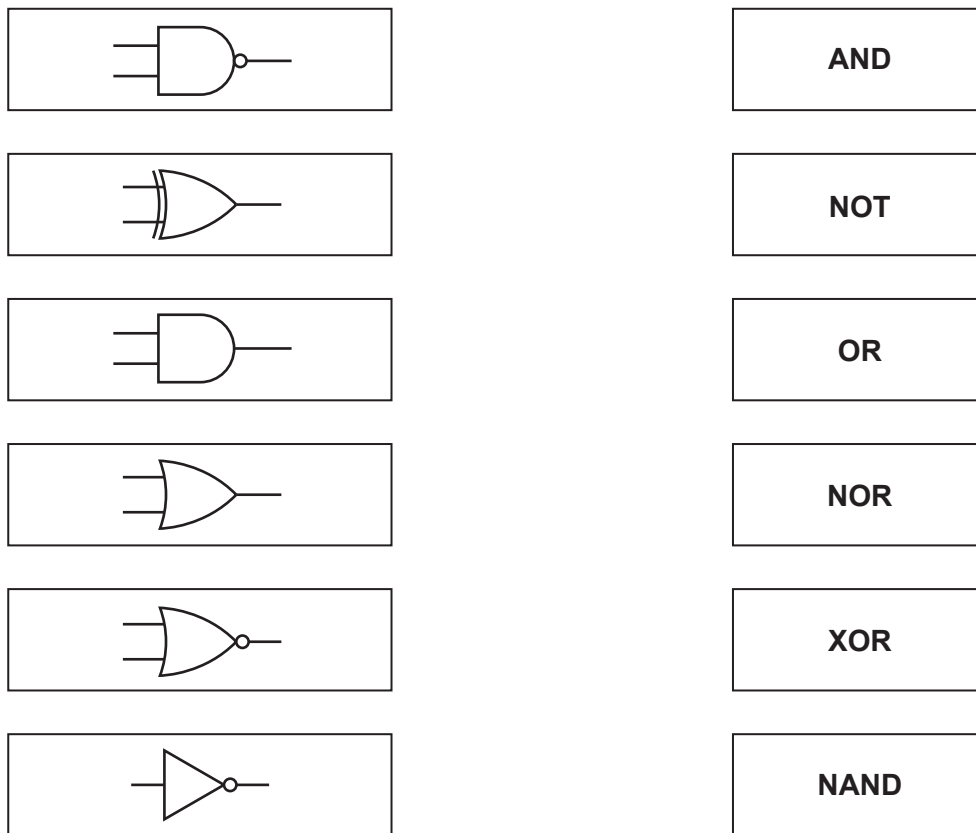

(a) Draw a line between each logic gate symbol and its name.

[5]

(b) Complete the truth table below for each of the **two** input gates listed.

Input A	Input B	AND gate output	OR gate output	NOR gate output	XOR gate output	NAND gate output
0	0					
0	1					
1	0					
1	1					

[5]

6 (a) Name **three** manufacturing processes that are used within commercial circuit construction.

1

2

3

[3]

(b) Quality assurance methods are used to check a commercially produced printed circuit board (PCB) with components installed and soldered.

List **five** faults that could be found on a circuit board during a visual inspection.

1

.....

2

.....

3

.....

4

.....

5

.....

[5]

(c) Complete the **two** missing values of the preferred E12 resistor series shown below.

	12	15	18	22	27	33		47	56	68	82
--	----	----	----	----	----	----	--	----	----	----	----

[2]

END OF QUESTION PAPER

ADDITIONAL ANSWER SPACE

If additional space is required, you should use the following lined page(s). The question number(s) must be clearly shown in the margin(s).

A large rectangular area with a vertical solid line on the left side and horizontal dotted lines across the rest of the page, providing space for writing answers.



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of Cambridge University Press & Assessment, which is itself a department of the University of Cambridge.