

Modified Enlarged 18pt

OXFORD CAMBRIDGE AND RSA EXAMINATIONS

Wednesday 21 May 2025 – Morning

Level 3 Cambridge Technical in Engineering

05822/05823/05824/05825/05873

Unit 4: Principles of electrical and electronic engineering

**Time allowed: 1 hour 30 minutes
plus your additional time allowance**

YOU MUST HAVE:

**the Formula Booklet for Level 3 Cambridge Technical in
Engineering (with this document)**

a ruler (cm/mm)

a scientific calculator

Please write clearly in black ink.

Centre number

--	--	--	--	--

Candidate number

--	--	--	--

First name(s)

Last name

Date of birth

D	D	M	M	Y	Y	Y	Y
---	---	---	---	---	---	---	---

READ INSTRUCTIONS OVERLEAF



INSTRUCTIONS

Use black ink. You can use an HB pencil, but only for graphs and diagrams.

Write your answer to each question in the space provided. If you need extra space use the lined pages at the end of this booklet. The question numbers must be clearly shown.

Answer ALL the questions.

Where appropriate, your answer should be supported with working.

Give your final answers to a degree of accuracy that is appropriate to the context.

INFORMATION

The total mark for this paper is 60.

The marks for each question are shown in brackets [].


ADVICE

Read each question carefully before you start your answer.

BLANK PAGE

1 A student takes measurements on a battery.

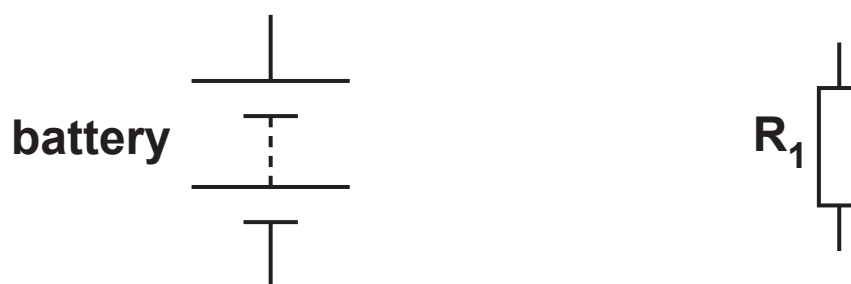- (a) The battery provides current to resistor R_1 .
An ammeter measures current through the resistor.
Complete the diagram below by adding a symbol for the ammeter and the connections needed to measure current through resistor R_1 . [2]



- (b) The ammeter shows a current of 34 mA when a $220\ \Omega$ resistor is used.
- (i) Calculate the voltage across the $220\ \Omega$ resistor.

voltage across $220\ \Omega$ resistor = _____ V [2]

(ii) Calculate the power dissipated in the 220Ω resistor.

power dissipated in the
 220Ω resistor = _____ W [1]

(c) The student changes the value of the resistor in the circuit and takes some more measurements.

(i) Complete the table of results below by calculating the missing values in the last THREE rows.

resistor value/ Ω	current /mA	voltage across resistor/V	power dissipated in resistor/W
22	132	2.9	0.39
33	114	3.8	0.43
47	97	4.5	0.44
68		5.4	0.42
100	62		0.38
150	46	6.9	

[3]

- (ii) The student was told that the internal resistance of the battery should be about $47\ \Omega$. Explain how the student's results support what they were told about the battery.

[2]

2 A student investigates a circuit with an inductor, capacitor and resistor in series with an AC supply.

(a) Complete the circuit diagram to show how the inductor, capacitor and resistor should be connected to the AC supply. [4]



(b) The student uses an inductor of value $L = 220 \mu\text{H}$.

Calculate the reactance of the inductor, X_L , when the frequency of the AC supply is $f = 350 \text{ Hz}$.

$$X_L = \text{_____} \Omega \text{ [2]}$$

- (c) The student investigates the effect of changing the frequency, f , of the AC supply on the phase angle, ϕ , between the voltage and current from the AC supply.

The values of the resistor, capacitor and inductor are as follows:

$$R = 3.3 \Omega$$




$$C = 3.2 \times 10^{-4} \text{ F}$$

$$L = 220 \mu\text{H}$$

Calculate the missing values to complete the table opposite.

Include the units for your phase angles.

[4]

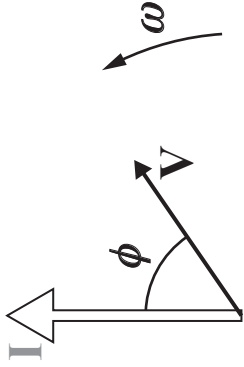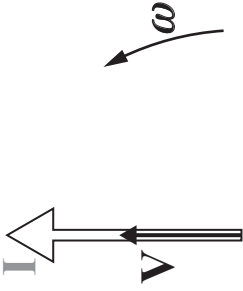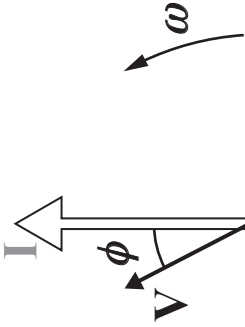frequency f/Hz	reactance of inductor X_L/Ω	reactance of capacitor X_C/Ω	impedance of series RLC circuit Z/Ω	phase angle ϕ	phasor diagram
100	0.14	5.0	5.9		
600	0.83	0.83		0°	
1450	2.0		3.7		

- 3 A series-wound DC motor is used to drive an electric scooter.**
- (a) The scooter uses a 24 V battery to supply electricity to the motor.**

The armature has a resistance of $6.0\ \Omega$ and a field coil resistance of $0.5\ \Omega$.

When the scooter is travelling at 15 mph the EMF generated in the armature, $E = 19\text{ V}$.

Use the equation for the DC series-wound motor to calculate the armature current, I_a .

$$I_a = \underline{\hspace{2cm}} \text{ A [3]}$$

- (b) The instructions for the scooter contain a warning that the motor should not be connected to the battery when the wheels are not in contact with the ground.**

Explain the reason for the warning in the instructions by referring to the behaviour of a series-wound DC motor.

[2]


- (c) When users want to slow down the scooter, they operate a switch that disconnects the battery and connects the motor to a resistor.

The motor then behaves as a series-wound self-excited DC generator.

- (i) Explain the difference between a motor and a generator.

[2]

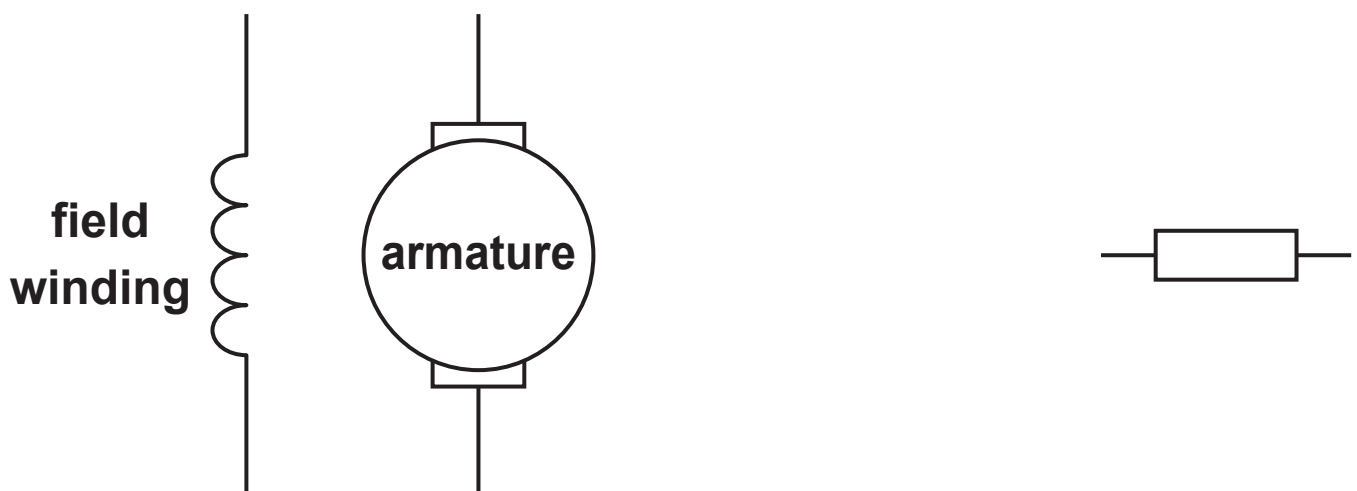- (ii) Complete the diagram to show how the armature and field winding of the series-wound self-excited DC generator should be connected to the resistor. [1]



(iii) Complete the sentences to explain how the series-wound DC generator is used to slow down the scooter.

Choose words from the following list.

Each word may be used once, more than once or not at all.

decreases increases maintains oscillates

Connecting the resistor to the generator causes a large current to flow through the field winding, which _____ the EMF generated in the armature and the voltage from the generator causing heating of the resistor. This _____ the torque required to turn the generator and decreases the speed of the scooter. [2]

BLANK PAGE

- 4 A farm is supplied with electricity using a single phase 3-wire system.


The electricity supply has a neutral wire, N, and two live wires, L_1 and L_2 .

The voltage between a live wire and the neutral wire is 230 VAC.



One of the live wires is used to supply 230 VAC electricity to the farmhouse where the people live.

The other live wire is used to supply 230 VAC electricity to the storage shed for fridges that keep the produce fresh.

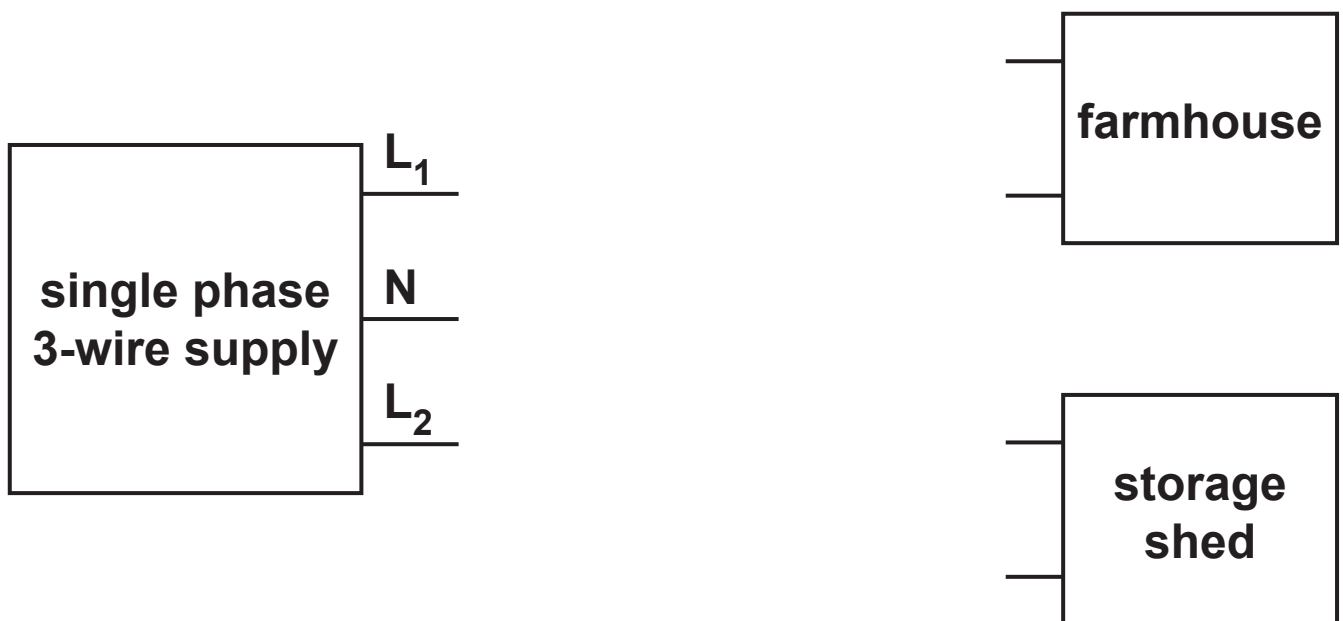- (a) Show how L_1 , L_2 and N should be connected to the farmhouse and to the storage shed. [2]



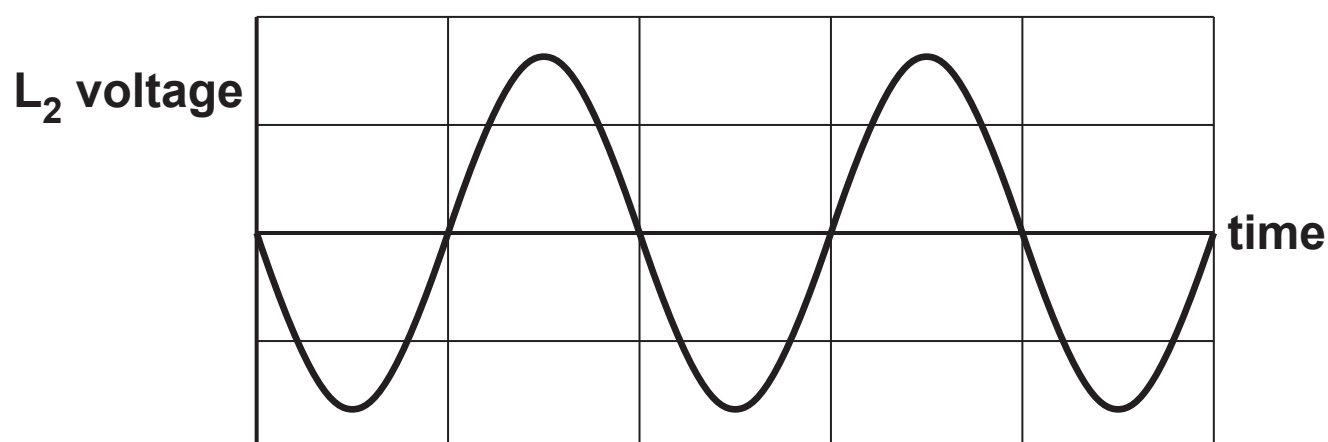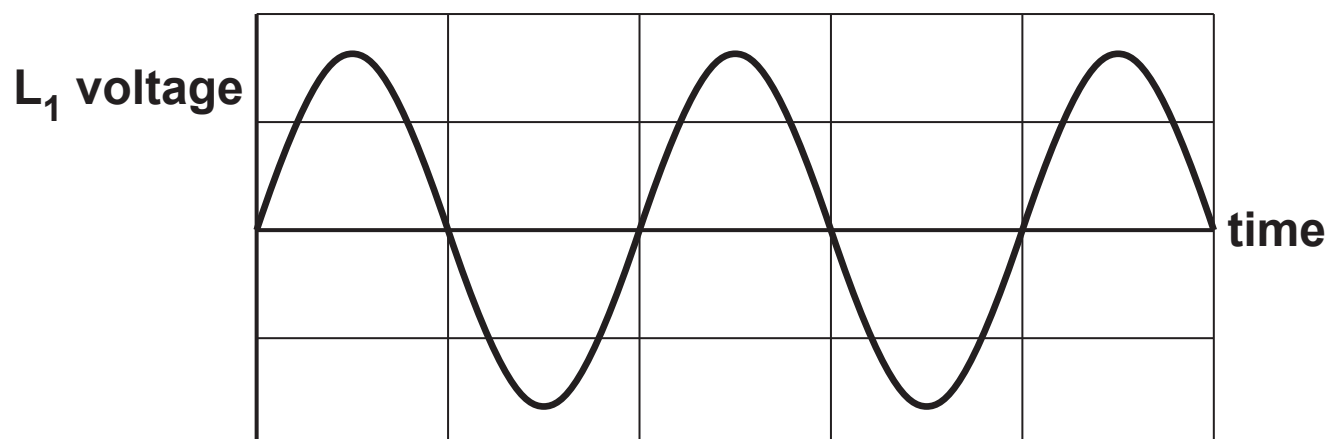(b) The graphs below show how the voltages of L_1 and L_2 vary with time.



State the phase difference between L_1 and L_2 .

_____ [1]

- (c) The fridges and power supply are protected by a circuit breaker.**

Explain how the circuit breaker protects the power supply and fridges.

[2]

- (d) The fridges are controlled by an electronic circuit that operates from 5VDC.**

Complete the block diagram opposite of a stabilized power supply for the electronic circuit.

Choose from the terms below. [5]

DC output


rectifier

smoothing
circuit

stabilising
circuit

star

transformer

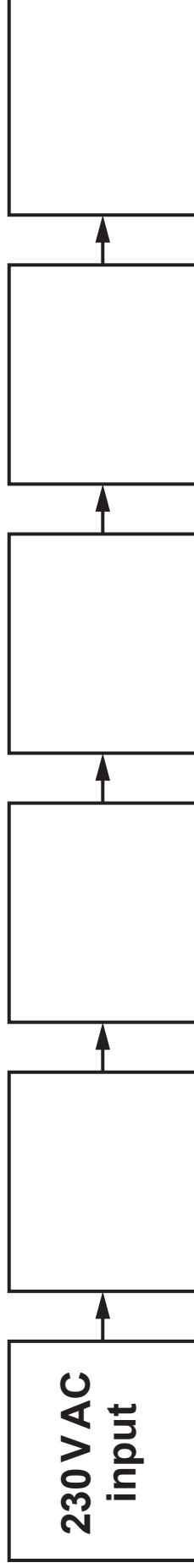

- 5 An engineer is building an op-amp inverting amplifier to amplify the signal from a force sensor.

The op-amp inverting amplifier has a voltage gain of -20 .

The equation of the amplifier is given by:

$$\text{Voltage Gain} = \frac{V_{\text{out}}}{V_{\text{in}}} = -\frac{R_{\text{F}}}{R_{\text{in}}}$$

- (a) The input voltage of the amplifier, $V_{\text{in}} = 160 \text{ mV}$.

Calculate the output voltage of the amplifier, V_{out} .

$$V_{\text{out}} = \underline{\hspace{2cm}} \text{ V [3]}$$

(b) The engineer uses a feedback resistor, $R_F = 100 \text{ k}\Omega$.

Calculate the value of the input resistor, R_{in} , in ohms.



$$R_{in} = \text{_____} \Omega [2]$$

(c) Complete the circuit diagram opposite of the op-amp inverting amplifier.

Show the connections to the force sensor and the output.

Label the resistors R_F and R_{in} . [5]


— output

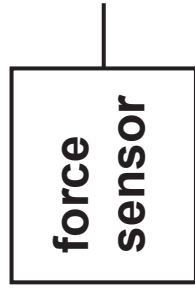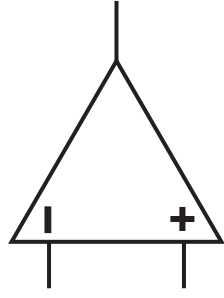

0V —

6



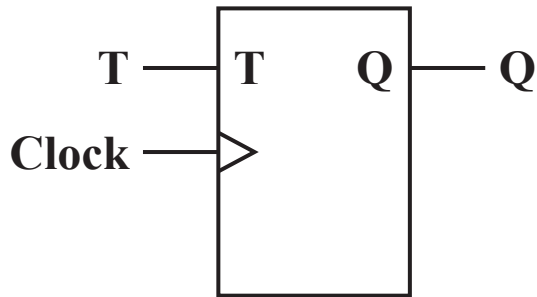
- (a) The circuit symbol for a rising edge triggered T-type flip-flop is shown below.



A timing diagram shows how the logic levels at T, Clock and Q vary with time.

The T and Clock signals have been completed; Q starts at logic 1.

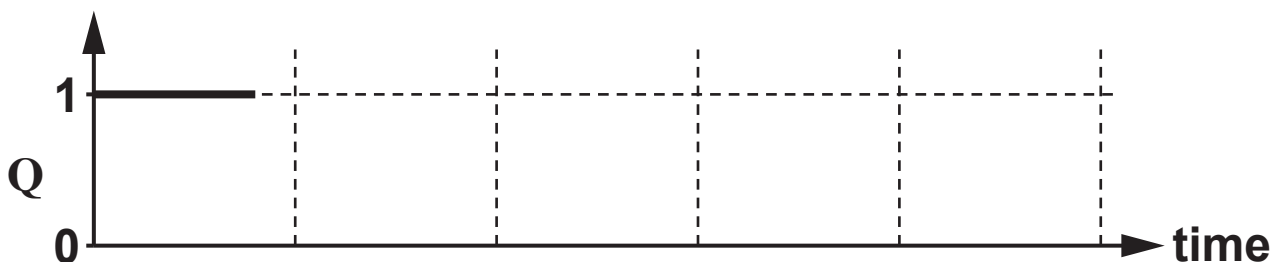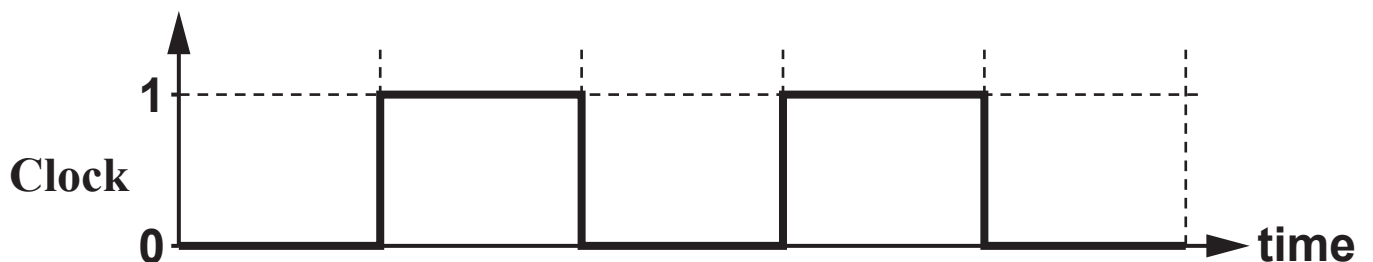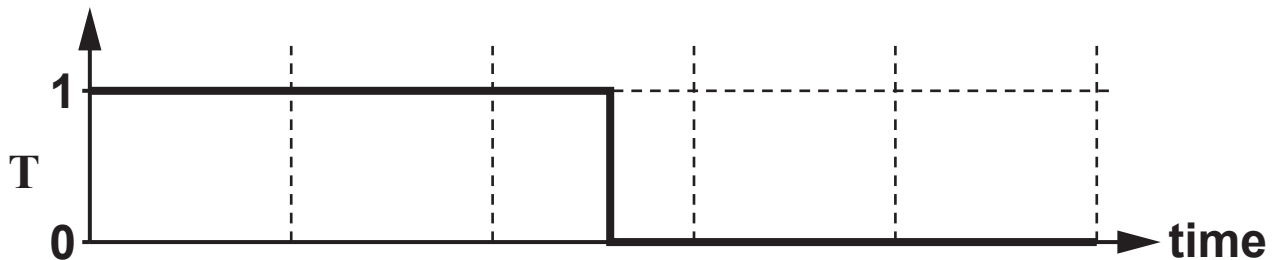Complete the timing diagram below to show how Q varies with time. [2]



- (b) An OR gate with output Q and inputs A and B is used in a circuit.
- (i) Draw the circuit symbol for an OR gate. Use the space below. [1]

- (ii) Complete the truth table for an OR gate. [2]

A	B	Q

- (iii) Which of the following is the correct Boolean expression for an OR gate? [1]

Tick (✓) ONE box.

$$Q = A \cdot B$$

☐

$$Q = A + B$$

☐


$$Q = A \oplus B$$

☐

$$Q = \overline{A \cdot B}$$

☐

(c) A logic circuit is shown below.

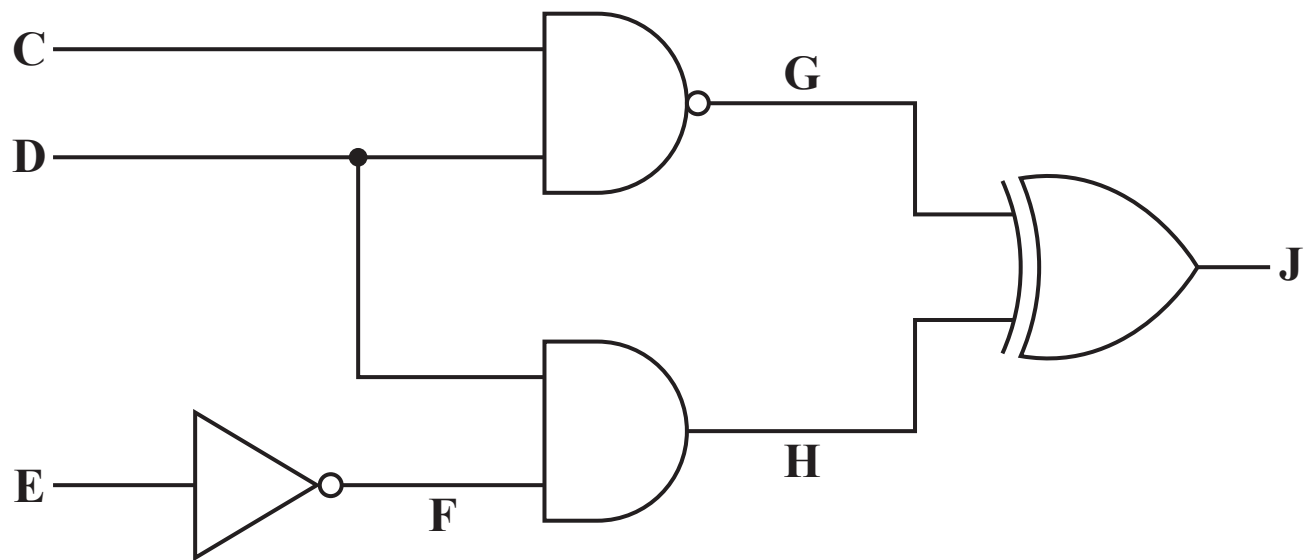

Complete the truth table for the logic circuit. [4]

C	D	E	F	G	H	J
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

END OF QUESTION PAPER

EXTRA ANSWER SPACE

If you need extra space use these lined pages. You must write the question numbers clearly in the margin.



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of Cambridge University Press & Assessment, which is itself a department of the University of Cambridge.