

OCR

Oxford Cambridge and RSA

Monday 23 May 2016 – Morning

PRINCIPAL LEARNING LEVEL 3 ENGINEERING

F559/01 Instrumentation and Control Engineering

Candidates answer on the Question Paper.


OCR supplied materials:

None

Other materials required:

- Scientific calculator

Duration: 2 hours

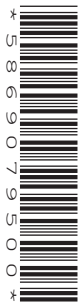

Candidate forename		Candidate surname	
-----------------------	--	----------------------	--


Centre number						Candidate number				
---------------	--	--	--	--	--	------------------	--	--	--	--

INSTRUCTIONS TO CANDIDATES

- Write your name, centre number and candidate number in the boxes above. Please write clearly and in capital letters.
- Use black ink. HB pencil may be used for graphs and diagrams only.
- Answer **all** the questions in **Section A** and any **four** questions from **Section B**.
- Read each question carefully. Make sure you know what you have to do before starting your answer.
- Write your answer to each question in the space provided. Additional paper may be used if necessary but you must clearly show your candidate number, centre number and question number(s).
- Do **not** write in the bar codes.

INFORMATION FOR CANDIDATES

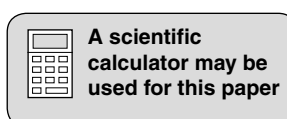- The number of marks is given in brackets [] at the end of each question or part question.
- The total number of marks for this paper is **60**.
- This document consists of **16** pages. Any blank pages are indicated.



SECTION A

Answer **all** questions in the spaces provided.

1 State **two** characteristics of a closed loop control system.

1

.....

2

.....

[2]

2 Calculate the open loop voltage gain for a system with an input of 100 volts and an output of 10 volts.

.....

..... [2]

3 Draw a diagram to represent an analogue signal and a digital signal.

Analogue Signal

Digital Signal

[2]

4 Fig. 1 shows a circuit diagram using an operational amplifier.

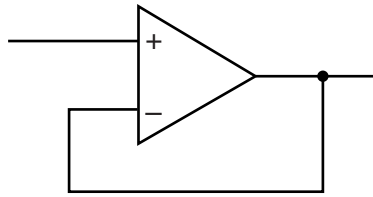


Fig. 1



Label the input terminal and state the name given to this type of circuit.

..... [2]

5 Explain what a thermistor is.

.....
.....
.....
..... [2]

6 Complete the table by naming each component or by drawing its graphical symbol.

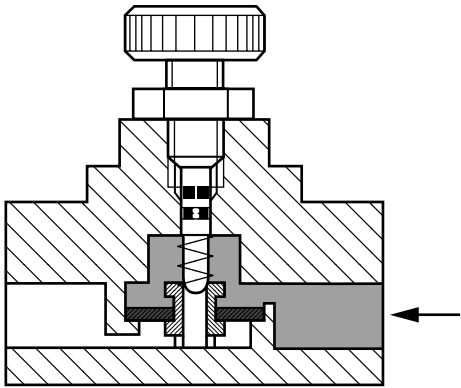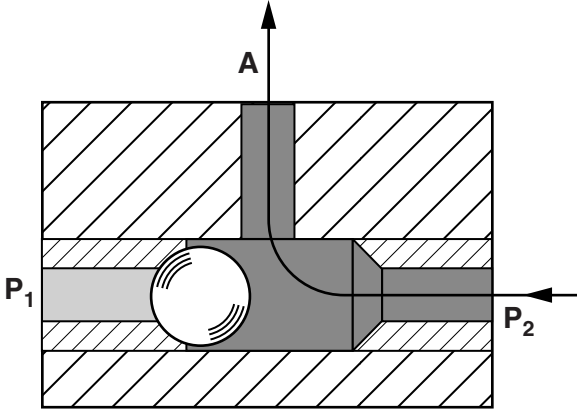Component cross sectional view	Name of Component or Graphical Symbol
	
	

[2]

7 Name **two** types of level sensors that can provide a feedback signal in a control system.

1

2

[2]

8 Define the term 'reliability' when referring to an embedded system.

.....

.....

..... [2]

9 Explain the purpose of a signal generator.

.....
.....
..... [2]

10 Explain why a multiplexer is used.

.....
.....
.....
..... [2]

[Total: 20]

SECTION B

Answer any **four** questions in the spaces provided.

- 1 (a) Fig. 2 shows a block diagram of a home central heating control system.

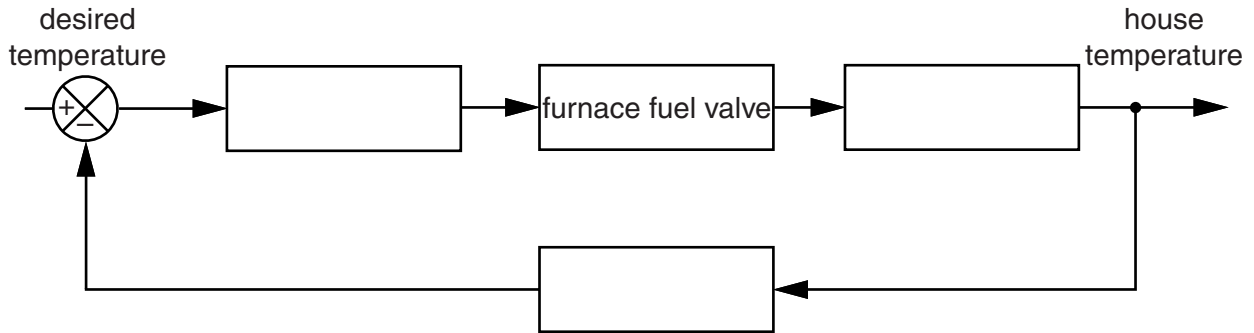


Fig. 2

- (i) Name the type of control system shown in Fig. 2.

..... [1]

- (ii) Label the block diagram with the terms:

- Feedback
- Thermostat Controller
- Home Heating Processor
- Error detector
- Output

[5]

- (b) Draw a labelled block diagram for a measurement system showing the following features:

- Input
- Display
- Signal processor

[4]

[Total: 10]

2 (a) Explain what is meant by the following terms giving **one** example of each:

Open loop control
.....
..... [2]

Closed loop control
.....
..... [2]


Negative feedback
.....
..... [2]

(b) Name **four** computer input devices.


- 1
- 2
- 3
- 4 [4]

[Total: 10]

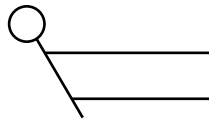
3 (a) Name the manually operated pneumatic components shown below in Fig. 3.



1

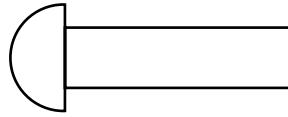

2

 

3

Fig. 3

[3]

(b) Fig. 4 shows a memory function circuit system.

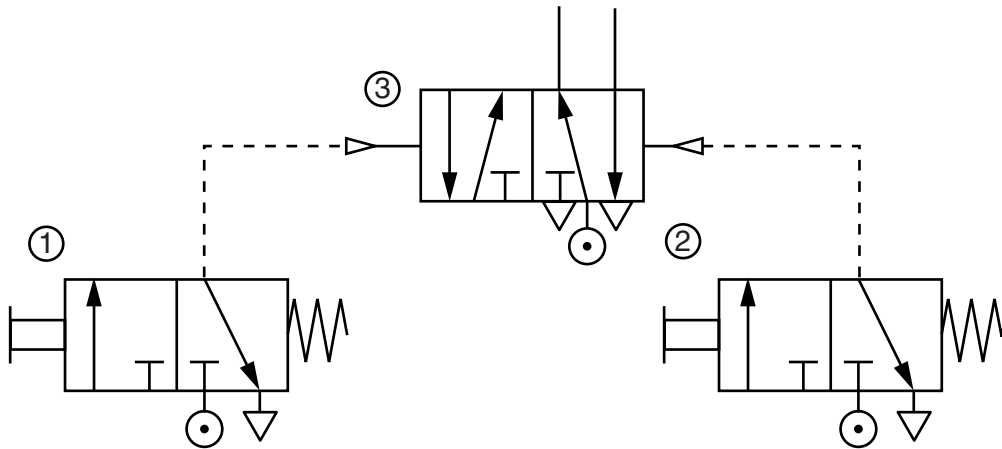


Fig. 4

(i) Name the type of control valve that is being used at position 3 in this system.

..... [1]

(ii) Explain how this circuit works.

.....

.....

.....

.....

.....

.....

.....

..... [6]

[Total: 10]

4 (a) Explain with the aid of a labelled diagram the construction and action of a Bourdon tube.

.....

.....

.....

.....

.....

.....

.....

..... [5]

(b) State why Bourdon tubes are often used in harsh environments.

.....

..... [1]

(c) State **four** effects of over-pressurising a Bourdon tube in a working environment.

1

2

3

4

[4]

[Total: 10]

5 Fig. 5 shows an orifice plate in a pipe.

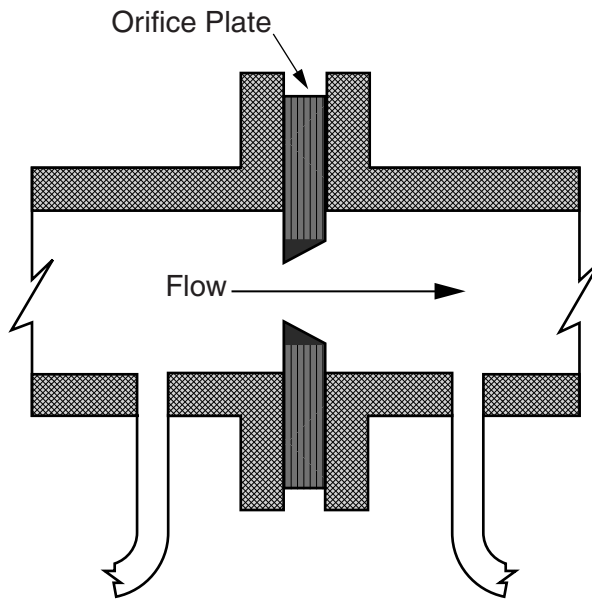


Fig. 5

(a) Explain how an orifice plate is used as a 'Flow Detector' as shown in Fig. 5.

.....
.....
.....
.....
.....
.....
.....
..... [6]

(b) State **two** advantages of using an orifice plate as a flow detector.

1
2 [2]

(c) State **two** alternative methods of measuring fluid flow.

1
2 [2]

[Total: 10]

Turn over

6 Fig. 6 shows part of a circuit diagram.

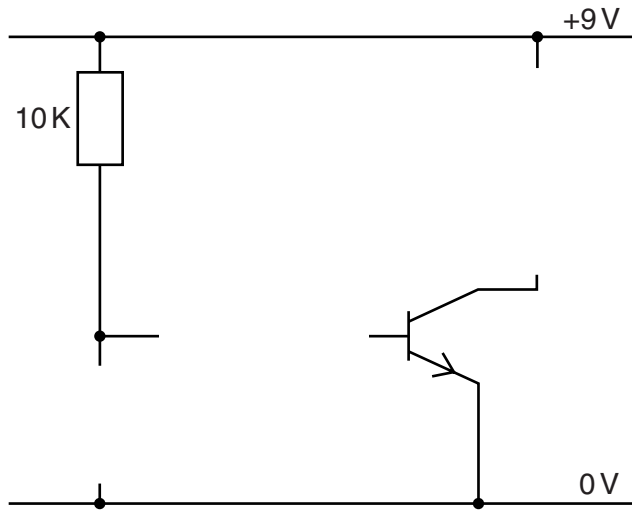


Fig. 6

(a) Name the type of transistor that is being used in the partly completed circuit.

..... [1]

(b) Complete the circuit diagram by adding the following component symbols to Fig. 6.

- a base resistor
- a light-dependent resistor (LDR) as an input device
- a signal lamp as an output device.

[3]

(c) Describe how the completed circuit would work.

.....

 [5]

(d) Name one practical application that uses this type of circuit.

..... [1]

[Total: 10]

7 (a) Explain what is meant by each of the following terms relating to hardware in embedded systems:

Processor

.....
.....
..... [2]

Memory

.....
.....
..... [2]

User Interface

.....
.....
..... [2]

Displays

.....
.....
..... [2]

(b) Give **two** benefits of an embedded system over a Programmable Logic Controller (PLC).

.....
.....
..... [2]

[Total: 10]

8 Fig. 7 shows a computer package being used to display a circuit diagram as a virtual image.

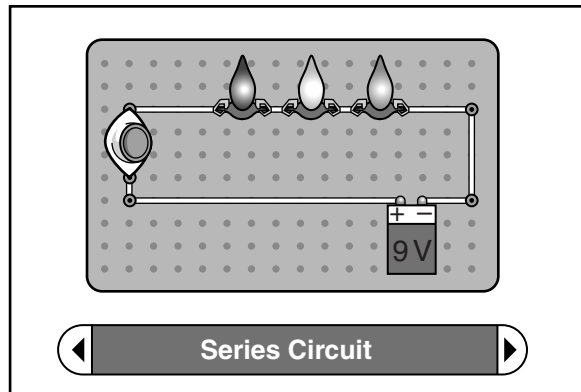


Fig. 7

(a) State **three** benefits of using a simulation software package rather than making the circuit with real components.

- 1
- 2
- 3 [3]

(b) Draw a labelled circuit diagram, using circuit symbols, from the information given in Fig. 7. Also include in the circuit diagram:

- a voltmeter to measure the potential difference of any one signal lamp
- a voltmeter to measure the total potential difference
- an ammeter to measure the total current.

[7]

[Total: 10]

END OF QUESTION PAPER

15
BLANK PAGE

PLEASE DO NOT WRITE ON THIS PAGE

PLEASE DO NOT WRITE ON THIS PAGE



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.