

**PRINCIPAL LEARNING  
LEVEL 3**

**ENGINEERING**

Instrumentation and Control Engineering

**F559**

**Thursday 13 January 2011  
Morning**

**Duration: 2 hours**

Candidates answer on the question paper.

**OCR supplied materials:**

None

**Other materials required:**

- Scientific calculator



Candidate forename		Candidate surname	
--------------------	--	-------------------	--


Centre number							Candidate number				
---------------	--	--	--	--	--	--	------------------	--	--	--	--

**INSTRUCTIONS TO CANDIDATES**

- Write your name, centre number and candidate number in the boxes above. Please write clearly and in capital letters.
- Use black ink. Pencil may be used for graphs and diagrams only.
- Read each question carefully. Make sure you know what you have to do before starting your answer.
- Write your answer to each question in the space provided. Additional paper may be used if necessary but you must clearly show your candidate number, centre number and question number(s).
- Answer **all** the questions in **Section A** and any **four** questions from **Section B**.
- Do **not** write in the bar codes.

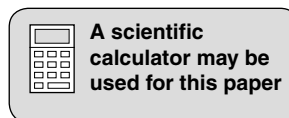**INFORMATION FOR CANDIDATES**

- The number of marks is given in brackets [ ] at the end of each question or part question.
- The total number of marks for this paper is **60**.
- This document consists of **12** pages. Any blank pages are indicated.



Section A

Answer **all** questions in the spaces provided.

1 The block diagram in Fig. 1 shows the layout of a central heating system.

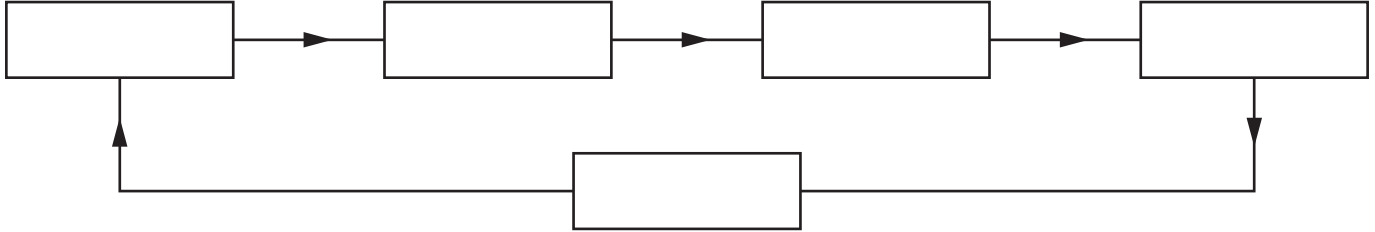


Fig. 1

Complete the block diagram by filling in the empty boxes using the items listed below.

- Feedback
- Control unit
- Temperature sensor
- Boiler and radiator pump
- Boiler switch

[5]

2 Name **two** types of system that use feedback control other than a central heating system.

(i) .....

(ii) .....

[2]

3 State which **two** of the following are passive transducers.

- Thermistor
- Thermocouple
- Solar cell
- Strain gauge.

(i) .....

(ii) .....

[2]

4 Name **one** input device and **one** output device used in a control system.

Input device .....

Output device ..... [2]

5 Explain what is meant by the term ‘instrument display’.

.....  
.....  
..... [2]

6 State **two** difficulties encountered when transmitting signals using wires when the frequency of the system increases above 2500 MHz.

(i) .....  
(ii) ..... [2]

7 Explain what is meant by the term ‘virtual test equipment’.

.....  
.....  
..... [2]

8 State the formula for overall gain in a system using positive feedback.

..... [1]

9 Explain why it is beneficial to have a video camera in a system capable of monitoring illegal activity.

.....  
.....  
..... [2]

[Section A Total: 20]

**Section B**

Answer any **four** questions in the spaces provided.

- 1 (a) State the function of a strain gauge and give one reason for measuring strain.

.....  
.....  
..... [2]

- (b) State **three** practical applications where a strain gauge is used.

1 .....  
2 .....  
3..... [3]

- (c) Describe in detail, with the aid of a labelled diagram, how a strain gauge circuit is used in a control system.

.....  
.....  
.....  
.....  
.....  
..... [5]

**[Total: 10]**

2 (a) (i) State which type of control system is required to maintain a room at a constant temperature.

.....

(ii) Name an input device used to sense temperature in a control system.

..... [2]

(b) Explain why it is important to monitor and control the temperature of a room.

.....  
.....  
.....

..... [3]

Fig. 2 shows a diagram of a control system.

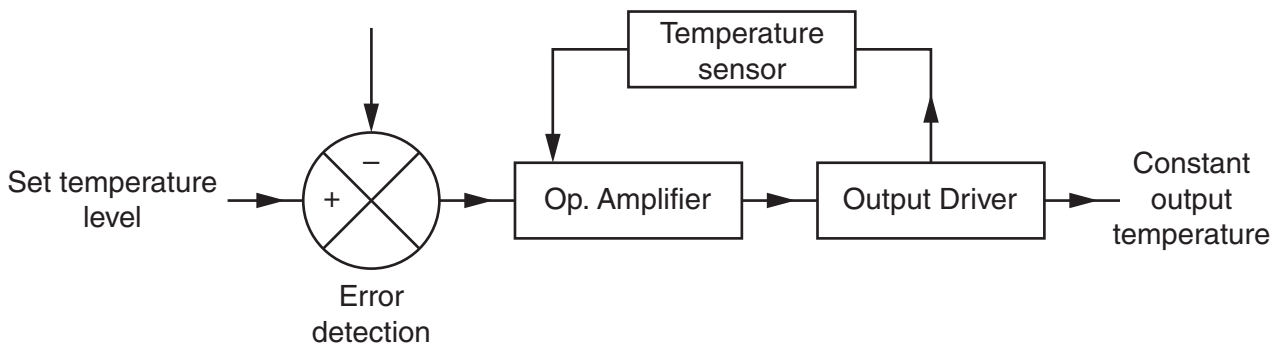


Fig. 2

(c) Describe in detail, how the system in Fig. 2 can be used to control the temperature of a room.

.....  
.....  
.....  
.....  
.....

..... [5]

[Total: 10]

3 (a) Give the meaning of the term 'closed loop' control.

.....  
.....  
..... [2]

(b) Explain, using an example, the advantages of a closed loop control system over an open loop control system.

.....  
.....  
.....  
..... [3]

(c) Describe in detail, with the aid of a labelled block diagram, how a mechanical closed loop system can be used to maintain the level of water in a storage tank.

.....  
.....  
.....  
.....  
.....  
..... [5]

[Total: 10]

4 (a) Draw, in the space provided, the symbol for the following pneumatic components:

(i) a single acting spring return cylinder.

[1]

(ii) a double acting cylinder.

[1]

(b) Explain how a single acting cylinder is used in a pneumatic control system.

.....  
.....  
.....  
..... [3]

(c) Describe in detail, with the aid of a labelled diagram, how a double-acting cylinder can be used with a five-port valve.

.....  
.....  
.....  
.....  
.....  
.....  
..... [5]

[Total: 10]

5 (a) Give **two** practical applications where a pressure gauge is used.

1 .....

2 ..... [2]

(b) Explain the difference between absolute pressure and gauge pressure.

.....

.....

.....

..... [3]

(c) Describe in detail, with the aid of a diagram, the construction and action of a bellows pressure gauge. Show how a change in pressure is converted into an analogue electrical signal.

.....

.....

.....

.....

.....

..... [5]

[Total: 10]



6 (a) Draw a labelled circuit diagram of an ideal operational amplifier.

[2]

(b) Name **three** characteristics of an ideal operational amplifier.

1 .....

2 .....

3 ..... [3]

(c) (i) An amplifier with a voltage gain of 20000 is used in a negative feedback circuit with a feedback fraction of 0.02.  
Calculate, correct to two decimal places, the overall gain.

.....

.....

.....

..... [2]

(ii) An amplifier having an open loop gain of 600 has overall negative feedback applied which reduces the overall gain to 100.  
Calculate the value of the feedback fraction.

.....

.....

..... [3]

[Total: 10]

- 7 (a) Draw a block diagram for an analogue-to-digital (A to D) converter. Show on your block diagram a typical input and output signal.

[2]

- (b) Explain why it is better to use an R-2R ladder DA converter as compared to a binary-weighted DA converter.

.....  
.....  
.....  
..... [3]

- (c) Describe in detail, with the aid of a circuit diagram, the principle of operation of an R-2R ladder DA converter.

.....  
.....  
.....  
.....  
.....  
..... [5]

[Total: 10]

8 (a) Give **two** practical applications for a liquid crystal display (LCD).

1 .....

2 ..... [2]

(b) Explain the advantages of using liquid crystal displays over other types of display.

.....

.....

.....

..... [3]

(c) Explain in detail, with the aid of diagrams, the difference between a transmissive mode LCD and a reflective mode LCD.

.....

.....

.....

.....

.....

..... [5]

[Total: 10]

[Section B Total: 40]

**PLEASE DO NOT WRITE ON THIS PAGE**



**Copyright Information**

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website ([www.ocr.org.uk](http://www.ocr.org.uk)) after the live examination series. If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.