Modified Enlarged 24pt

OXFORD CAMBRIDGE AND RSA EXAMINATIONS

Thursday 9 January 2020 – Afternoon

Level 1/2 Cambridge National in Systems Control in Engineering

R113/01 Electronic principles

Time allowed: 1 hour
plus your additional time allowance

YOU MUST HAVE:
a scientific or graphical calculator

Please write clearly in black ink.

Centre number | | | | | |

Candidate number | | | | |

First name(s) _____

Last name _____

READ INSTRUCTIONS OVERLEAF

© OCR 2019 [A/505/3542]
DC (PQ/SW) 198555

91607935 31

INSTRUCTIONS

Use black ink. You can use an HB pencil, but only for graphs and diagrams.

Write your answer to each question in the space provided. If you need extra space use the lined pages at the end of this booklet. The question numbers must be clearly shown.

Answer ALL the questions.

INFORMATION

The total mark for this paper is 60.

The marks for each question are shown in brackets [ ].

Quality of written communication will be assessed in questions marked with an asterisk (*).

ADVICE

Read each question carefully before you start your answer.

BLANK PAGE

Answer ALL the questions.

1 (a) Complete the table by naming the component for each electronic symbol shown.
Part of each answer has been given for you. [4]

Symbol	Component
	polarised _____
	_____ lamp
	_____ to _____ switch
	_____ resistor

(b) Calculate the resistance in ohms of a lamp rated at 12 volts 0.5 amperes.

_____

_____

_____

_____ [3]

(c) Calculate the energy in kilowatt hours when a 900 watt hairdryer is used for 10 minutes.

_____

_____

_____

_____ [3]

(d) Circle the TWO polarised capacitors in the list of capacitor types below. [2]

ceramic	polyester	electrolytic
polystyrene	tantalum	

2 (a) Complete the table by identifying which components are INPUT devices and which are OUTPUT devices.
The first one has been done for you. [6]

Component	Type of Device
Solenoid	Output
Relay	
Microphone	
Phototransistor	
Pressure switch	
Light Emitting Diode	
Touch screen	

(b) The diagram below shows a resistor and a colour code chart.

Colour	Band 1	Band 2	Band 3	Band 4
Black	0	0	×1	
Brown	1	1	×10	±1%
Red	2	2	×100	±2%
Orange	3	3	×1 K	
Yellow	4	4	×10 K	
Green	5	5	×100 K	±0.5%
Blue	6	6	×1 M	±0.25%
Violet	7	7	×10 M	
Grey	8	8		
White	9	9		
Gold			×0.1	±5%
Silver			×0.01	±10%

(i) State the value of a resistor colour coded Brown, Grey, Red and Gold.

_____

_____ [3]

(ii) State why resistors of different power ratings are available.

_____ [1]

3 A multimeter is used to test electronic circuits.

(a) Name FOUR other pieces of equipment that are used to test electronic circuits.

1 _____

2 _____

3 _____

4 _____

[4]

(b) (i) Describe FOUR stages in using a multimeter to test for continuity in a fuse.

_____

_____

_____

_____

_____

_____

_____

_____ [4]

(ii) Give TWO other specific uses for a multimeter.

1 _____

2 _____

[2]

4 (a) Complete the table below by naming THREE benefits and THREE drawbacks of using surface mount components in commercial circuit construction.

The first one has been done for you. [6]

Statement	Benefit or Drawback
The components of SMT are smaller.	Benefit
Fewer holes need to be drilled onto the circuit board.	
Large, high-power or high-voltage parts are unsuitable for surface mount construction.	
Manual prototype or component level repair is more difficult.	
Skilled operators are needed with expensive tools as the parts are much smaller.	
Components can be placed on either side of the circuit boards.	
Better mechanical performance under shake and vibration conditions.	

(b) **Visual Inspection is one method used within quality assurance in commercial printed circuit board (PCB) production.**
Describe the visual checks that the manufacturer can carry out.

_____

_____

_____

_____

_____

_____ **[4]**

5 (a)* Discuss the function and applications of a Liquid Crystal Display (LCD) module.

[6]

(b) A typical seven segment LCD module is shown in Fig. 1.

FIG. 1

Label each segment shown in Fig. 1 with the correct letters A to G and DP. [4]

6 (a) Fig. 2 shows a linear integrated circuit (IC).

FIG. 2

(i) State the name of the component shown at positions Q_1 to Q_5 in Fig. 2.

_____ [2]

(ii) State the name that is given to the group of components arranged as shown in Fig. 2.

_____ [2]

(b) **Draw a labelled diagram that shows the connections for a Darlington Pair. Use the space below. [4]**

END OF QUESTION PAPER

ADDITIONAL ANSWER SPACE

If additional space is required, you should use the following lined page(s). The question number(s) must be clearly shown in the margin(s).

BLANK PAGE

BLANK PAGE

OCR
Oxford Cambridge and RSA

Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact The OCR Copyright Team, The Triangle Building, Shaftesbury Road, Cambridge CB2 8EA.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.